


L 25 Electricity and Magnetism [3]

- Electric circuits
 - what conducts electricity
 - what does and doesn't conduct electricity
- Current, voltage and resistance
 - Ohm's Law
 - Power loss due to heat produced in a resistor
- Simple circuit connections

1

Electric current (symbol I)

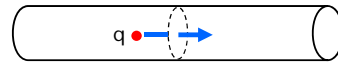- Electric current is the flow of electric charge q



- It is the amount of charge q that passes a given point in a wire in a time t :

$$I = \frac{q}{t}$$

- Current is measured in **amperes**
- **1 ampere (A) = 1 C / 1 s**

2

Examples

- A charge of 1 microcoulomb (10^{-6} C) passes through a wire every millisecond (10^{-3} s). What is the current in the wire?
 $\rightarrow I = q/t = 10^{-6} \text{ C} / 10^{-3} \text{ s} = 10^{-6+3} \text{ s} = 10^{-3} \text{ A}$
 $= 1 \text{ milliamp} = 1 \text{ mA}$
- A current of 3 A flows in a wire. Over a period of 1 minute, how much charge passes a given point in the wire?
 $\rightarrow q = I \times t = 3 \text{ A} \times 60 \text{ s} = 180 \text{ C}$

3

Potential difference or Voltage (symbol V)

- To make water flow in a pipe, a pressure difference must be applied between the ends of the pipe
- A potential difference or **voltage** must be applied between the ends of a conductor to make the electrons flow
- Voltage is supplied by a battery (DC) or a an electrical outlet (AC)


4


Electrical resistance (symbol R)

- Conductors have "free electrons" that roam around randomly \rightarrow no current
- To push these free electrons through a conductor, i.e., to make a **current**, some external force must be applied to the conductor
- This external force must be continually applied because the electrons experience a **resistance** to motion, because they keep bumping into the atoms and slowing down
- The slowing down of the electrons is called "resistance" (**R**) and is measured in Ohms (Ω)
- The battery provides the external force (**voltage**) that keeps the electrons moving

5

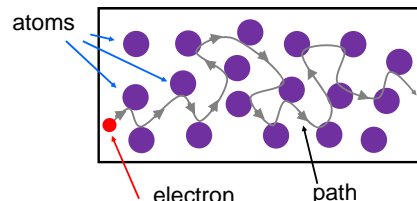
Electrons pass through an obstacle course in a conductor



- The **resistance (R)** is a measure of the degree to which the conductor impedes the flow of current
- We use the symbol  to represent the electrical resistance in a circuit


6

A battery is a charge pump

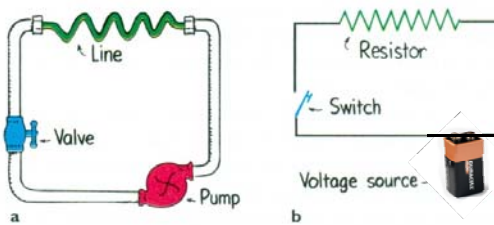

7


Direction of current flow

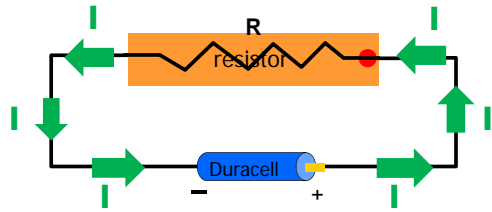

By convention, the current direction is taken as the direction that positive charges would flow, so it is *opposite* to the electron flow

8

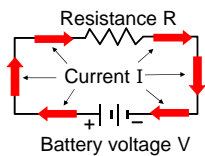Current, Voltage and Resistance: OHM'S LAW



R could represent, the resistance of a light bulb, hair dryer, coffee pot, vacuum cleaner, etc.

- **Ohm's law** is a relation between current (I), voltage (V) and resistance (R)
- **$I = \text{Voltage} / \text{Resistance} = V / R$**
 - V in volts (V), R in ohms (Ω), I in amps (A)
 - equivalent forms: $V = I R$, $I = V / R$, $R = V / I$

9

Examples

- (1) If a 3 volt flashlight bulb has a resistance of 9 ohms, how much current will it draw?

$$\rightarrow I = V / R = 3 \text{ V} / 9 \Omega = 1/3 \text{ A (Ampere)}$$

- (2) If a light bulb draws 2 A of current when connected to a 120 volt circuit, what is the resistance of the light bulb?

$$\rightarrow R = V / I = 120 \text{ V} / 2 \text{ A} = 60 \Omega \text{ (Ohms)}$$

10

Heat produced in a resistor

- As we have seen before, friction causes heat
- The collisions between the electrons and the atoms in a conductor produce heat \rightarrow wires get **warm** when they carry currents: **in an electric stove this heat is used for cooking**
- The amount of energy converted to heat each second is called the **power loss in a resistor**
- If the resistor has a voltage V across it and carries a current I, the electrical power converted to heat is given by
- **Power: $P = I \times V = I \times (I \times R) = I^2 \times R$**

From Ohm's law



11

Heat produced in a resistor

- Power $\rightarrow P = I \times V$ or $I^2 \times R$
- Power is measured in **Watts = amps \times volts**
- One Watt is one Joule per second
- Wires are rated for the maximum current that can be handled based on how hot it can get
- To carry more current you need wire of a larger diameter \rightarrow this is called the wire gauge, the lower the gauge the more current it can carry
- Using extension cords can be dangerous!

12

examples

- How much current is drawn by a 60 Watt light bulb connected to a 120 V power line?
- Solution:** $P = 60 \text{ W} = I \times V = I \times 120$
so $I = 0.5 \text{ Amps (A)}$
- What is the resistance of the bulb?
- Solution:** $V = I R \rightarrow 120 \text{ V} = 0.5 \text{ A} \times R$
so $R = 240 \Omega$, or $R = V/I$



How much current is used by a 2000 W hair dryer plugged into a 120 V power source?
 $\rightarrow P = I V \rightarrow I = P / V = 2000 \text{ W} / 120 \text{ V} \approx 17 \text{ A}$



13

extension cords and power strips

- extension cords are rated for maximum current \rightarrow you must check that whatever is plugged into it will not draw more current than the cord can handle safely.
- power strips are also rated for **maximum current** \rightarrow since they have multiple inputs you must check that the total current drawn by everything on it does not exceed the posted **current rating**

14

Unsafe practices

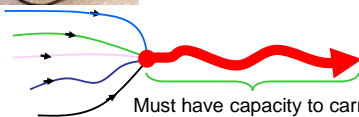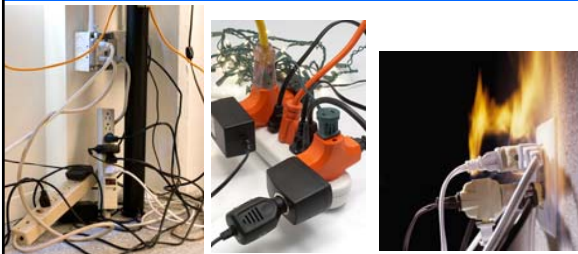

Must have capacity to carry all current 15

Parallel and Series Connections


- Parallel connection**
 - All bulbs have the same voltage = 12 V.
 - The current provided by the battery is divided equally among the 3 light bulbs.

- Series connection**
 - The same current passes through each light bulb.
 - Each bulb has a voltage of 4 V across it.

16

Simple direct current (DC) electric circuits

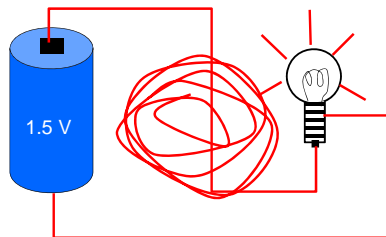Exercise: given a battery, some wire and a light bulb, connect them so that the bulb is on.



The battery polarity +/- does not matter, Either way the bulb Will be on.

17

Electric circuits - key points

- Electrons carry the current in a conductor
- a circuit provides a closed path for the electrons to circulate around
- Conductors have a property called resistance which impedes the flow of current
- the battery is like a pump that re-energizes the electrons each time they pass through it
- Ohm's law is the relation between current, voltage and resistance: **$V = I R$**
- When current passes through a wire, the wire heats up, the amount of heat energy produced each second (Power) is **$P = I V = I^2 R$**

18


What is DC (direct current) ?

- With DC or direct current the current always flows in the same direction
- **this is the type of current you get when you use a battery as the voltage source.**
- the direction of the current depends on how you connect the battery
- **the electricity that you get from the power company is not DC it is AC (alternating).**
- We will discuss AC in the next lecture

19


connecting batteries → do's and don'ts

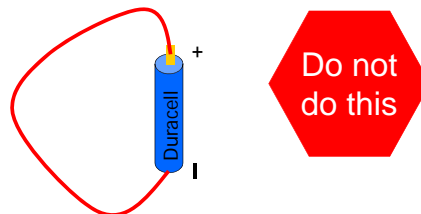don't connect a wire from the + side to the – side, this shorts out the battery and will make it get hot and will shorten its lifetime.



20

dueling batteries

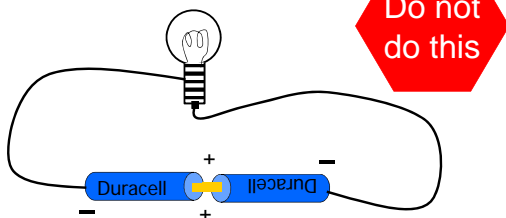


The batteries are trying to push currents in opposite directions → they are working against each other. This does not work.

21

Proper battery connections

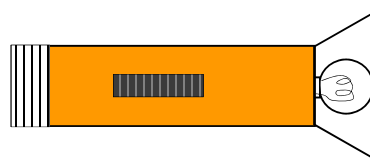
Connecting two 1.5 volt batteries gives like this gives 3.0 volts.



A Flashlight!

22

Batteries in parallel

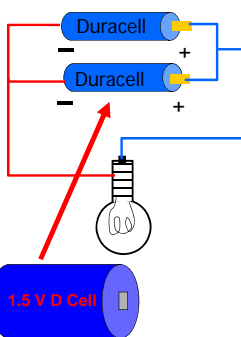


This connection still gives 1.5 volts but since there are 2 batteries **it will provide electrical current for a longer time**



23

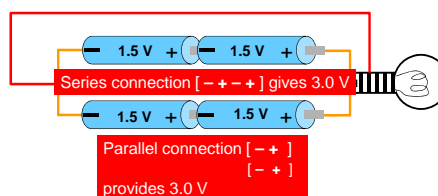Longer lasting power series and parallel combination



This connection provides 3.0 volts and will provide power for a longer amount of time

24

Disposable vs. Rechargeable Batteries

- **Disposable batteries** are electrochemical cells that convert chemical energy into electrical energy. Because the electrode materials are irreversibly changed during discharge, they must be replaced
- **Rechargeable batteries** are also electrochemical cells, but use materials in which the chemical reactions can be reversed in the recharging process

25