

8)

there are two important observations

(1) the current through all devices
in this circuit are identical

(2) the charges on all capacitors
are identical because there is
no net charge in the devices
connecting the capacitors

using the loop equations

$$0 = \sum L_n \frac{dI_n}{dt} + \sum R_n I_n + \sum \frac{Q_n}{C_n}$$
$$= \frac{dI}{dt} (\sum L_n) + I (\sum R_n) + Q (\sum \frac{1}{C_n})$$

this behaves like an RLC circuit with

$$L = \sum_n L_n \quad R = \sum_n R_n \quad \frac{1}{C} = \sum_n \frac{1}{C_n}$$

#21) $C = 64 \times 10^{-6} \text{ F}$

$$I(t) = (1.6 \text{ A}) \sin(2500t + .680)$$

a) $2500t + .680 = \frac{\pi}{2}$

$$t = \left(\frac{\pi}{2} - .680\right) / 2500 = 3.56 \times 10^{-4} \text{ s}$$

b) $\omega = \frac{1}{\sqrt{LC}} \quad L = \frac{1}{C\omega^2} = \frac{1}{(64 \times 10^{-6} \text{ F})(2500 \text{ s}^{-1})^2} = 2.5 \times 10^{-3} \text{ H}$

c) $\mathcal{E} = \frac{1}{2} LI^2 \max = \frac{1}{2} (1.6 \text{ A})^2 \times (2.5 \times 10^{-3}) = 3.2 \times 10^{-3} \text{ J}$

$$25) \quad q(t) = q(0) e^{-Rt/2L} \cos(\omega't + \phi)$$

$$\omega' = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

$$L = 220 \times 10^{-3} \text{ H}$$

$$C = 12 \times 10^{-6} \text{ F}$$

The time for 50 cycles is

$$\omega't = 50 \times 2\pi$$

$$t = 50 \times 2\pi / \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

In that time

$$\left| \frac{q(t)}{q(0)} \right| = e^{-Rt/2L} = .99$$

$$\ln .99 = -Rt/2L$$

$$\ln .99 = -\left(\frac{R}{2L}\right) 50 \times 2\pi \frac{1}{\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}}$$

$$(\ln .99)^2 \left(\frac{1}{LC} - \left(\frac{R}{2L}\right)^2\right) = \left(\frac{R}{2L}\right)^2 (50 \times 2\pi)^2$$

$$(\ln .99)^2 \frac{1}{LC} = \left(\frac{R}{2L}\right)^2 \left((50 \times 2\pi)^2 - \underbrace{(\ln .99)^2}_{\text{small compared to } (50 \times 2\pi)^2} \right)$$

small compared to $(50 \times 2\pi)^2$

$$\frac{R}{2L} \approx \frac{|\ln .99|}{\sqrt{LC}} \frac{1}{50 \times 2\pi}$$

$$R = \frac{|\ln .99|}{50 \pi} \sqrt{\frac{L}{C}} = \frac{|\ln .99|}{50 \cdot \pi} \sqrt{\frac{220 \times 10^{-3} \text{ H}}{12 \times 10^{-6} \text{ F}}}$$

$$= 8.66 \times 10^{-3} \Omega$$

$$27) \quad u = \frac{1}{2} q^2 / c$$

$$= \frac{1}{2} \frac{q(\omega)^2}{c} e^{-Rt/L} \cos^2(\omega't + \phi)$$

In one cycle $\omega \Delta t = 2\pi$ $\Delta t = 2\pi/\omega'$

$$\Delta u = \frac{1}{2} \frac{q(\omega)^2}{c} \left(e^{-Rt/L} - e^{-R(t+\Delta t)/L} \right) \cos^2(\omega't + \phi)$$

$$= \frac{1}{2} \frac{q(\omega)^2}{c} e^{-Rt/L} \left(1 - e^{-R\Delta t/L} \right) \cos^2(\omega't + \phi)$$

$$\frac{\Delta u}{u} = \left(1 - e^{-R\Delta t/L} \right) \approx \frac{R\Delta t}{L} = \frac{2\pi R}{L\omega'} \approx \frac{2\pi R}{L\omega}$$

(If the loss is small per cycle then $\omega' \approx \omega$)

$$35) \quad I = \frac{\mathcal{E}_0}{Z} \cos(\omega t + \phi)$$

$$L = 88 \times 10^{-3} \text{H}$$

$$C = .94 \times 10^{-6} \text{f}$$

$$\omega = 2\pi \times 930 \text{ s}^{-1}$$

$$\mathcal{E} = \mathcal{E}_0 \cos(\omega t)$$

$$\frac{X_C - X_L}{R} = \tan \phi$$

$$R = \cot \phi \left(\frac{1}{C\omega} - L\omega \right)$$

$$= \cot(75^\circ) \left(\frac{1}{.94 \times 10^{-6} \times 2\pi \times 930} - 88 \times 10^{-3} \times 2\pi \times 930 \right)$$

$$= 8.9 \times 10^1$$

this circuit is inductive — we should have $\phi = -75^\circ$

$$53) \quad R = 12 \, \Omega \quad X_L = 1.3 \, \Omega \quad \mathcal{E}_{\text{rms}} = 120 \, \text{V}$$

$$a) \quad Z = \sqrt{R^2 + X_L^2} = 12.07 \, \Omega$$

$$b) \quad P = I_{\text{rms}}^2 R = \left(\frac{\mathcal{E}_{\text{rms}}}{Z} \right)^2 R = \mathcal{E}^2 \frac{R}{Z^2}$$

$$= (120)^2 \frac{12}{12^2 + 1.3^2}$$

$$= 1.18 \times 10^3 \, \text{Watts}$$

56) The power supplied to the light bulb is

$$P = \mathcal{E}^2 \frac{1}{Z} \cdot \frac{R}{Z} = \mathcal{E}^2 \frac{R}{L^2 + R^2}$$

to find L max

$$a) \quad \frac{1}{5} P = \frac{1}{5} \frac{\mathcal{E}^2}{R} = \mathcal{E}^2 \frac{R}{L^2 + R^2} \quad (1)$$

$$1 = \frac{5R^2}{L^2 + R^2} \Rightarrow L^2 = 4R^2 \quad L = 2R$$

$$\therefore L = 2 \left(\frac{\mathcal{E}^2}{1000 \, \text{W}} \right) = \frac{2 \times (120)^2}{1000} = 28.8 \, \text{H}$$

d, b) yes - but additional energy would be lost through the other resistor

$$c) \quad I(R_1 + R_2) = \mathcal{E} \quad I = \frac{\mathcal{E}}{R_1 + R_2}$$

$$P_1 = \frac{1}{5} \frac{\mathcal{E}^2}{R} = \frac{\mathcal{E}^2}{(R_1 + R)^2} \cdot R$$

$$1 = \frac{5R^2}{(R_1 + R)^2} \Rightarrow R_1 + R = \sqrt{5} R \quad R_1 = (\sqrt{5} - 1)R$$

$$\begin{aligned} R_1 &= (\sqrt{5} - 1) \times \frac{e^2}{1000 \omega} \\ &= (\sqrt{5} - 1) \frac{(120)^2}{1000} = \\ &= 17.79 \Omega \end{aligned}$$