

Solutions

26.25


$$R = \rho l / A = 6 \Omega$$

Assume that the volume is fixed

$$lA = (3l)(\frac{1}{3}A) \Rightarrow$$

$$R \rightarrow \rho(3l)(\frac{3}{A}) = 9 \times (\rho l / A) = 9 \times 6 \Omega = 54 \Omega$$

26.33



$3.5 \times 10^{-4} \text{ m}^2 = A$ $V = 35.8 \text{ V}$

$l = .158 \text{ m}$ $n = 5.33 \times 10^{22} \text{ e/m}^3$ $R = 935$

$$R = \rho l / A \quad \rho = \frac{RA}{l}$$

(a) $I = \frac{V}{R} = \frac{35.8 \text{ V}}{935 \Omega} = 3.83 \times 10^{-2} \text{ A}$

(b) $J = \frac{I}{A} = \frac{3.83 \times 10^{-2}}{3.5 \times 10^{-4}} = 1.09 \times 10^2 \text{ A/m}^2$

(c) $\frac{I}{A} = J = n v_e$

$$v = \frac{I}{n e A} = \frac{(3.83 \times 10^{-2} \text{ A})}{(5.33 \times 10^{22} \text{ e/m}^3)(1.60 \times 10^{-19} \text{ e})(3.5 \times 10^{-4} \text{ m}^2)} = 1.28$$

$$= 1.28 \times 10^{-2} \text{ m/s}$$

(d) $E = V / l = \frac{35.8 \text{ V}}{.158 \text{ m}} = 2.27 \times 10^2 \text{ V/m}$


26.45

a) $I = \frac{P}{V} = \frac{1250 \text{ W}}{115 \text{ V}} = 10.9 \text{ A}$

b) $R = \frac{V}{I} = \frac{115 \text{ V}}{10.9 \text{ A}} = 10.6 \Omega$

c) $E = PT = (1250)(60 \times 60) \text{ s} = 4.5 \times 10^6 \text{ J}$

27.16

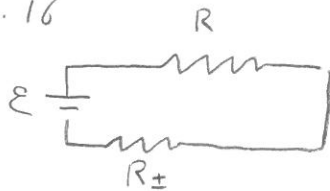

$$\mathcal{E} - I(R + R_{\pm}) = 0$$

$$IR = \mathcal{E} - IR_{\pm} = V$$

$$I = V/R$$

We have two unknowns \mathcal{E} , R_{\pm}

$$\mathcal{E} - \frac{V_1}{R_1} R_{\pm} = V_1$$

$$\mathcal{E} - \frac{V_2}{R_2} R_{\pm} = V_2$$

$$(V_1 - V_2) = \left(\frac{V_2}{R_2} - \frac{V_1}{R_1} \right) R_{\pm}$$

$$a) \quad R_{\pm} = \frac{V_1 - V_2}{\left(\frac{V_2}{R_2} - \frac{V_1}{R_1} \right)} = \frac{0.1 - 0.15}{0.15/1000 - 0.1/500} = 1 \times 10^{-3} \Omega$$


$$b) \quad \mathcal{E} = V_1 \left(1 + \frac{1}{R_1} \frac{V_1 - V_2}{\frac{V_2}{R_2} - \frac{V_1}{R_1}} \right) = (0.1V) \left(1 + \frac{1 \times 10^{-3} \Omega}{500 \Omega} \right) = 0.3V$$

$$c) \quad \frac{\text{Power out}}{\text{Power in}} \times 100 = \left(\frac{V^2}{R} \right) \cdot \left(\frac{1}{2 \times 10^{-3} \text{ W/cm}^2 \cdot 5 \text{ cm}^2} \right) \times 100$$

$$= \frac{(0.15)^2}{1000} \cdot \frac{1}{10^{-3} \text{ W}} \times 100$$

$$= 2.25 \%$$

27.22

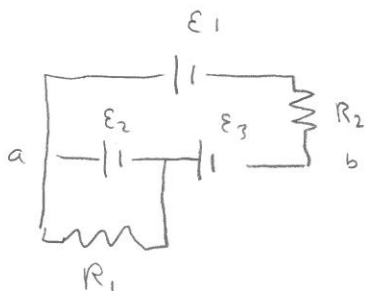

$$R_1 = 100 \Omega$$

$$R_2 = 50 \Omega$$

$$\mathcal{E}_1 = 6V$$

$$\mathcal{E}_2 = 5V$$



$$\mathcal{E}_3 = 4V$$

$$a) \quad I_1 = \frac{\mathcal{E}_2}{R_1} = \frac{5V}{100 \Omega} = 5 \times 10^{-2} A$$

$$b) \quad I_2 = \frac{\mathcal{E}_1 - \mathcal{E}_2 - \mathcal{E}_3}{R_2} = \frac{6 - 5 - 4}{50 \Omega} V = -\frac{3V}{50 \Omega} = -6 \times 10^{-2} A$$

$$c) \quad V_a - V_b = \mathcal{E}_2 + \mathcal{E}_3 = 5V + 4V = 9V$$

27.62

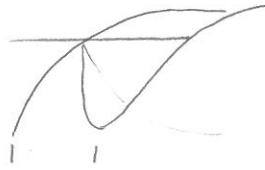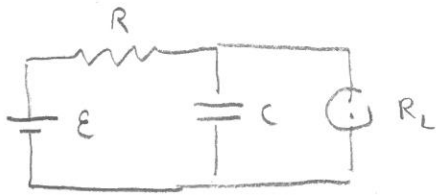

We assume that the lamp discharges quickly so the time between flashes is the time needed to charge the capacitor to 72V

$$V(t) = \frac{Q(t)}{C} = \mathcal{E} \left(1 - e^{-t/RC} \right)$$


$$\frac{V}{\mathcal{E}} = 1 - e^{-t/RC} \quad e^{-t/RC} = 1 - \frac{V}{\mathcal{E}}$$

$$-t/RC = \ln \left(1 - \frac{V}{\mathcal{E}} \right) =$$

$$RC = t \frac{1}{\ln \left(\frac{\mathcal{E}}{\mathcal{E} - V} \right)}$$

$$R = \frac{t}{C} \frac{1}{\ln \left(\frac{\mathcal{E}}{\mathcal{E} - V} \right)} = \left(\frac{0.5 \text{ s}}{.15 \times 10^{-6} \text{ F}} \right) \times \frac{1}{\ln \left(\frac{95}{23} \right)} = 2.35 \times 10^6 \Omega$$

27.80

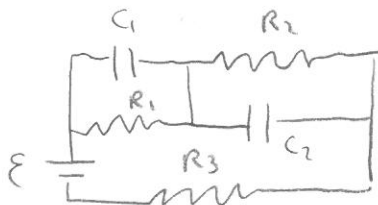

at steady state there is no current through the capacitors so

$$\mathcal{E} = I(R_1 + R_2 + R_3) \Rightarrow I = \frac{\mathcal{E}}{R_1 + R_2 + R_3}$$

$$V_{C_1} = IR_2 = \frac{\mathcal{E}R_2}{R_1 + R_2 + R_3}$$

$$V_{C_2} = IR_3 = \frac{\mathcal{E}R_3}{R_1 + R_2 + R_3}$$

$$\begin{aligned} \mathcal{U}_{C_1} &= \frac{1}{2} C_1 V_{C_1}^2 = \frac{1}{2} C_1 \frac{\varepsilon^2 R_1^2}{(R_1 + R_2 + R_3)^2} \\ &= \frac{1}{2} (5 \times 10^{-6} \text{ F}) \frac{(20 \text{ V})^2 (5)^2}{(5 + 10 + 15)^2} \\ &= 2.78 \times 10^{-5} \text{ J} \end{aligned}$$

$$\begin{aligned} \mathcal{U}_{C_2} &= \frac{1}{2} C_2 V_{C_2}^2 = \frac{1}{2} C_2 \frac{\varepsilon^2 R_2^2}{(R_1 + R_2 + R_3)^2} \\ &= \frac{1}{2} (10 \times 10^{-6}) \frac{(20 \text{ V})^2 (10)^2}{(5 + 10 + 15)^2} \\ &= 8 \times \mathcal{U}_{C_1} = 5 \times 10^{-4} \text{ Joules} \end{aligned}$$