

## HW Solutions

53

$$L = 6.3 \times 10^{-6} \text{ H}$$

$$R = 1.2 \times 10^3 \Omega$$

$$\mathcal{E} = 14 \text{ V}$$

$$\mathcal{E}(t) = L \frac{dI}{dt} + IR \Rightarrow I(t) = \frac{\mathcal{E}}{R} \left( 1 - e^{-\frac{tR}{L}} \right)$$

$$a) \quad .8 \frac{\mathcal{E}}{R} = \frac{\mathcal{E}}{R} \left( 1 - e^{-\frac{tR}{L}} \right)$$

$$.2 = e^{-\frac{tR}{L}}$$

$$\ln\left(\frac{1}{5}\right) = -\frac{tR}{L} = -\ln 5$$

$$t = \frac{L}{R} \ln 5 = \frac{6.3 \times 10^{-6} \text{ H}}{1.2 \times 10^3 \Omega} \ln 5 = 8.45 \times 10^{-9}$$

$$b) \quad I(t) = \frac{\mathcal{E}}{R} \left( 1 - e^{-1} \right) = \frac{\mathcal{E}}{R} \left( \frac{e-1}{e} \right)$$

$$= \frac{14 \text{ V}}{1.2 \times 10^3 \Omega} \left( \frac{e-1}{e} \right) = 7.4 \times 10^{-3} \text{ A}$$

57a

$$R = 15 \Omega \quad L = 5 \text{ H} \quad \mathcal{E} = 10 \text{ V}$$

When the switch is closed the current through the fuse is the same as the current through the inductor

$$\mathcal{E} = L \frac{dI}{dt} \Rightarrow \frac{dI}{dt} = \frac{\mathcal{E}}{L} \quad I(t) = \frac{\mathcal{E}}{L} t$$

$$t = \frac{L \cdot I_{\text{max}}}{\mathcal{E}} = \frac{(5 \text{ H})(3 \text{ A})}{(10 \text{ V})} = 1.5 \text{ sec}$$

$$\underline{62} \quad L = 2.0 \text{ H} \quad \mathcal{E} = 100 \text{ V}$$

$$R = 10 \Omega$$

$$I(t) = \frac{\mathcal{E}}{R} (1 - e^{-tR/L})$$

$$\begin{aligned} \text{(a)} \quad \frac{dU_B}{dt} &= \frac{d}{dt} \left( \frac{1}{2} LI^2 \right) = \frac{1}{2} 2 LI \frac{dI}{dt} \\ &= L \frac{\mathcal{E}}{R} (1 - e^{-tR/L}) \frac{\mathcal{E}}{R} \frac{R}{L} e^{-tR/L} \\ &= \frac{\mathcal{E}^2}{R} (e^{-tR/L} - e^{-2tR/L}) \\ &= \frac{(100 \text{ V})^2}{10 \Omega} \left( e^{-\frac{10}{2 \cdot 10}} - e^{-\frac{2 \cdot 10}{2 \cdot 10}} \right) \\ &= 2.39 \times 10^2 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{(b)} \quad \frac{dU_R}{dt} &= I^2 R = \frac{\mathcal{E}^2}{R} (1 - e^{-tR/L})^2 \\ &= \frac{\mathcal{E}^2}{R} (1 - 2e^{-tR/L} + e^{-2tR/L}) \\ &= \frac{(100 \text{ V})^2}{10} \left( 1 - 2e^{-\frac{10}{2 \cdot 10}} + e^{-\frac{2 \cdot 10}{2 \cdot 10}} \right) \\ &= 1.55 \times 10^2 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{(c)} \quad \frac{dU}{dt} &= \mathcal{E} I = \frac{\mathcal{E}^2}{R} (1 - e^{-tR/L}) \\ &= \frac{(100 \text{ V})^2}{10} (1 - e^{-\frac{10}{2 \cdot 10}}) \\ &= 3.94 \times 10^2 \text{ W} \end{aligned}$$

Note  $a + b = c$  so energy is conserved

77

$$a) \quad \mathcal{E} = \underbrace{-L_1 \frac{dI_1}{dt} - M \frac{dI_2}{dt}}_{\text{EMF in coil 1 due to self and mutual inductance}} - \underbrace{L_2 \frac{dI_2}{dt} - M \frac{dI_1}{dt}}_{\text{EMF in coil 2 due to self and mutual inductance}}$$

since  $I_1 = I_2 \Rightarrow$

$$\mathcal{E} = - \underbrace{(L_1 + M + L_2 + M)}_{\text{effective inductance of the 2 coil system}} \frac{dI}{dt}$$



this would change the direction of the flux and induced field in the second coil

It changes the direction of the mutual inductance EMF

$$\mathcal{E} \rightarrow \underbrace{(L_1 - M + L_2 - M)}_{\text{effective } L} \frac{dI}{dt}$$

$$4) \quad u = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} L \frac{d^2 Q}{dt^2}$$

$$a) \quad C = \frac{Q^2}{2u} = \frac{(1,6 \times 10^{-6} \text{ C})^2}{2 \times 140 \times 10^{-6}} = 9,14 \times 10^{-9} \text{ F}$$

$$9) \quad L = 50 \times 10^{-3} \quad C = 4 \times 10^{-6} \text{ F}$$

maximum current  $\Rightarrow \frac{1}{4}$  period  
will be maximum charge

$$\frac{1}{4} T = \frac{1}{4f} = \frac{2\pi}{4\omega} = \frac{\pi}{2} \sqrt{LC}$$

$$\frac{1}{4} T = \frac{\pi}{2} \sqrt{(50 \times 10^{-3})(4 \times 10^{-6})} = 7,02 \times 10^{-4} \text{ s}$$

$$10) \quad f = \frac{\omega}{2\pi} = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}$$

$$L = \frac{1}{4\pi^2 f^2 C} = \frac{1}{4\pi^2 (10 \times 10^3)^2 (6,7 \times 10^{-6} \text{ F})} = 3,78 \times 10^{-3} \text{ H}$$