

Lecture 16

Multiloop circuits

$$V = IR \quad \text{ohms Law}$$

Resistors in series

$$R = \sum_{i=1}^n R_i$$

Resistors in parallel

$$\frac{1}{R} = \sum_{i=1}^n \frac{1}{R_i}$$

Power Dissipated

$$P = IV = I^2R = V^2/c$$

Ideal EMF device

$$\begin{array}{c} + \\ | \\ - \end{array} \quad \mathcal{E}$$

does work

key concepts

① charge conservation

* net current into any junction
is 0

② energy conservation

* work done moving a charge
to its original position is 0 \Rightarrow
potential does not change
around a closed loop

Steps

① draw circuit



Resistors EMF Capacitors Switches


label components

Draw arrows indicating guessed current direction

label currents


② require current conservation at each vertex

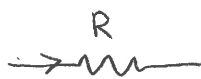require potential conservation around any closed loop



$$V = IR$$

decreases
in direction
of arrow

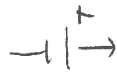

$$V = \mathcal{E}$$


increases
in direction
of arrow



$$V = Q/C$$

③ determining number of unknowns

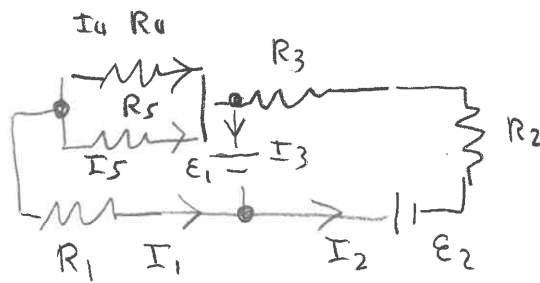construct equations using
loops and vertex equations



vertex equations •

$$I_1 + I_3 = I_2$$

$$I_2 + I_4 + I_5 = I_3$$

$$0 = I_1 + I_4 + I_5$$

loop equations:

$$-R_5 I_5 + R_4 I_4 = 0$$



$$I_5 R_5 - I_1 R_1 - E_1 = 0$$

$$E_2 - I_2 R_2 - I_3 R_3 + E_1 = 0$$

there are additional loop equations
 this gives a system of 5 linear equations that can be solved for the currents

these can be put in the form of a matrix equation that can be solved using methods of linear algebra.

In this case we can replace

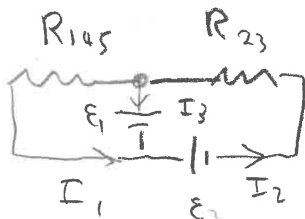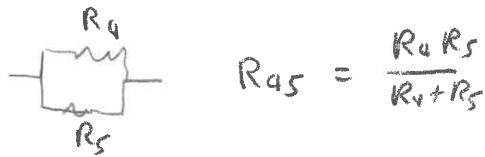

$$E_1 - I_1 R_{145}$$

$$- E_1 - E_2 - I_2 R_3 = 0$$

$$I_1 + I_3 = I_2$$

$$I_1 = \frac{E_1}{R_{145}}$$

$$I_2 = - \frac{(E_1 + E_2)}{R_3}$$

$$I_3 = - \frac{(E_1 + E_2)}{R_3} - \frac{E_1}{R_{145}}$$

given these we use

$$I_5 = (E_1 + I_1 R_1) / R_5$$

$$I_4 = \frac{R_5}{R_4} I_5 = (E_1 + I_1 R_1) / R_4$$

so we can get some simplification using combined circuit elements

EMF devices

① convert chemical or mechanical energy into electrical energy

this in turn can be converted to energy in a device

The power is the rate of change of energy.

$$dW = V dq$$

$$\frac{dW}{dt} = V \frac{dq}{dt} = VI = P$$

combining this with ohm's law

$$P = VI = I^2 R = V^2/R$$

consider a 100 watt light bulb →

$$VI = 100 = V^2/R = (110)^2/R$$

$$\boxed{R = 121 \Omega}$$

next consider the power dissipated by 2 light bulbs in series or parallel.

series: for fixed potential difference

$$R = 2R_1$$

$$P = V^2/R \rightarrow V^2/2R$$

parallel

$$R = \frac{R R}{R+R} = \frac{1}{2} R$$

$$P = V^2/(\frac{1}{2}R) = 2V^2/R$$

By putting the bulbs in parallel 4 times as much power is dissipated than if they are in series - in fact 2 bulbs in series use less power than one in series.

This is why home wiring is in parallel.

Meters: Volts Amps



For a volt meter the goal is to minimize the current through the meter

$$R_{||} = \frac{R R_m}{R_m + R} = \frac{R}{1 + R/R_m}$$

($R_m \gg R \Rightarrow R_{||} \sim R$ so IR does not

We treat this using energy conservation

$$\mathcal{E} - \frac{Q}{C} - IR = 0 \quad \left(\begin{array}{l} \text{change in} \\ \text{potential around} \\ \text{a loop} = 0 \end{array} \right)$$

recall that $I = \frac{dQ}{dt}$, using this
in the above equation gives

$$\boxed{R \frac{dQ}{dt} + \frac{Q}{C} - \mathcal{E} = 0}$$

this is called a differential equation
this can be solved using

$$\frac{dQ}{dt} = \frac{1}{R} \left(\mathcal{E} - \frac{Q}{C} \right)$$

We write this as

$$dQ = \frac{1}{R} \left(\mathcal{E} - \frac{Q}{C} \right) dt$$

$$dt = \frac{dQ}{\frac{1}{R} \left(\mathcal{E} - \frac{Q}{C} \right)}$$

We assume $Q(t=0) = 0$; then

$$\int_0^t dt = \int_0^{Q(t)} \frac{dQ}{\frac{1}{R} \left(\mathcal{E} - \frac{Q}{C} \right)}$$

$$\text{Let } u = \frac{1}{R} \left(\mathcal{E} - \frac{Q}{C} \right)$$

$$du = -\frac{1}{RC} dQ$$

$$dQ = -RC du$$

$$\text{at } t=0 \quad Q=0 \quad u = \frac{\mathcal{E}}{R}$$

$$\int_0^t = \int_{\mathcal{E}/R}^{u(t)} \left(-RC \frac{du}{u} \right) \Rightarrow RC \ln \left(\frac{u}{\mathcal{E}/R} \right) = t$$

$$\ln \left(\frac{u}{\mathcal{E}/R} \right) = -\frac{t}{RC}$$

$$e^{\ln \left(\frac{u}{\mathcal{E}/R} \right)} = e^{-t/RC}$$

$$u = \frac{\mathcal{E}}{R} e^{-t/RC} = \frac{\mathcal{E}}{R} - \frac{Q}{RC}$$

$$\frac{Q}{RC} = \frac{\mathcal{E}}{R} \left(1 - e^{-t/RC} \right)$$

$$\boxed{Q(t) = C\mathcal{E} \left(1 - e^{-t/RC} \right)}$$

this indicates that the charge starts at 0, and eventually reaches $C\mathcal{E}$.

We can also determine the current in the resistor

$$I(t) = \frac{dQ}{dt} = CE(-(-\frac{1}{RC})e^{-t/RC})$$

$$I(t) = \frac{E}{R} e^{-t/RC}$$

In this case the current starts at $\frac{E}{R}$ and exponentially goes to 0,

since t/RC must be dimensionless, then $RC = \tau$ has dimension of time, it is called the time constant. - it increases with increasing R or C .

We can also consider discharging a capacitor. In this case $E=0$

$$R \frac{dQ}{dt} + \frac{Q}{C} = 0$$

This is the same equation with $E=0$. In this case the initial $Q = Q_0$.

$$\frac{dQ}{Q} = - \frac{dt}{RC}$$

integrating

$$\int_{Q_0}^Q \frac{dQ'}{Q'} = \int_0^t -\frac{dt}{RC}$$

$$\ln Q - \ln Q_0 = -t/RC$$

$$\ln\left(\frac{Q}{Q_0}\right) = -\frac{t}{RC}$$

$$e^{\ln\left(\frac{Q}{Q_0}\right)} = e^{-t/RC}$$

$$\boxed{Q = Q_0 e^{-t/RC}}$$

as t gets large the charge on the capacitor decrease to 0. The current is

$$I = \frac{dQ}{dt} = -\frac{Q_0}{RC} e^{-t/RC}$$

The power $V = Q/C$

$$P = IV = \left(-\frac{Q_0}{RC} e^{-t/RC}\right) \left(\frac{Q_0}{C} e^{-t/RC}\right)$$

$$P = -\frac{Q_0^2}{RC^2} e^{-2t/RC}$$

We can use this to find the energy stored in the capacitor

$$E = \int_0^{\infty} P dt = -\frac{Q_0^2}{RC^2} \int_0^{\infty} e^{-2t/RC}$$

$$= -\frac{Q_0^2}{RC^2} \cdot \frac{RC}{2} \int_0^{\infty} e^{-u} du$$

$$= -\frac{Q_0^2}{C} \left(-e^{-\infty} - -e^{-0}\right)$$

$$u = 2t/RC$$

$$du = \frac{2}{RC} dt$$

$$dt = \frac{RC}{2} du$$

$$= -\frac{1}{2} \frac{Q_0^2}{C}$$

This shows that the energy lost by the capacitor is exactly the stored energy. For small RC it discharges quickly

problem Leaky capacitor

$$C = 2 \mu\text{F} \quad Q(0) = Q_0 \quad Q(2\text{s}) = \frac{1}{4} Q_0$$

$$Q = Q_0 e^{-t/RC}$$


$$\frac{1}{4} Q_0 = Q_0 e^{-t/RC}$$

$$\ln \frac{1}{4} = -t/RC$$

$$0 - \ln 2 = -t/RC$$

$$\boxed{R = \frac{t}{C \ln 2}} \quad \frac{2\text{s}}{2 \times 10^{-6} \ln 2} =$$

capacitors in parallel

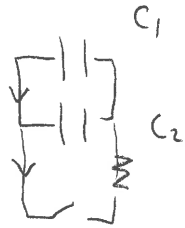

assume these start fully charged

loop 1 $C = C_1 + C_2$

$$Q(t) = Q_0 e^{-t/R(C_1+C_2)}$$

$$Q = Q_1 + Q_2 \quad V = \frac{Q_1}{C_1} = \frac{Q_2}{C_2} \quad Q_2 = \frac{C_2}{C_1} Q_1$$

$$= Q_1 \left(1 + \frac{C_2}{C_1}\right)$$

$$Q_1(t) = \frac{1}{\left(1 + \frac{C_2}{C_1}\right)} Q_0 e^{-t/R(C_1+C_2)} = \frac{Q_0 C_1}{C_1+C_2} e^{-t/R(C_1+C_2)}$$

$$Q_2(t) = \frac{Q_0 C_2}{C_1+C_2} e^{-t/R(C_1+C_2)}$$

$$I_1 = - \frac{Q_0 C_1}{R} e^{-t/R(C_1+C_2)}$$

$$I_2 = \frac{Q_0 C_2}{R} e^{-t/R(C_1+C_2)}$$