

Lecture 17

Why are homes wired in parallel

① resistance of a 100 watt light bulb

$$P = I^2 R = V^2 / R$$

$$R = V^2 / P = (110)^2 / (100) = 121 \Omega$$

② power output of 2 121Ω resistors in parallel

$$R' = \frac{R R}{R + R} = \frac{R}{2}$$

$$P = V^2 / R' = \frac{(110)^2}{121/2} = 200 \text{ Watts}$$


③ power output of 2 121Ω resistors in series

$$R' = R + R = 2R$$

$$P = V^2 / R' = \frac{V^2}{2R} = \frac{1}{2} 100 = 50 \text{ Watts}$$

The combined output of 2 100 Watt light bulbs in series is 50 Watts

charging and discharging capacitors

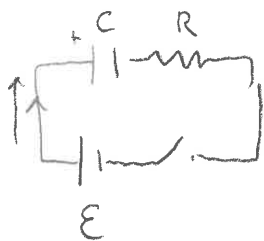

loop equation

$$\boxed{\mathcal{E} - \frac{Q}{C} - IR = 0}$$

note $I = \frac{dQ}{dt}$

using this in the loop equation gives

$$\boxed{\varepsilon - \frac{Q}{C} - R \frac{dQ}{dt} = 0}$$

To solve this we need to specify the initial conditions.

* Assume that the capacitor is uncharged at time $t=0$

* We use the differential equation to find $Q(t)$ at later times

To solve the equation write it in the form:

$$\frac{dQ}{dt} = \frac{1}{R} (\varepsilon - \frac{Q}{C}) = -\frac{1}{R} (\frac{Q}{C} - \varepsilon)$$

we write this as

$$\frac{dQ}{\frac{Q}{C} - \varepsilon} = -\frac{dt}{R}$$

multiply by C

$$\frac{dQ}{Q - \varepsilon C} = -\frac{dt}{RC}$$

To incorporate the initial condition
integrate

$$\int_{Q(0)}^{Q(t)} \frac{dQ}{Q - EC} = - \int_0^t \frac{dt}{RC}$$

let $u = Q - EC \quad du = dQ$

$$u(t) = Q(t) - EC$$

$$u(0) = Q(0) - EC$$

$$\int_{Q(0) - EC}^{Q(t) - EC} \frac{du}{u} = - \frac{t}{RC} = \ln(Q(t) - EC) - \ln(Q(0) - EC)$$

use $\ln a - \ln b = \ln a/b$

$$- \frac{t}{RC} = \ln \left(\frac{Q(t) - EC}{Q(0) - EC} \right) = \ln \left(\frac{EC - Q(t)}{EC - Q(0)} \right)$$

taking exp

$$e^{-t/RC} = \frac{EC - Q(t)}{EC - Q(0)}$$

$$Q(t) = EC - (EC - Q(0)) e^{-t/RC}$$

If we set $Q(0) = 0$ this becomes

$$Q(t) = EC(1 - e^{-t/RC})$$

This has the right properties

① when $t=0$ $Q(0)=0$

② as t gets very large $Q(t)$ approaches $EC = VC$, which is the charge on a capacitor with a voltage E .

③ RC has units of seconds. - It is called the time constant of the RC circuit

④ Large t be $t \gg \tau$.

How long does it take for a capacitor to reach 99% of its full charge.

$$Q(t) = EC(1 - e^{-t/RC})$$

$$Q(t) = 0.99 EC$$

$$0.99 EC = EC - EC e^{-t/RC}$$

$$e^{-t/RC} = 0.01$$

Taking \ln s

$$-\frac{t}{RC} = \ln 0.01$$

$$t = -RC \ln\left(\frac{1}{100}\right) = RC \ln 100$$

$$= \tau \ln 100$$

$$= 4.6 \tau$$

If we have an expression for $Q(t)$ we can use it to find the current

$$Q(t) = EC(1 - e^{-t/RC})$$

$$I(t) = \frac{dQ}{dt} = 0 - E(e^{-t/RC}(-\frac{1}{RC}))$$

$$I(t) = \frac{E}{R} e^{-t/RC}$$

here $\frac{E}{R}$ is the steady state current through a resistor with resistance R . At $t=0$ the current is at this maximum value. When t gets large it heads toward 0 as the charge on the capacitor builds up.

The same ideas can be used to treat the discharge of a capacitor. In this case there is no emf in the circuit

$$0 = -IR - \frac{Q}{C}$$

which becomes

$$- \frac{dQ}{dt} R - \frac{Q}{C} = 0$$

$$\frac{dQ}{dt} = - \frac{Q}{RC}$$

This becomes

$$\frac{dQ}{Q} = - \frac{dt}{RC}$$

In this case at time 0 we assume that the capacitor is fully charged with charge Q

$$\int_Q^{Q(t)} \frac{dQ}{Q} = - \frac{1}{RC} \int_0^t dt$$

Integrating

$$\ln Q(t) - \ln Q = - \frac{t}{RC}$$

$$\frac{Q(t)}{Q(0)} = e^{-t/RC}$$

$$Q(t) = Q(0) e^{-t/RC}$$

In this case the time constant is the same as in the case of charging.


The time to loose half the charge is

$$\frac{1}{2} Q = Q e^{-t/RC}$$

$$\ln\left(\frac{1}{2}\right) = - \ln 2 = - t/RC$$


$$t = RC \ln 2 = \tau \ln 2 = .69 \tau$$

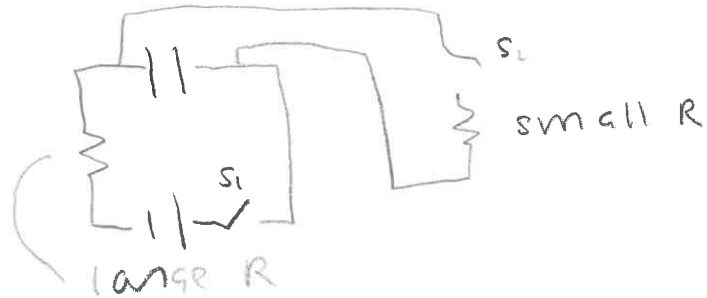making R or C larger increases the time constant - it increases the charge time and discharge time



S_1 closed S_2 open - slow charge
 S_2 closed S_1 open - fast discharge

example

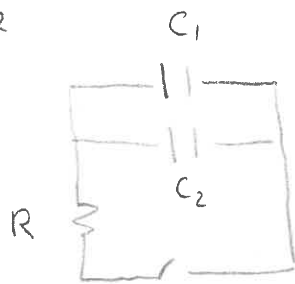

In this case the effective capacitance is

$$C' = C_1 + C_2$$

charging

$$Q(t) = \epsilon C' (1 - e^{-t/\tau RC})$$

We can figure out the charge on each capacitor

$$\frac{Q_1}{C_1} = V = \frac{Q_2}{C_2}$$

$$Q = Q_1 + Q_2 = Q_1 + \frac{C_2}{C_1} Q_1 = \left(1 + \frac{C_2}{C_1}\right) Q_1$$

$$= \left(\frac{C_1 + C_2}{C_1}\right) Q_1$$

$$Q_1 = \frac{C_1}{C_1 + C_2} \cdot Q =$$

$$= \frac{C_1}{C_1 + C_2} \varepsilon C' (1 - e^{-t/RC'})$$

$$= \frac{C_1}{C_1 + C_2} \varepsilon (C_1 + C_2) (1 - e^{-t/RC'})$$

$$= \varepsilon C_1 (1 - e^{-t/RC'})$$

similarly

$$Q_2 = \varepsilon C_2 (1 - e^{-t/RC'})$$

We can also find the current in each capacitor

$$I_1 = \frac{dQ_1}{dt} = \frac{\varepsilon}{R} \left(\frac{C_2}{C_1}\right) e^{-t/RC'} = \frac{\varepsilon}{R} \frac{C_2}{C_1 + C_2} e^{-t/RC'}$$

$$I_2 = \frac{dQ_2}{dt} = \frac{\varepsilon}{R} \frac{C_1}{C_1} e^{-t/RC'} = \frac{\varepsilon}{R} \frac{C_1}{C_1 + C_2} e^{-t/RC'}$$

Leaky capacitor

$$C = 2 \mu\text{F} \quad Q(2) = \frac{1}{4} Q(0) \quad \text{Find } R \quad t = 2$$

$$Q(2) = \frac{1}{4} Q(0) = Q(0) e^{-2/RC}$$

$$-\ln 4 = -\frac{2}{RC}$$

$$\boxed{R = \frac{2}{C \ln 4}}$$

There is another kind of force on charge particles that occurs when moving electric charges pass by a magnet.

so far no one has observed magnetic charges, so for this reason it is useful to start with the definition of the magnetic field

recall $\vec{E} = \lim_{q \rightarrow 0} \frac{\vec{F}}{q}$

for magnetic forces on a charged particle

- (1) the force is proportional to the speed of the particle
- (2) the force is perpendicular to the velocity
- (3) the force is proportional to the charge

It turns out observations are consistent with

$$\boxed{\vec{F}_m = q \vec{v} \times \vec{B}}$$

This force is called the Lorentz force - the direction of \vec{F} and \vec{v} is consistent with a magnetic field vector $\vec{B}(x,t)$

$$\vec{F} = q \vec{v} \times \vec{B}$$

$$\begin{aligned} \vec{v} \times \vec{F} &= q \vec{v} \times (\vec{v} \times \vec{B}) \\ &= q (\vec{v} (\vec{v} \cdot \vec{B}) - \vec{B} (v^2)) \end{aligned}$$

$$\vec{B} = q \vec{v} (\vec{v} \cdot \vec{B}) - \frac{1}{q} (\vec{v} \times \vec{F})$$

This is maximized when $\vec{v} \perp \vec{B}$

In terms of magnitude

$$|\vec{F}| = |q| |\vec{v} \times \vec{B}| = |q| v B \sin \theta$$

where θ is the angle between \vec{B} and \vec{v} and the direction is given by the right hand rule

Remarks

- ① The Lorentz force does no work because \vec{F} is \perp to $\vec{v} = d\vec{x}/dt$
- ② The Lorentz force vanishes when the particle is at rest

The unit of magnetic field is s

$$1 \text{ Tesla} = \frac{\text{Newton sec}}{\text{Coulomb, meter}}$$

Like the electric field, there is a magnetic field vector at every point in space.

Where do magnetic fields come from


- (1) electric currents can cause magnetic fields
- (2) there are also permanent magnets that create magnetic fields
- (3) the earth has a magnetic field

Motion of a charged particle moving with constant velocity \vec{v}

$$\vec{F} = q \vec{v} \times \vec{B}$$

assume \vec{B} has a component \perp to \vec{v} , then $|\vec{F}| = q|\vec{v}||\vec{B}| \sin \theta$

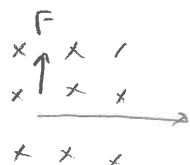which is the angle between \vec{B} and \vec{v}



(x = into plane of paper)

consider first $\vec{v} \perp \vec{B}$

Then there is a force \perp to \vec{v} . This does no work. It causes the particle to move in a circle

$$\frac{mv^2}{r} = qvB$$

$$r = \frac{mv^2}{qvB} = \frac{m}{q} \left(\frac{v}{B} \right)$$

If the velocity also has a component parallel to \vec{B} , there is no magnetic force in this direction.

When this is combined with the circular motion, the motion is helical



if we know the component of $\vec{v} \perp \vec{B}$ we can measure the charge to mass ratio by measuring r, v_{\perp}, B . This is a standard way to measure the mass of an electron.

measuring mass of electron


$$qE = qvB$$

$$v = \frac{E}{B}$$

$$\frac{1}{2}mv^2 = qE'L = qV$$

$$\frac{q}{m} = \frac{v^2}{2V} = \frac{1}{2V} \left(\frac{E^2}{B^2} \right)$$

Hall effect

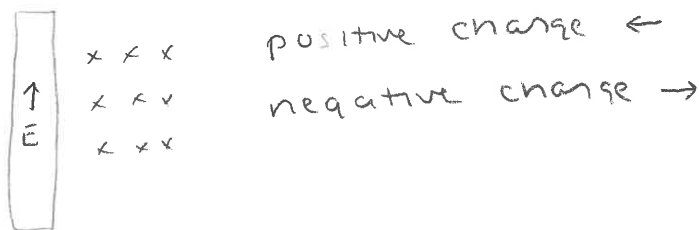

↳ gives a potential on either side of conductor. Depending on the sign of the potential - we can determine the sign of the charge carrier.

We can use an electric field to cancel the \perp component of the motion

$$E = \frac{V}{d} \quad qE = q\frac{V}{d} = qvB$$

where v is the drift velocity on electron

$$I = JA = nev_d A$$

$$n = \frac{I}{ev_d A} = \frac{I}{eA} \cdot \frac{B}{E} = \frac{IB}{e(dA)E} = \frac{IB}{eVd}$$

