

Lecture 26

Exam

Average = 102/170

St. Dev = 35

- 1a) $P = IV \rightarrow I = \frac{P}{V} = \frac{100 \text{ W}}{100 \text{ V}} = 1 \text{ A}$
- 1b) $R = V/I \rightarrow R = \frac{100 \text{ V}}{1 \text{ A}} = 100 \Omega$
- 1c) $R_T = 10R = 1000 \Omega$
- 1d) $I = V/R = 100 \text{ V} / 1000 \Omega = .1 \text{ A}$
- 1e) $P = IV = (.1 \text{ A})(100 \text{ V}) = 10 \text{ Watts}$

2a) $C_T = \frac{(C_1 + C_2)C_3}{C_1 + C_2 + C_3} = \frac{2}{3}C = \frac{4}{3} \times 10^6 \text{ F}$

2b) $Q = CV = \frac{4}{3} \times 10^6 \times 12 = 16 \times 10^6 \text{ C} = 1.6 \times 10^5 \text{ C}$

2c) $V = \frac{Q}{2C} = \left(\frac{4}{3} \times 10^6 \times 12\right) (2 \times 2 \times 10^6)^{-1} = \frac{12}{3} \text{ V} = 4 \text{ V}$

2d) $\text{energy} = \frac{1}{2} CV^2 = \frac{1}{2} \times (2 \times 10^6) (12 - 4)^2 = 64 \times 10^6 \text{ J} = 6.4 \times 10^5 \text{ J}$

3a) Amperes Law + Superposition

$$\vec{B} = \frac{\mu_0 I}{2\pi d} \left(\frac{1}{4} + \frac{1}{3} + \frac{1}{2}\right) \hat{y} = \frac{\mu_0 I}{2\pi d} \cdot \frac{13}{12} \hat{y}$$

3b) $\vec{0}$ fields are equal and opposite

3c) $\vec{F}/e = I \frac{\mu_0 I}{2\pi d} \left(\frac{1}{4} + \frac{1}{2}\right) (-\hat{x}) = -\frac{\mu_0 I^2}{\pi d} \left(\frac{3}{4}\right)$

3d) $\vec{F} = I d \vec{x} \times \vec{B} = 0$ for $I = 0$

4a) $Q(t) = Q(0)e^{-t/RC}$ $Q(0) = CV = (1 \times 10^6) \times (12) \text{ C}$

$$\frac{1}{e} = e^{-t/RC} \Rightarrow -\ln e = -1 = \ln e^{-t/RC} = -t/RC$$

$$R = \frac{t}{C} = \frac{1}{1 \times 10^{-6}} = 10^5 \Omega$$

4b) $Q(t) = CV e^{-10t} = (12 \times 10^6) e^{-10t} \text{ C}$

4c) $I(t) = \frac{dQ}{dt} = \frac{V}{R} e^{-10t} = \frac{12}{10^5} e^{-10t} = 1.2 \times 10^{-4} e^{-10t}$

4d) $P = I^2(t)R = \frac{V^2}{R} e^{-20t} = 144 \times 10^5 e^{-20t} \text{ WATTS}$

Faraday's Law


$$\Phi = \int \vec{B} \cdot \hat{n} dA$$

$$\frac{d\Phi}{dt} = -EMF = - \oint \vec{E} \cdot d\vec{l} \quad \frac{\partial \vec{B}}{\partial t} = -\vec{\nabla} \times \vec{E}$$

change in flux creates a field that creates a current that opposes the change in magnetic flux.

consider a solenoid with n turns of wire per unit length

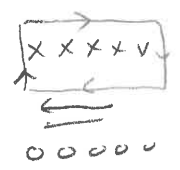the magnetic field inside the solenoid can be computed using ampere's law



$$|\vec{B}|l = \mu_0 I n l \rightarrow B = \mu_0 I n$$

the total flux in length l is

$$\Phi = \pi R^2 n l B$$

$$\Phi = \pi R^2 l \cdot \mu \cdot n^2 I$$

In this case we see that the magnetic flux in this solenoid is proportional to the current

We write this as

$$\Phi = LI$$

or

$$L = \frac{\Phi}{I}$$

The quantity L is called the inductance of the solenoid. For our ideal solenoid

$$L = \pi R^2 \mu_0 n^2 \quad (\text{ideal solenoid})$$

which are all geometric factors

If we differentiate Φ with respect to time we get the relation

$$\frac{d\Phi}{dt} = -\mathcal{E} = L \frac{dI}{dt}$$

or

$$\mathcal{E} = -L \frac{dI}{dt}$$


The MKS unit of inductance is

$$1 \text{ HENRY} = \frac{1 \text{ Tesla Meter}^2}{\text{coulomb}} \cdot \text{second}$$

Inductors are circuit elements like capacitors, the notation is



The loop equation

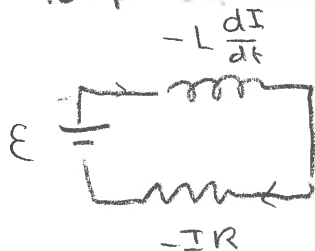

To analyze this loop

$$-L \frac{dI}{dt} - IR + \epsilon = 0$$

$$\boxed{\frac{dI}{dt} = \frac{1}{L} (\epsilon - IR)}$$

this is another differential equation
(for an RL circuit)

To solve this

$$\frac{\frac{dI}{dt}}{IR - \mathcal{E}} = -\frac{1}{L}$$

multiply both sides by R

$$\frac{\frac{dI}{dt}}{I - \mathcal{E}/R} = -\frac{R}{L}$$

or
$$\frac{dI}{I - \mathcal{E}/R} = -\frac{R}{L} dt$$

integrating both sides using

$$u = I - \mathcal{E}/R$$

$$du = dI$$

$$\int_{I(0) - \mathcal{E}/R}^{I(t) - \mathcal{E}/R} \frac{du}{u} = -\frac{R}{L}(t - 0)$$

$$\ln\left(\frac{I(t) - \mathcal{E}/R}{I(0) - \mathcal{E}/R}\right) = -\frac{Rt}{L} = \ln\left(\frac{\mathcal{E}/R - I(t)}{\mathcal{E}/R - I(0)}\right)$$

taking exponential

$$(\mathcal{E}/R - I(t)) = (\mathcal{E}/R - I(0)) e^{-Rt/L}$$

$$I(t) = \frac{\mathcal{E}}{R} - \left(\frac{\mathcal{E}}{R} - I(0)\right) e^{-Rt/L}$$

$$I(t) = \frac{\mathcal{E}}{R} (1 - e^{-Rt/L}) + I(0) e^{-Rt/L}$$

If the initial current is 0 then

$$I(t) = \frac{\mathcal{E}}{R} (1 - e^{-Rt/L})$$

In this case as t increases $I(t) \rightarrow \frac{\mathcal{E}}{R}$ which is what you expect from Ohm's law, but it does not reach this state immediately. - if R is small or L is large it takes more time to reach a steady state

If the battery is removed then

$$I(t) = I(0) e^{-Rt/L}$$

If $I(0)$ is \mathcal{E}/R (Ohm's law current) then

$$I(t) = \frac{\mathcal{E}}{R} e^{-tR/L}$$

The power given off is

$$\begin{aligned} P &= I^2 R \\ &= \frac{\mathcal{E}^2}{R} e^{-2tR/L} \end{aligned}$$

Integrating this from $0 \rightarrow \infty$ gives the energy initially stored in the inductor.

$$\text{energy} = \int_0^{\infty} \frac{\mathcal{E}^2}{R} e^{-\frac{2Rt}{L}} dt$$

$$\text{Let } u = \frac{2Rt}{L} \quad du = \frac{2R}{L} dt \quad dt = \frac{L}{2R} du$$

$$= \int_0^{\infty} \frac{\mathcal{E}^2}{R} \left(\frac{L}{2R}\right) e^{-u} du$$

$$= \frac{1}{2} \left(\frac{\mathcal{E}}{R}\right)^2 L (-e^{-\infty} - (-e^{-0}))$$

$$\boxed{\text{energy} = \frac{1}{2} I^2 L}$$

since $I = \frac{\Phi}{L}$ this becomes

$$\text{energy} = \frac{1}{2} \Phi^2 \frac{1}{L}$$

for our solenoid

$$= \frac{1}{2} \frac{(B n l A)^2}{A \mu_0 n^2} = \frac{1}{2\mu_0} B^2 A l$$

$$= \frac{1}{2\mu_0} B^2 \times \text{volume}$$

this suggests that like the electric field - energy is stored in the magnetic field with energy / volume given by

$$\boxed{\frac{\text{magnetic energy}}{\text{volume}} = \frac{B^2}{2\mu_0}}$$

Mutual inductance

consider 2 current loops



The current in Loop 1 creates a magnetic flux in loop 2
 the flux in Loop 2 is proportional to the current in loop 1. This gives

$$\Phi_2 = M_{21} I_1$$

similarly

$$\Phi_1 = M_{12} I_2$$

If we differentiate both sides with respect to t

$$\begin{aligned} \mathcal{E}_2 &= - \frac{d\Phi_2}{dt} = -M_{21} \frac{dI_1}{dt} \\ \mathcal{E}_1 &= - \frac{d\Phi_1}{dt} = -M_{12} \frac{dI_2}{dt} \end{aligned}$$

The quantity M_{12} and M_{21} are actually the same

example :



To treat this circuit we use conservation of charge and energy again

$$I_1 = I_2 + I_3$$

$$\varepsilon - I_1 R_1 - I_2 R_2 = 0$$

$$\varepsilon - I_1 R_1 - L \frac{dI_3}{dt}$$

first eliminate I_2

$$I_2 = I_1 - I_3$$

$$\varepsilon - I_1 R_1 - (I_1 - I_3) R_2$$

eliminate I_1

$$I_1 (R_1 + R_2) = \varepsilon + I_3 R_2$$

$$I_1 = \frac{\varepsilon + I_3 R_2}{R_1 + R_2}$$

last equation

$$\left| \varepsilon - R_1 \left(\frac{\varepsilon + I_3 R_2}{R_1 + R_2} \right) - L \frac{dI_3}{dt} = 0 \right.$$

This gives a simple differential equation for I_3

$$\frac{dI_3}{dt} = \underbrace{\frac{1}{L} \left(\mathcal{E} - \frac{R_1}{R_1+R_2} \mathcal{E} \right)}_A - \underbrace{\frac{R_1 R_2}{L(R_1+R_2)}}_B I_3$$

$$\frac{dI_3}{dt} = A - B I_3$$

$$\frac{dI_3}{B I_3 - A} = -dt \quad \text{mut by } B$$

$$\frac{dI_3}{I_3 - A/B} = -B dt$$

$$u = I_3 - A/B \quad du = dI_3$$

$$\int_{I_3(0) - A/B}^{I_3(t) - A/B} \frac{du}{u} = -B \int_0^t dt$$

$$\ln \left(\frac{A/B - I_3(t)}{A/B - I_3(0)} \right) = -Bt$$

$$(A/B - I_3(t)) = (A/B - I_3(0)) e^{-Bt}$$

$$I_3(t) = A/B (1 - e^{-Bt}) + I_3(0) e^{-Bt}$$

$$A = \frac{\mathcal{E}}{L} \frac{R_2}{R_1+R_2} \quad B = \frac{R_1 R_2}{L(R_1+R_2)}$$

$$I_1(t) = \frac{\mathcal{E} + I_3(t) R_2}{(R_1+R_2)}$$

$$I_2(t) = \frac{\mathcal{E}}{R_1+R_2} + I_3(t) \left(\frac{R_2}{R_1+R_2} - 1 \right)$$

$$= \frac{\mathcal{E}}{R_1+R_2} - \frac{R_1}{R_1+R_2} I_3$$

Inductors in parallel and series

$$\mathcal{E} = -L \frac{dI}{dt}$$

2 inductors in series

$$\left. \begin{array}{l} L_1 \frac{dI}{dt} = -V_1 \\ L_2 \frac{dI}{dt} = -V_2 \end{array} \right\} \begin{array}{l} V = V_1 + V_2 = -(L_1 \frac{dI}{dt} + L_2 \frac{dI}{dt}) \\ = -(L_1 + L_2) \frac{dI}{dt} \end{array}$$

In this case the effective inductance

is

$$\boxed{L = L_1 + L_2 \quad \text{inductors in series}}$$

2 inductors in parallel



$$V = L \frac{dI}{dt} = L_1 \frac{dI_1}{dt} = L_2 \frac{dI_2}{dt}$$


$$\frac{V}{L} = \frac{dI}{dt} = \frac{dI_1}{dt} + \frac{dI_2}{dt} = \frac{V}{L_1} + \frac{V}{L_2}$$

since \$V\$ is the same

$$\text{or } \boxed{\begin{array}{l} \frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2} \\ L = \frac{L_1 L_2}{L_1 + L_2} \end{array} \quad \text{inductors in parallel}}$$

So far we have discussed RC and RL circuits. We can also consider LC and RLC circuits as well.

Case of an LC circuit

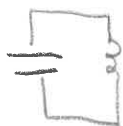

The energy conservation equation gives

$$0 = -\frac{Q}{C} - L \frac{dI}{dt}$$

We note $I = \frac{dQ}{dt}$ $\frac{dI}{dt} = \frac{d^2Q}{dt^2}$ so

we can write this equation as

$$\boxed{L \frac{d^2Q}{dt^2} = -\frac{Q}{C}}$$

This should look familiar

$$m \frac{d^2x}{dt^2} = -kx$$

which is the equation for a particle of mass m attached to a spring

These equations have the same form if we replace

$$m \rightarrow L$$

$$k \rightarrow \frac{1}{C}$$

$$x \rightarrow Q$$

If we write this as

$$\frac{d^2 Q}{dt^2} = -\frac{1}{LC} Q$$

We know from mechanics that the general solution has the form

$$Q(t) = Q(0) \cos\left(\frac{t}{\sqrt{LC}}\right) + I(0) \sqrt{LC} \sin\left(\frac{t}{\sqrt{LC}}\right)$$

where $Q(0)$ is the initial charge and $I(0)$ is the initial current.

$$I(t) = \frac{dQ}{dt} = -Q(0) \frac{1}{\sqrt{LC}} \sin\left(\frac{t}{\sqrt{LC}}\right) + I(0) \cos\left(\frac{t}{\sqrt{LC}}\right)$$

If at $t=0$ the capacitor is initially charged and the initial current is 0 then

$$Q(t) = Q(0) \cos\left(\frac{t}{\sqrt{LC}}\right)$$

$$I(t) = -\frac{Q(0)}{\sqrt{LC}} \sin\left(\frac{t}{\sqrt{LC}}\right)$$

In the absence of any dissipation
these continue to oscillate with
angular frequency

$$\omega = \frac{1}{\sqrt{LC}} = 2\pi f$$

and period

$$T = \frac{1}{f} = 2\pi\sqrt{LC}$$

Alternative treatment
complex numbers

$$i = \sqrt{-1}$$

$$Z = X + iY$$

$$\begin{aligned} Z_1 Z_2 &= (X_1 + iY_1)(X_2 + iY_2) \\ &= (X_1 X_2 - Y_1 Y_2) + i(X_1 Y_2 + Y_1 X_2) \end{aligned}$$

consider

$$e^{ia}$$

$$\frac{d}{dt} e^{iat} = ia e^{iat}$$

$$\frac{d^2}{dt^2} e^{iat} = (ia)^2 e^{iat} = -a^2 e^{iat}$$

we note

$$\cos at \quad \text{and} \quad \sin at$$

satisfy the same equation.

these are independent solutions so we must have

$$\cos ax = \alpha e^{iax} + \beta e^{-iax}$$

$$\sin ax = \gamma e^{iax} + \delta e^{-iax}$$

for $x=0$

$$1 = \alpha + \beta$$

$$0 = \gamma + \delta$$

differentiating

$$-a \sin ax = i a \alpha e^{iax} - i a \beta e^{-iax}$$

$$a \cos ax = i \gamma a e^{iax} - i \delta a e^{-iax}$$

setting $x=0$

$$0 = \alpha - \beta$$

$$1 = i(\gamma - \delta)$$

this gives $\alpha = \beta = \frac{1}{2}$ $\delta = -\gamma = -\frac{1}{2i}$

$$\cos ax = \frac{1}{2} (e^{iax} + e^{-iax})$$

$$\sin ax = \frac{1}{2i} (e^{iax} - e^{-iax})$$

We can also invert these to get

$$e^{iax} = \cos ax + i \sin ax$$

$$e^{-iax} = \cos ax - i \sin ax$$