

Lecture 28

Last time

LRC circuits

$$-L \frac{dI}{dt} - RI - \frac{Q}{C} = 0$$

use

$$I(t) = \frac{dQ}{dt}, \quad \frac{dI}{dt} = \frac{d^2Q}{dt^2}$$

$$-L \frac{d^2Q}{dt^2} - R \frac{dQ}{dt} - \frac{Q}{C} = 0$$

We looked for solutions of the general form e^{at} where a could be a complex number, using this solution in the equation gave

$$\left(-La^2 - Ra - \frac{1}{C}\right)e^{at} = 0$$

this will vanish for all time if a is a root of the quadratic equation.

$$La^2 + Ra + \frac{1}{C} = 0$$

using the quadratic formula gives

$$\alpha = \frac{-R \pm \sqrt{R^2 - 4 \frac{L}{C}}}{2L}$$

$$= -\frac{R}{2L} \left(1 \pm \sqrt{1 - 4 \frac{L}{R^2 C}} \right) = \alpha_{\pm}$$

This gives 2 independent solutions

$$Q(t) = Q_+ e^{\alpha_+ t} + Q_- e^{\alpha_- t}$$

$$I(t) = Q_+ \alpha_+ e^{\alpha_+ t} + Q_- \alpha_- e^{\alpha_- t}$$

We can express both of these solutions in terms of the initial charge on the capacitor and current through the resistor

$$Q(0) = Q_+ + Q_-$$

$$I(0) = Q_+ \alpha_+ + Q_- \alpha_-$$

using

$$Q_- = Q(0) - Q_+$$

$$I(0) = Q_+ \alpha_+ + (Q(0) - Q_+) \alpha_-$$

$$= Q_+ (\alpha_+ - \alpha_-) + \alpha_- Q(0)$$

$$Q_+ = \frac{I(0) - \alpha_- Q(0)}{\alpha_+ - \alpha_-}$$

$$Q_- = Q(0) - \frac{I(0) - \alpha_- Q(0)}{\alpha_+ - \alpha_-}$$

$$= \frac{Q(0) \alpha_+ - I(0)}{\alpha_+ - \alpha_-}$$

this gives

$$Q(t) = \frac{I(0) - a_- Q(0)}{a_+ - a_-} e^{a_+ t} + \frac{Q(0) a_+ - I(0)}{a_+ - a_-} e^{a_- t}$$
$$I(t) = \frac{I(0) - a_- Q(0)}{a_+ - a_-} a_+ e^{a_+ t} + \frac{Q(0) a_+ - I(0)}{a_+ - a_-} a_- e^{a_- t}$$

where

$$a_{\pm} = -\frac{R}{2L} \left(1 \pm \sqrt{1 - \frac{4L}{R^2 C}} \right)$$

As mentioned earlier - there are three types of time dependence, depending on

(1) $0 < 1 - \frac{4L}{R^2 C} < 1$

(2) $\frac{4L}{R^2 C} > 1$

(3) $\frac{4L}{R^2 C} = 1$

In case 1 the quantity in the square root is positive so

a_{\pm} are both negative real numbers

this means both $Q(t)$ and $I(t)$ go smoothly to 0 without any oscillations

case 2 $\frac{4L}{R^2C} > 1$ then

$$a_{\pm} = -\frac{R}{2L} \left(1 \pm i \sqrt{\frac{4L}{R^2C} - 1} \right)$$

in this case the solutions have the form

$$e^{-\frac{R}{2L} \mp i \sqrt{\frac{4L}{R^2C} - 1} t}$$

$$e^{-\frac{R}{2L} \left(\cos\left(\sqrt{\frac{4L}{R^2C} - 1} t\right) \mp i \sin\left(\sqrt{\frac{4L}{R^2C} - 1} t\right) \right)}$$

this has the form of a decaying exponential multiplied by an oscillating amplitude with angular frequency $\omega = \sqrt{\frac{4L}{R^2C} - 1}$

In this case we could also write the general solution as

$$\begin{aligned} & e^{-\frac{R}{2L} t} \left(A \cos\left(\sqrt{\frac{4L}{R^2C} - 1} t\right) + B \sin\left(\sqrt{\frac{4L}{R^2C} - 1} t\right) \right) \\ & = e^{-\frac{R}{2L} t} \left(C \cos\left(\sqrt{\frac{4L}{R^2C} - 1} t + \phi\right) \right) \end{aligned}$$

in all case either Q_+ & Q_- , A, B or C, ϕ can be chosen to get the correct initial charge and current.

these can we related using

$$\cos(\omega t + \phi) = \cos(\omega t) \cos(\phi) - \sin(\omega t) \sin(\phi)$$

the third case is more interesting

In that case $I = \frac{4L}{R^2 C}$ $a = e^{-\frac{R}{2L}t}$

the independent solutions are

$$e^{-\frac{R}{2L}t} \quad t e^{-\frac{R}{2L}t}$$

To check this for $e^{-\frac{R}{2L}t}$

$$L \left(\frac{R^2}{4L^2} \right) + R \left(-\frac{R}{2L} \right) + \frac{1}{C} = 0 \Rightarrow$$

$$\frac{R^2}{4C} = 1$$

for $t e^{-\frac{R}{2L}t}$

$$\frac{d}{dt}: -\frac{R}{2L} t e^{-\frac{R}{2L}t} + e^{-\frac{R}{2L}t}$$

$$\frac{d^2}{dt^2}: -\frac{R}{2L} e^{-\frac{R}{2L}t} + \frac{R^2}{4L^2} t e^{-\frac{R}{2L}t} - \frac{R}{2L} e^{-\frac{R}{2L}t}$$

$$\left[L \left(-\frac{R}{2L} + \frac{R^2 t}{4L^2} - \frac{R}{2L} t \right) + R \left(-\frac{R}{2L} t + 1 \right) + \frac{t}{C} \right] e^{-\frac{R}{2L}t}$$

$$\left[\underbrace{\left(-\frac{R}{2} - \frac{R}{2} + R \right)}_0 + t \underbrace{\left(\frac{R^2}{4L} - \frac{R^2}{2L} + \frac{1}{C} \right)}_0 \right] e^{-\frac{R}{2L}t}$$

so in the third case there are still two smoothly decaying solutions

$$Q(t) = e^{-\frac{R}{2L}t} (a + bt)$$

$$I(t) = -\frac{R}{2L} e^{-\frac{R}{2L}t} (a + bt) + b e^{-\frac{R}{2L}t}$$

at $t=0$ $Q(0) = a$

$$I(0) = -\frac{R}{2L} Q(0) + b$$

$$b = I(0) + \frac{R}{2L} Q(0)$$

$$Q(t) = e^{-\frac{R}{2L}t} \left(Q(0) + \left(I(0) + \frac{R}{2L} Q(0) \right) t \right)$$

$$I(t) = e^{-\frac{R}{2L}t} \left(-\frac{R}{2L} Q(0) + \left(I(0) + \frac{R}{2L} Q(0) \right) \left(1 - \frac{R}{2L} t \right) \right)$$

It is easy to check that these have the correct initial conditions.

These equations are analogous to the equations for a harmonic oscillator in a viscous fluid - where R represents the viscosity.

AC circuits

AC circuits have an oscillating EMF


We use the symbol

$$\textcircled{\sim} = \mathcal{E}_0 \cos(\omega t)$$

$$\mathcal{E}_0 \sin(\omega t)$$

$$\mathcal{E}_0 e^{i\omega t}$$

These are all possible - consider

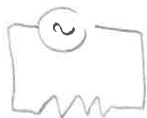

$$\mathcal{E} - IR = 0$$

In this case

$$IR = \mathcal{E}_0 e^{i\omega t}$$


$$I = \frac{\mathcal{E}_0}{R} e^{i\omega t}$$

$$(e^{i\omega t} = \cos \omega t + i \sin \omega t)$$

the real or imaginary of this is

$$I_r = \frac{\mathcal{E}_0}{R} \cos(\omega t)$$
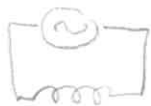
$$I_i = \frac{\mathcal{E}_0}{R} \sin(\omega t)$$



$$\mathcal{E} - L \frac{dI}{dt}$$

$$L \frac{dI}{dt} = \mathcal{E}_0 e^{i\omega t}$$

$$\frac{dI}{dt} = \frac{\mathcal{E}_0}{L} e^{i\omega t}$$

Integrating

$$\int \frac{dI}{dt} = \int \frac{\mathcal{E}_0}{L} e^{i\omega t} dt$$

$$I(t) - I(0) = \frac{1}{i\omega} \frac{\mathcal{E}_0}{L} e^{i\omega t} - \frac{1}{i\omega} \frac{\mathcal{E}_0}{L}$$

note $i^{-1} = e^{-i\frac{\pi}{2}}$

$$I(t) - I(0) = \frac{\mathcal{E}_0}{L\omega} \left(e^{i(\omega t - \frac{\pi}{2})} - e^{-i\frac{\pi}{2}} \right)$$

for the current

$$I(t) = \frac{\mathcal{E}_0}{L\omega} e^{i(\omega t - \frac{\pi}{2})}$$

taking real and imaginary parts

$$I_r(t) = \frac{\mathcal{E}_0}{L\omega} \cos(\omega t - \frac{\pi}{2})$$


$$I_i(t) = \frac{\mathcal{E}_0}{L\omega} \sin(\omega t - \frac{\pi}{2})$$

we define $X_L = L\omega$ called the inductive reactance

$$\boxed{\mathcal{E}(t) = X_L I(t)}$$

where the phase of the current in the inductor is $\frac{\pi}{2}$ behind the phase of the emf

For a capacitor

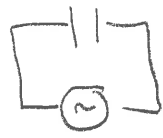

$$\mathcal{E} - \frac{Q}{C} = 0$$

$$\mathcal{E}_0 e^{i\omega t} = \frac{Q}{C}$$

the current in the capacitor

$$\begin{aligned} I_c &= \frac{dQ}{dt} = C \mathcal{E}_0 i\omega e^{i\omega t} \\ &= \mathcal{E}_0 C \omega e^{i(\omega t + \frac{\pi}{2})} \end{aligned}$$

We define the capacitive reactance

$$X_c = \frac{1}{C\omega}$$


and we have

$$\mathcal{E}(t) = I(t) X_c$$

where the phase of the current through the resistor is $\frac{\pi}{2}$ ahead of the phase of the EMF.

$$\begin{aligned} \therefore \mathcal{E}(t) &= I(t) R && \text{in phase} \\ &= I(t) X_c && X_c = \frac{1}{C\omega} \quad +\frac{\pi}{2} \\ &= I(t) X_L && X_L = \omega L \quad -\frac{\pi}{2} \end{aligned}$$

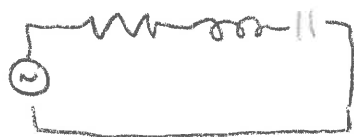Next consider a general driven RLC circuit



$$\mathcal{E} = \mathcal{E}_0 \cos \omega t$$

The energy conservation equation gives

$$-L \frac{dI}{dt} - IR - \frac{Q}{C} + \mathcal{E}_0 \cos \omega t = 0$$

express this in terms of Q

$$I = \frac{dQ}{dt} \quad \frac{dI}{dt} = \frac{d^2Q}{dt^2}$$

$$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q = \frac{\mathcal{E}_0}{2} (e^{i\omega t} + e^{-i\omega t}) \quad (1)$$

let Q_1, Q_2, Q_3 be solutions to

$$L \frac{d^2Q_1}{dt^2} + R \frac{dQ_1}{dt} + \frac{1}{C} Q_1 = 0$$

$$L \frac{d^2Q_2}{dt^2} + R \frac{dQ_2}{dt} + \frac{1}{C} Q_2 = \frac{\mathcal{E}_0}{2} e^{i\omega t}$$

$$L \frac{d^2Q_3}{dt^2} + R \frac{dQ_3}{dt} + \frac{1}{C} Q_3 = \frac{\mathcal{E}_0}{2} e^{-i\omega t}$$

If we define $Q = Q_1 + Q_2 + Q_3$ and add the 3 equations above we get a solution to (1)

the equation for Q_1 we just studied and found that the solutions had the form

$$Q_1(t) = Q_+ e^{a_+ t} + Q_- e^{a_- t}$$

where both eventually decayed to 0.

We can find solutions to Q_2 and Q_3 assuming they have the form $Q_2(t) e^{i\omega t}$ $Q_3(t) e^{-i\omega t}$, using these in the equation give

$$(-L\omega^2 + iR\omega + \frac{1}{C}) Q_2(t) e^{i\omega t} = \frac{\epsilon}{2} e^{i\omega t}$$

$$(-L^2\omega^2 - iR\omega + \frac{1}{C}) Q_3(t) e^{-i\omega t} = \frac{\epsilon}{2} e^{-i\omega t}$$

$$Q_2(t) = \frac{\epsilon}{2} \frac{1}{-L\omega^2 + iR\omega + \frac{1}{C}} e^{i\omega t}$$

$$Q_3(t) = \frac{\epsilon}{2} \frac{1}{-L\omega^2 - iR\omega + \frac{1}{C}} e^{-i\omega t}$$

factoring out $\pm i\omega$ from the denominators

$$Q_2(t) = \frac{\epsilon}{2\omega} \frac{1}{iL\omega + R - \frac{i}{\omega C}} e^{i(\omega t - \frac{\pi}{2})}$$

$$Q_3(t) = \frac{\epsilon}{2\omega} \frac{1}{-iL\omega + R + \frac{i}{\omega C}} e^{-i(\omega t - \frac{\pi}{2})}$$

We can express these in terms of X_L X_C

$$Q_2(t) = \frac{\epsilon}{2\omega} \frac{1}{R+i(X_L-X_C)} e^{i(\omega t - \frac{\pi}{2})}$$

$$Q_3(t) = \frac{\epsilon}{2\omega} \frac{1}{R-i(X_L-X_C)} e^{-i(\omega t - \frac{\pi}{2})}$$

multiply the denominator and numerator
 $R \pm i(X_L - X_C)$

$$Q_2(t) = \frac{\epsilon}{2\omega} \frac{R-i(X_L-X_C)}{R^2+(X_L-X_C)^2} e^{i(\omega t - \frac{\pi}{2})}$$

$$Q_3(t) = \frac{\epsilon}{2\omega} \frac{R+i(X_L-X_C)}{R^2+(X_L-X_C)^2} e^{-i(\omega t - \frac{\pi}{2})}$$

We define the impedance of this circuit

$$Z = \sqrt{R^2 + (X_L - X_C)^2} \frac{R-i(X_L-X_C)}{\sqrt{R^2+(X_L-X_C)^2}} = e^{i\phi}$$

$$Q_2(t) = \frac{\epsilon}{2\omega} \frac{1}{Z} e^{i(\omega t - \frac{\pi}{2} + \phi)}$$

$$Q_3(t) = \frac{\epsilon}{2\omega} \frac{1}{Z} e^{-i(\omega t - \frac{\pi}{2} + \phi)}$$

putting everything together,

$$Q(t) = Q_1(t) + Q_2(t) + Q_3(t) =$$

$$Q_+ e^{a_+ t} + Q_- e^{a_- t} + \frac{\epsilon_0}{\omega Z} \frac{1}{2} e^{i(\omega t - \frac{\pi}{2} + \phi)} - e^{-i(\omega t - \frac{\pi}{2} + \phi)} =$$

$$Q_+ e^{a_+ t} + Q_- e^{a_- t} + \frac{\epsilon_0}{\omega Z} \cos(\omega t - \frac{\pi}{2} + \phi)$$

In this expression Q_+ and Q_- are arbitrary. They can be used to fix $Q(0)$ and $I(0)$.

eventually $e^{a_+ t} e^{a_- t} \rightarrow 0$ for large t and what remains is

$$Q(t) \rightarrow \frac{\epsilon_0}{\omega Z} \frac{1}{2} \left(e^{i(\omega t - \frac{\pi}{2} + \phi)} + e^{-i(\omega t - \frac{\pi}{2} + \phi)} \right)$$

differentiating gives the current

$$I(t) = \frac{dQ}{dt} = -\frac{\epsilon_0}{\omega Z} \frac{1}{2i} \left(e^{i(\omega t - \frac{\pi}{2} + \phi)} - e^{-i(\omega t - \frac{\pi}{2} + \phi)} \right)$$

$$= -\frac{\epsilon_0}{\omega Z} \sin(\omega t - \frac{\pi}{2} + \phi)$$

$$Q(t) = \frac{\epsilon_0}{\omega Z} \cos(\omega t - \frac{\pi}{2} + \phi)$$

note that the denominator will be smallest when

$$X_L = X_C \quad \text{since } Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$L\omega = \frac{1}{\omega C} \quad \omega^2 = \frac{1}{LC}$$

when ω is the natural frequency of the LC circuit. - this means that the current is maximized when $\omega = 1/\sqrt{LC}$