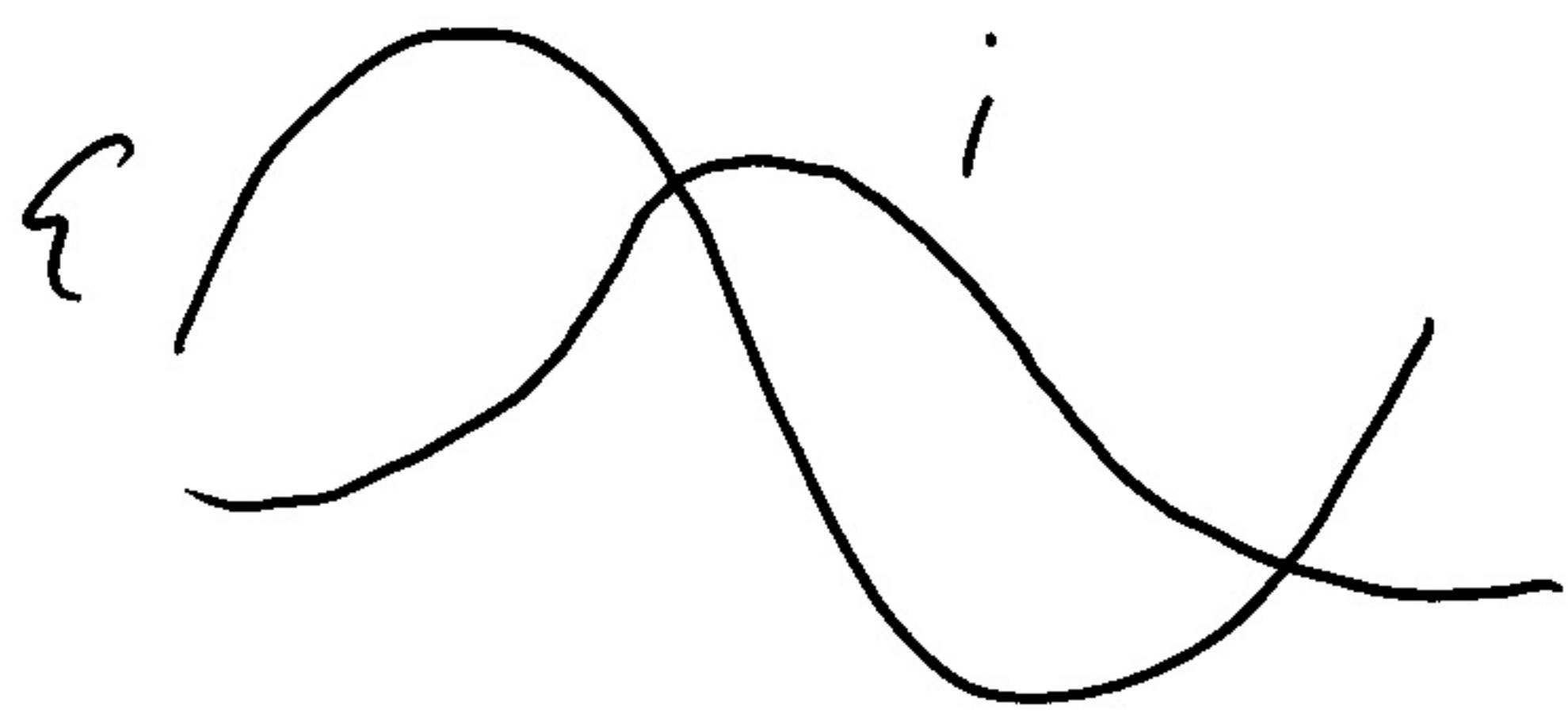


C1:



a. i lags E

so if $E = E_m \sin \omega t$

$$i = E_m \sin(\omega t - \phi)$$


$$\phi > 0$$

b. circuit is inductive

so want to decrease X_L & L


c. want to increase X_C , so
decrease C

C2:

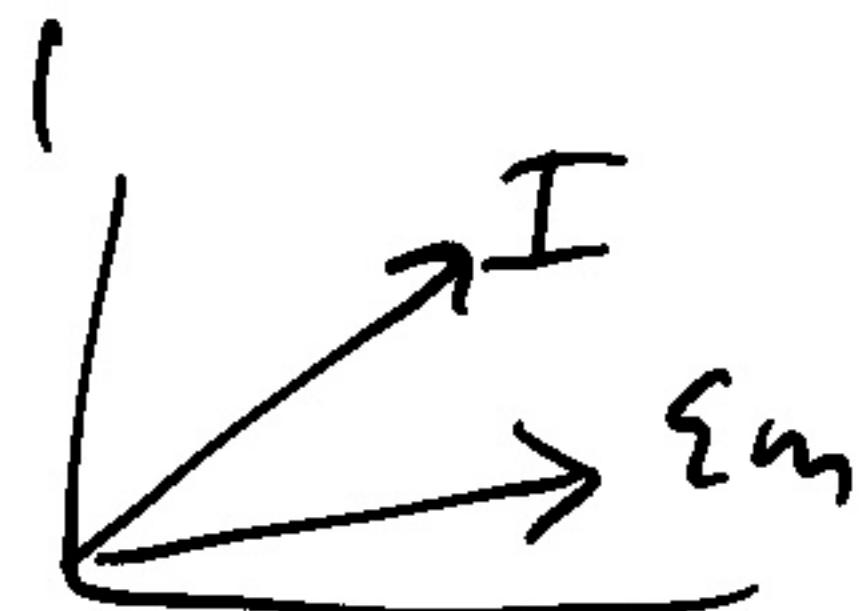


capacitive

$$\omega_d < \omega_r$$

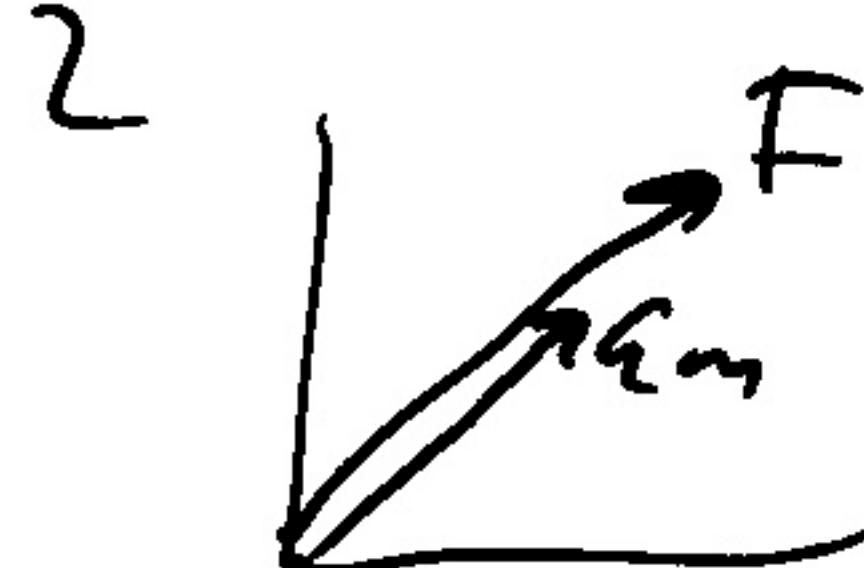

resistive

$$\omega_d = \omega_r$$

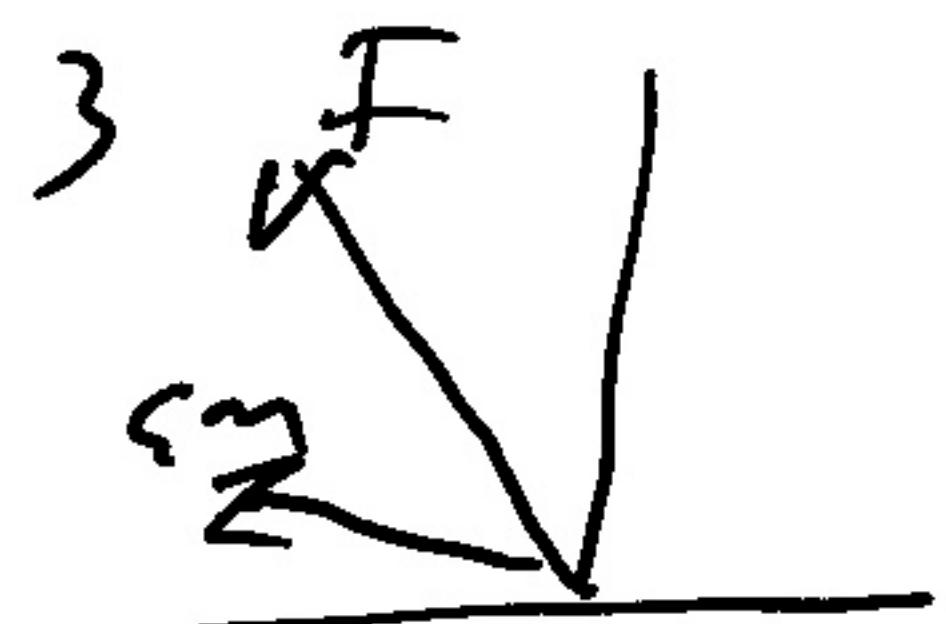

inductive

$$\omega_d > \omega_r$$

C3:




capacitive

- increasing L, C, ω

- all make circuit more inductive

- shift i right & increase amplitude

C4:

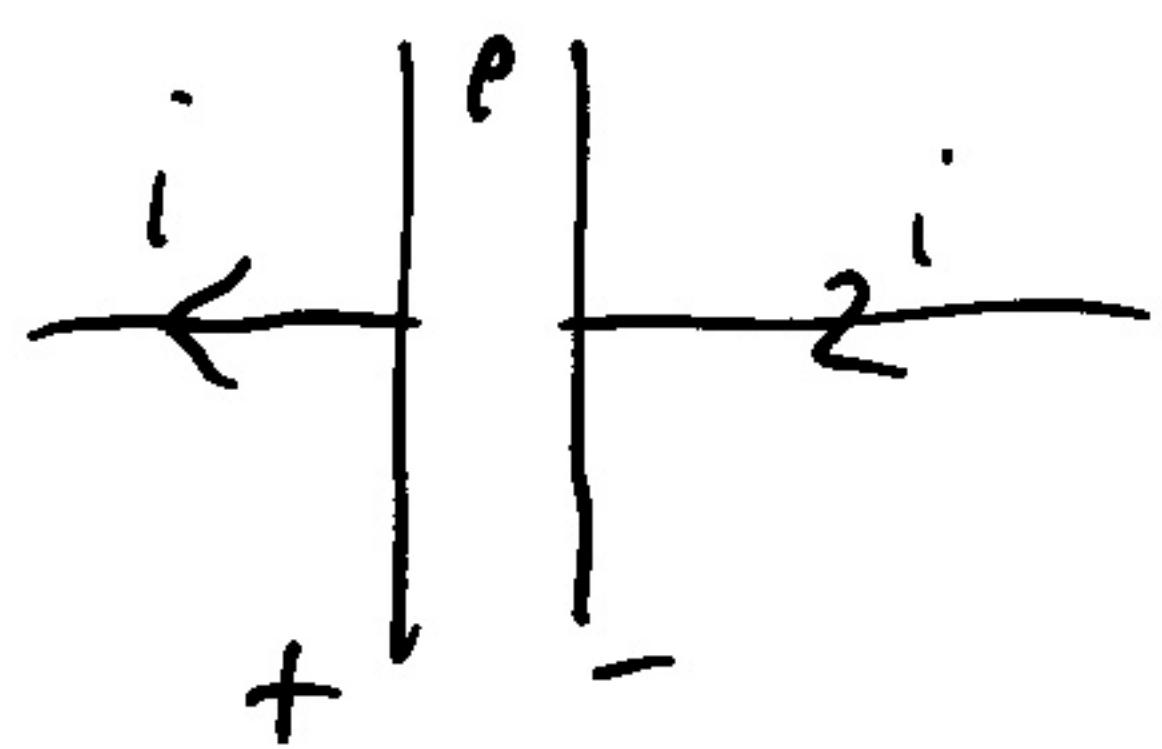

capacitor
discharging

$$E \rightarrow$$

$$i_d \leftarrow$$


$$\beta \oplus p \quad \oplus$$

C5: $\oint \vec{B} \cdot d\vec{l} = \mu_0 \epsilon_0 \frac{d\Phi_E}{dt}$


$$= \mu_0 \epsilon_0 A \frac{dE}{dt}$$

for fixed area

- a. RHR gives dE/dt up,
 $|E|$ decreasing

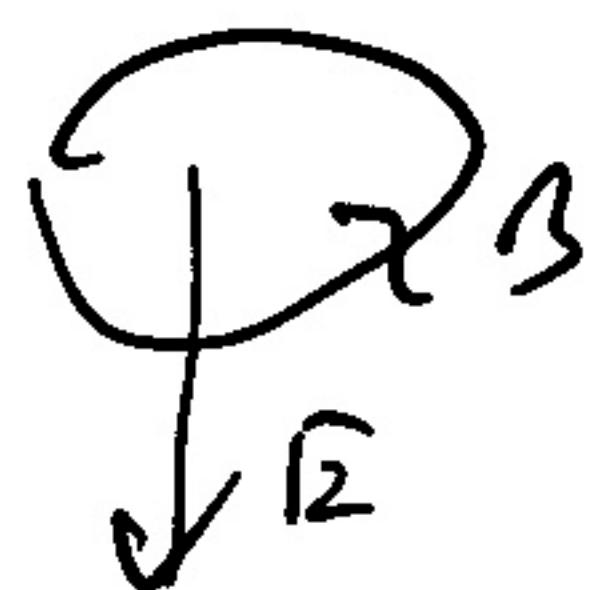

- b. dE/dt down, $|E|$ decreasing

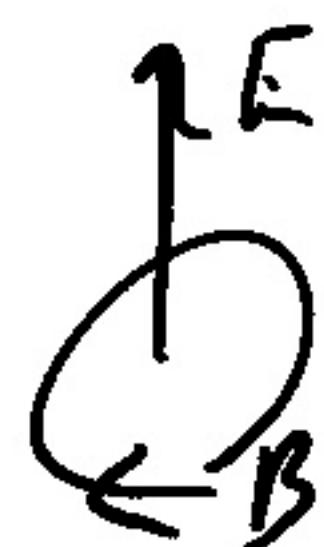

$$M1: \begin{aligned} a. X_C &= Y_{AC} & \omega = 2\pi f \\ b. Z &= \sqrt{R^2 + \sqrt{(L - Y_{AC})^2}} \\ c. I &= E_m / Z \end{aligned}$$

$$M2: \begin{aligned} a. P_S &= q_i \\ &= q_m \sin(\omega t) \cdot E_m / Z \sin(\omega t - \varphi_0) \end{aligned}$$

$$\begin{aligned} b. P_C &= V_C i \\ &= a/c \cdot i \\ &= -Y_{AC} I(0)(\omega t - \varphi_0) \cdot I \sin(\omega t - \varphi_0) \\ &= -E_m^2 / Z^2 \cdot X_C \cdot \cos(\omega t - \varphi_0) \sin(\omega t - \varphi_0) \end{aligned}$$


$$\begin{aligned} c. P_L &= V_L i \\ &= i_L \cdot i / dt \\ &= I \sin(\omega t - \varphi_0) \cdot L \cdot \omega_d \cdot I \cos(\omega t - \varphi_0) \\ &= E_m^2 / Z^2 \cdot X_L \cdot \sin(\omega t - \varphi_0) \cos(\omega t - \varphi_0) \end{aligned}$$

$$\begin{aligned} d. P_R &= i^2 R \\ &= E_m^2 / Z^2 \cdot R \cdot \sin^2(\omega t - \varphi_0) \end{aligned}$$

$$P_S = P_C + P_L + P_R$$

$$M_3: \oint \vec{B} \cdot d\vec{s} = \mu_0 \epsilon_0 \frac{d\phi_E}{dt}$$
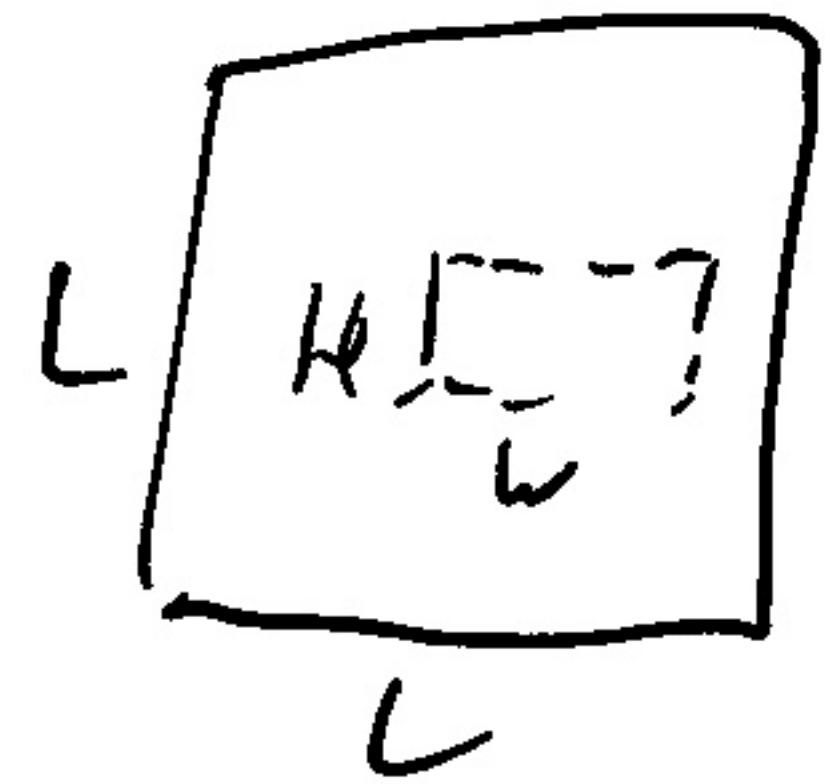
$$\text{idenc} = i \cdot H \cdot w / L^2 = \mu_0 \text{idenc}$$



$$M_4: \oint \vec{B} \cdot d\vec{s} = 0 \cdot 2\pi r \\ = \mu_0 i \text{idenc} \\ = \mu_0 i \cdot \cancel{\pi r^2 / \pi R^2}$$

$$\Rightarrow B = \frac{\mu_0 i r}{2\pi R^2}$$

$$i = E/R e^{-t/\tau_{RC}} \quad \text{w/ } C = \epsilon_0 A/d$$

$$M_5: V = V_0 e^{-t/\tau}$$

$$E = V/d$$

$$q_{0,2} = EA = E \cdot \pi r^2 = \frac{V_0}{d} \cdot \pi r^2 e^{-t/\tau}$$

$$|\frac{d\phi_E}{dt}| = \frac{\pi r^2 V_0}{\tau} e^{-t/\tau}$$

$$|\vec{B}| = \mu_0 \epsilon_0 |\frac{d\phi_E}{dt}| \cdot \frac{1}{2\pi r}$$

$$= \frac{\mu_0 \epsilon_0 r V_0}{2\pi \tau} e^{-t/\tau}$$

Parallel Eqs.

$$\oint \vec{B} \cdot d\vec{l} = \mu_0 \epsilon_0 \frac{d\phi_E}{dt}$$

$$\oint \vec{E} \cdot d\vec{l} = - \frac{d\phi_B}{dt}$$

- why difference in sign?

(-) in Faraday's Law

\Rightarrow changing B produces EMF that drives current that opposes change in B

(+) in Ampere's Law

\Rightarrow changing E produces an effective current that "completes the circuit" and reinforces the change

- If both were (+) or both (-) light waves would not oscillate