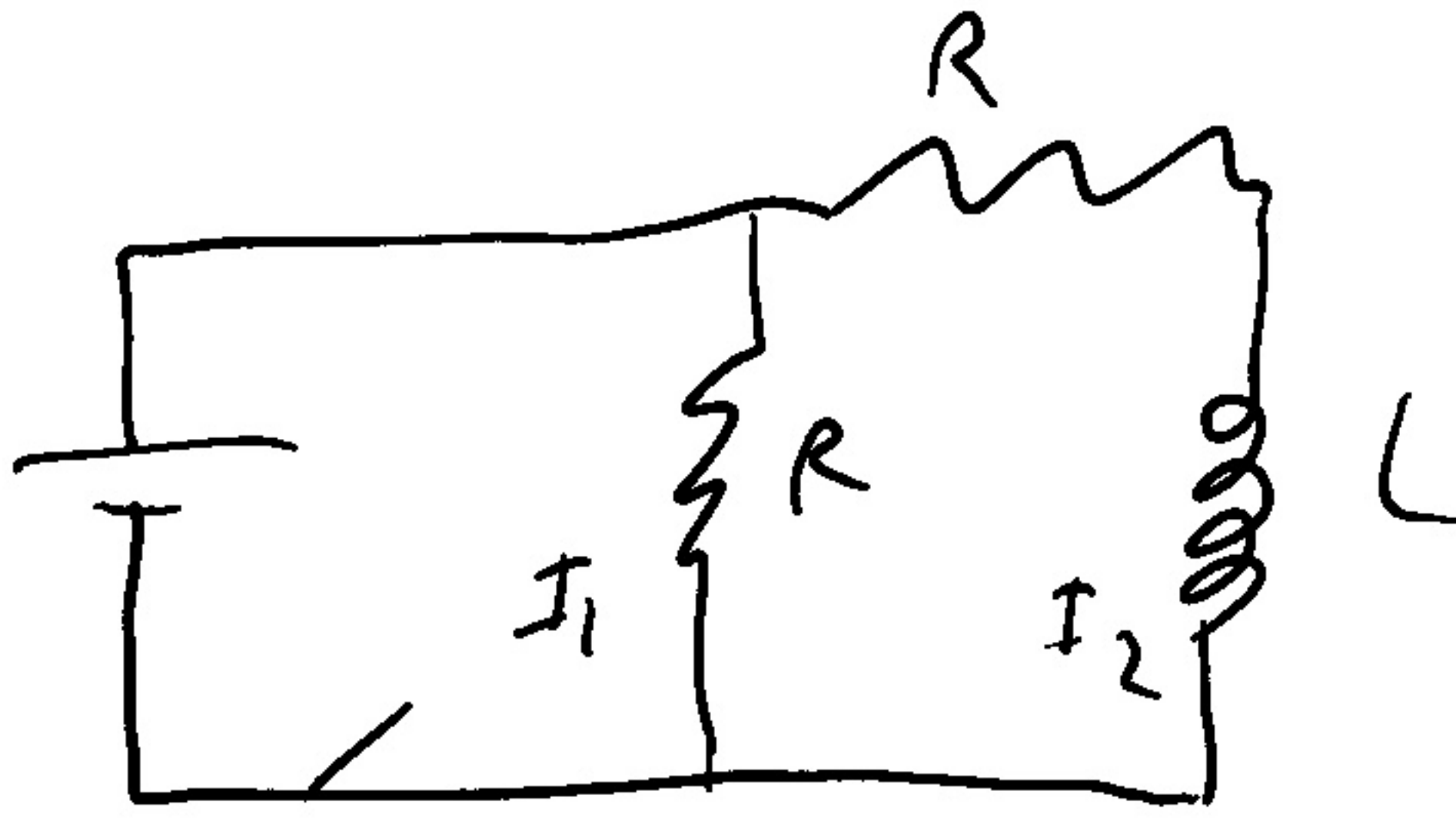


C1:




⑤ $t \sim 0 \quad I_1 \gg I_2$

⑥ $t \sim \infty \quad I_1 = I_2$

after re-opening
much later $I_1 = I_2$
 $I_1 = I_2 = 0$

C2:

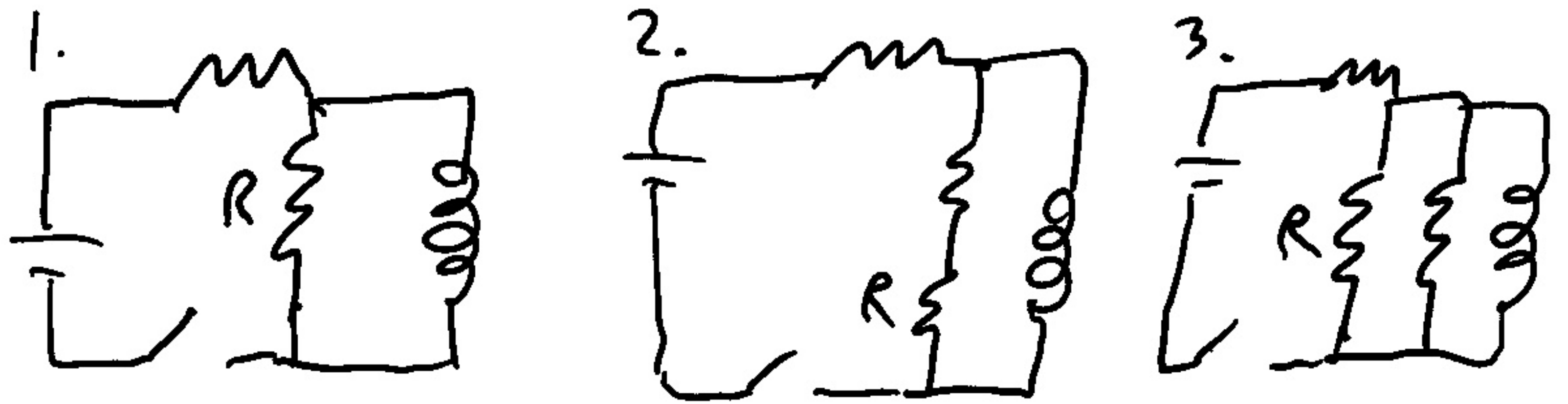


① $t = \infty, I_1 = I_2 = I_3 = 0$


after re-opening $I_1 = I_2 > I_3$

② $t = \infty, I_1 = I_2 = I_3 = 0$

C3: $Q(\omega) = Q_{max}$

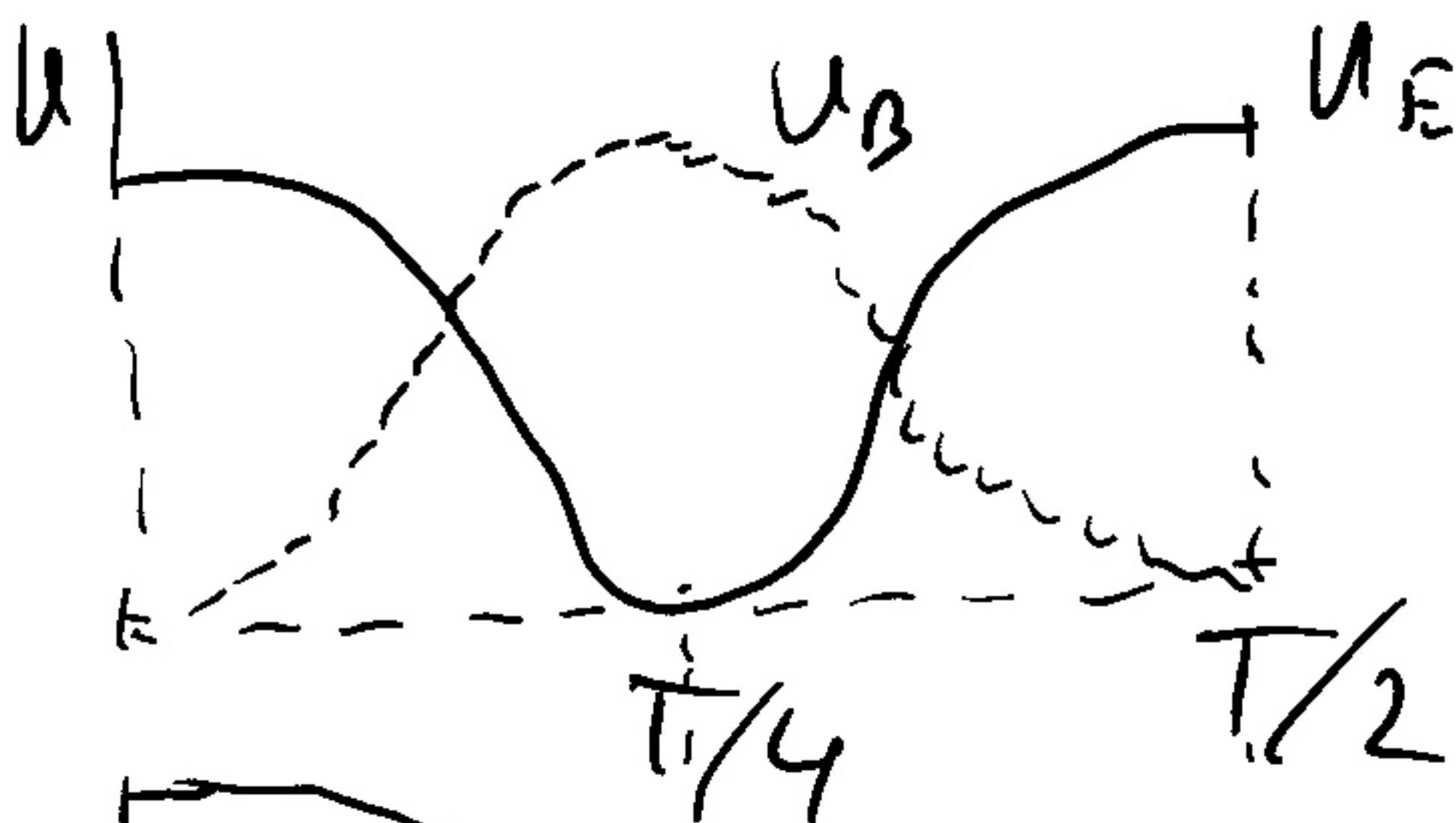

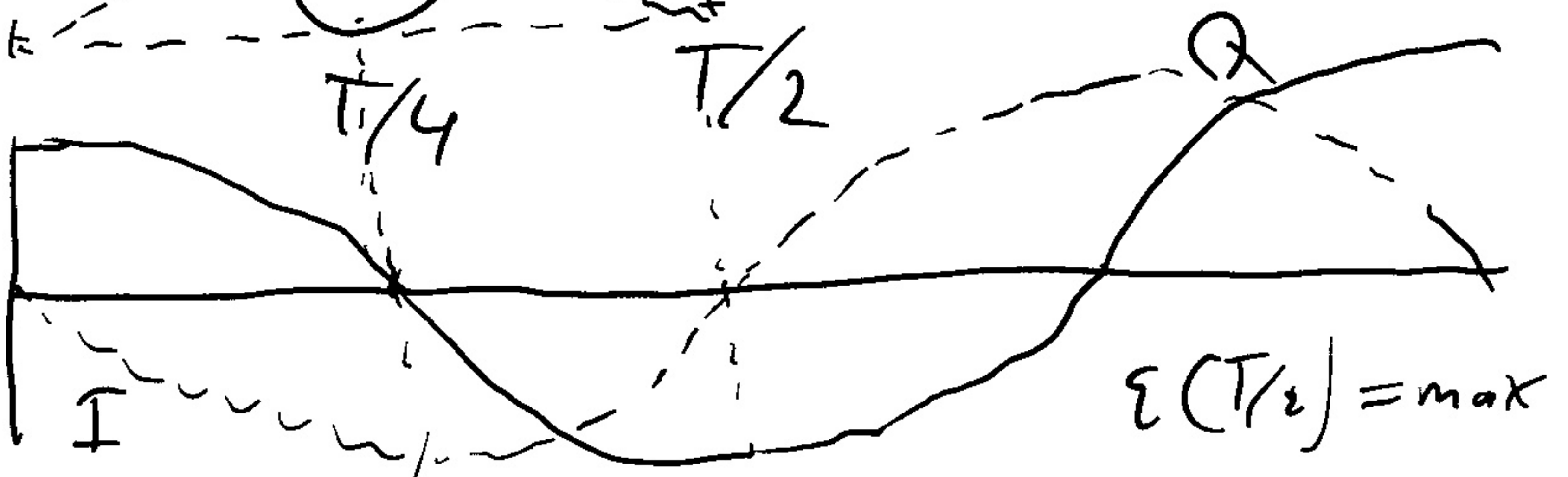$U_B(T/4) = \max$
 $Q \cos(T/4) = \max$
 $di/dt(T/2) = \max$




$Q(T/2) = \max$

CL. $q_1 = 2 \cos(4t)$
 $q_2 = 4 \cos t$
 $q_3 = 3 \cos(4t)$


$i = dq/dt$
 $I_3 > I_1 > I_2$

$T = 2\pi/\omega$
 $T_2 > T_1 = T_3$

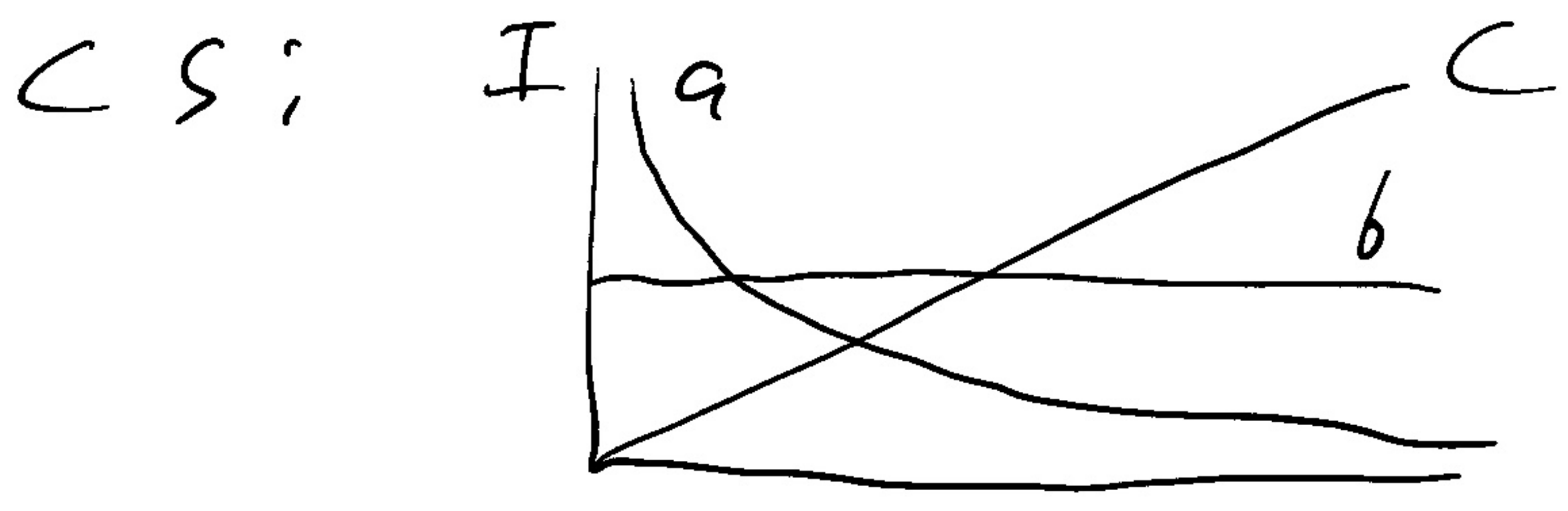

$I = \mathcal{E} / Z$
 $Z_R = R \Rightarrow$
 $Z_C = 1/\omega C$
 $Z_L = \omega L$
 a. L
 b. R
 c. C

M1:

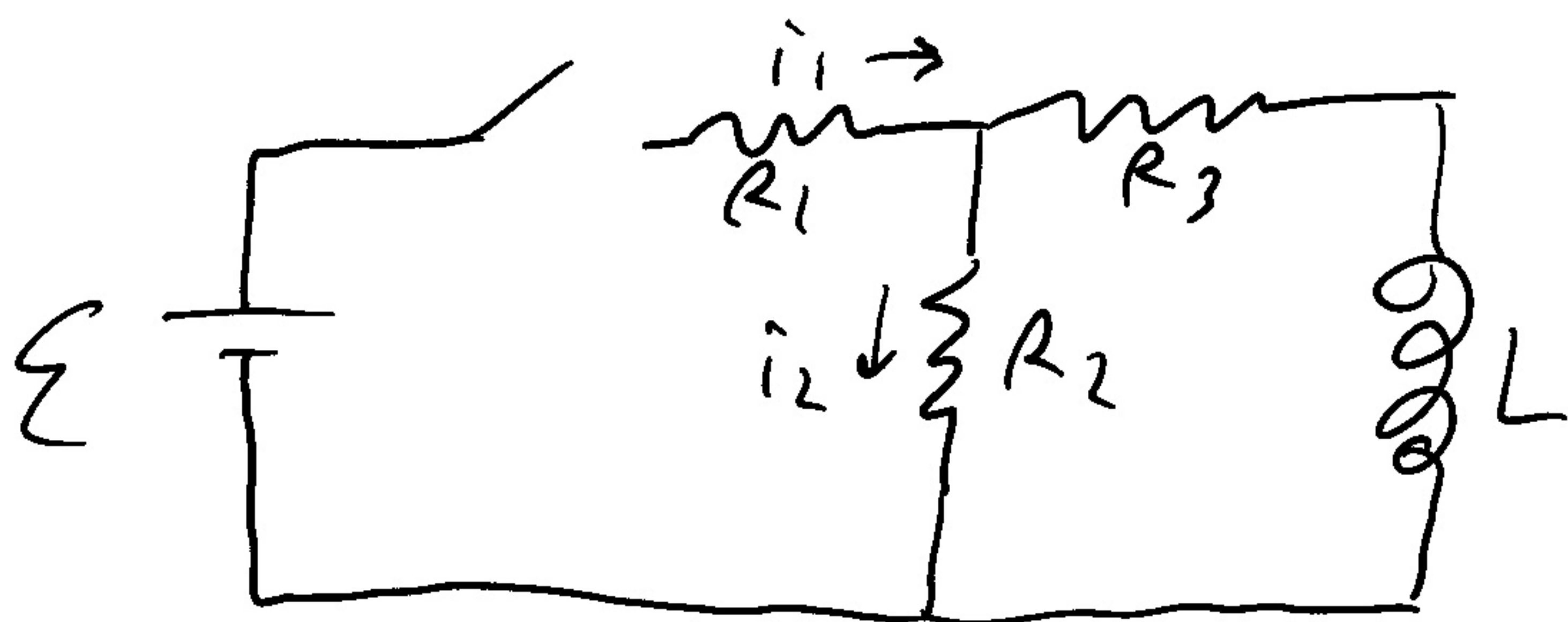

① $t = 0$ no current through L
 $i_1 = i_2 = \mathcal{E} / (R_1 + R_2)$

② $t = \infty$ L is a wire

$$i_1 = \mathcal{E} / \left(R_1 + \frac{R_2 R_3}{R_2 + R_3} \right)$$

$$i_2 = i_1 \cdot \frac{R_2 R_3}{R_2 + R_3} \cdot \frac{1}{R_2} = \frac{\mathcal{E} R_3}{R_1 (R_2 + R_3) + R_2 R_3}$$

after opening switch

$$i_1 = 0$$

$$i_2 = -\mathcal{E} R_2 / (R_1 (R_2 + R_3) + R_2 R_3)$$

long time later

$$i_1 = i_2 = 0$$

$$M2: i = \mathcal{E}/R (1 - e^{-t/\tau_L})$$

$$a. P_{\text{battery}} = \mathcal{E} i \\ = \frac{\mathcal{E}^2}{R} (1 - e^{-t/\tau_L})$$

$$U_{\text{battery}} = \int P dt \\ = \mathcal{E}^2/R t + \mathcal{E}^2 \tau_L / R e^{-t/\tau_L} \Big|_0^6$$


$$= 6 \mathcal{E}^2 / R + \frac{\mathcal{E}^2 L}{R^2} [e^{-6/\tau_L} - 1]$$

$$b. U_{\text{inductor}} = \frac{1}{2} L I^2 \\ = \frac{1}{2} L \cdot \left[\frac{\mathcal{E}}{R} (1 - e^{-t/\tau_L}) \right]^2 \\ = \frac{1}{2} L \cdot \mathcal{E}^2 / R^2 \cdot (1 - 2e^{-6/\tau_L} + e^{-12/\tau_L})$$

$$c. U_{\text{resistor}} = \int i^2 R dt \\ = \int \frac{\mathcal{E}^2}{R} (1 - 2e^{-t/\tau_L} + e^{-2t/\tau_L}) dt \\ = \frac{\mathcal{E}^2}{R} \left(t + 2\tau_L e^{-t/\tau_L} - \frac{\tau_L}{2} e^{-2t/\tau_L} \right) \Big|_0^6 \\ = 6 \mathcal{E}^2 / R + 2 \mathcal{E}^2 L / R^2 (e^{-6/\tau_L} - 1) + \frac{\mathcal{E}^2 L}{2 R^2} (1 - e^{-12/\tau_L})$$

$$U_{\text{bat}} = U_{\text{ind}} + U_{\text{res}}$$

M3:

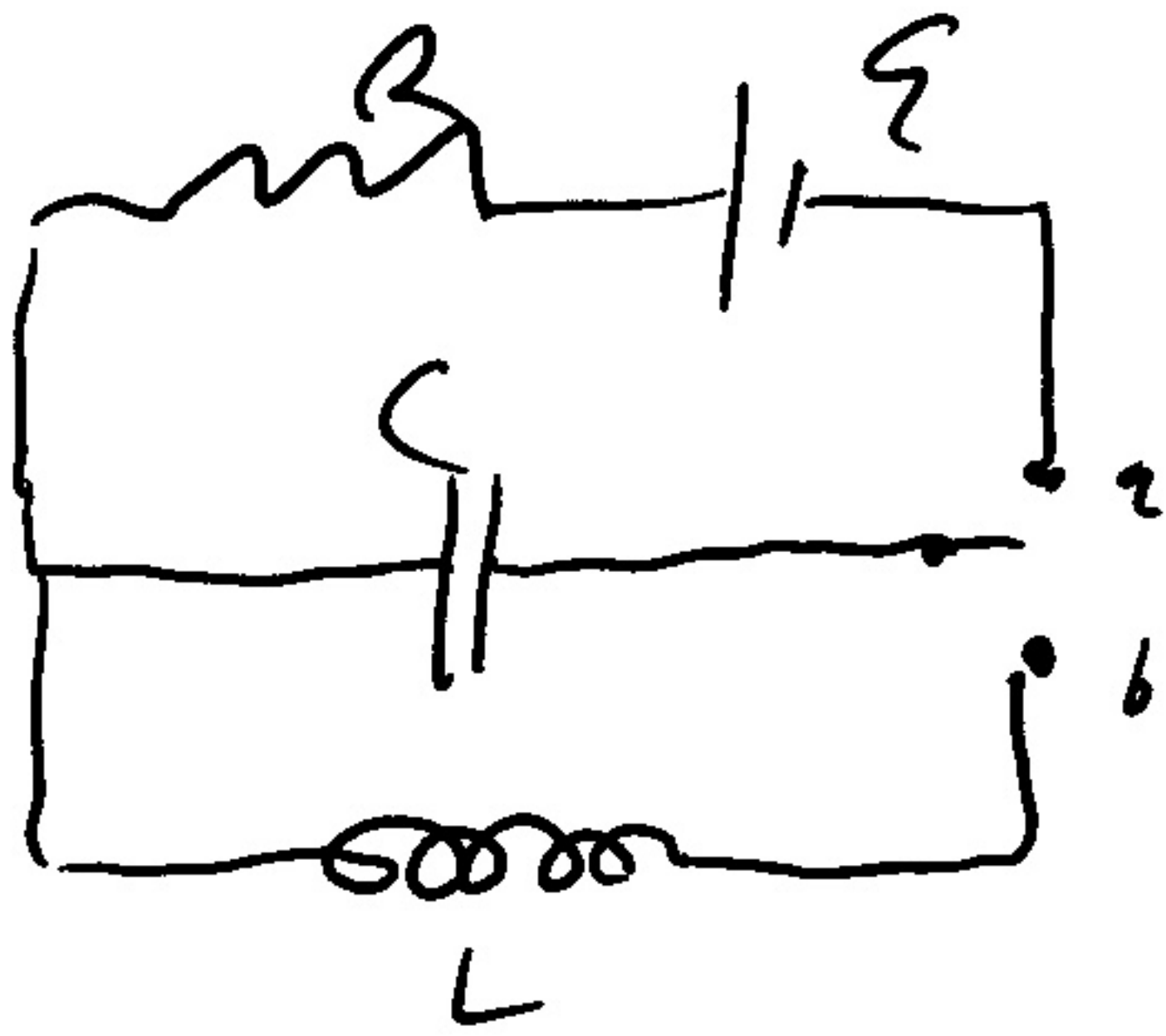


- After long time, $I = 0$
 $Q = C \mathcal{E}$
- Switch from a to b

$$\omega = \frac{1}{\sqrt{LC}} \Rightarrow f = \frac{1}{2\pi\sqrt{LC}}$$

$$U_{0\max} = \frac{1}{2} L I^2 = U_{\mathcal{E}\max} = \frac{Q^2}{2C}$$

$$\begin{aligned} \Rightarrow I_{\max} &= Q_{\max} / \sqrt{LC} \\ &= C \mathcal{E} / \sqrt{LC} \\ &= \mathcal{E} \sqrt{C/L} \end{aligned}$$

M4:

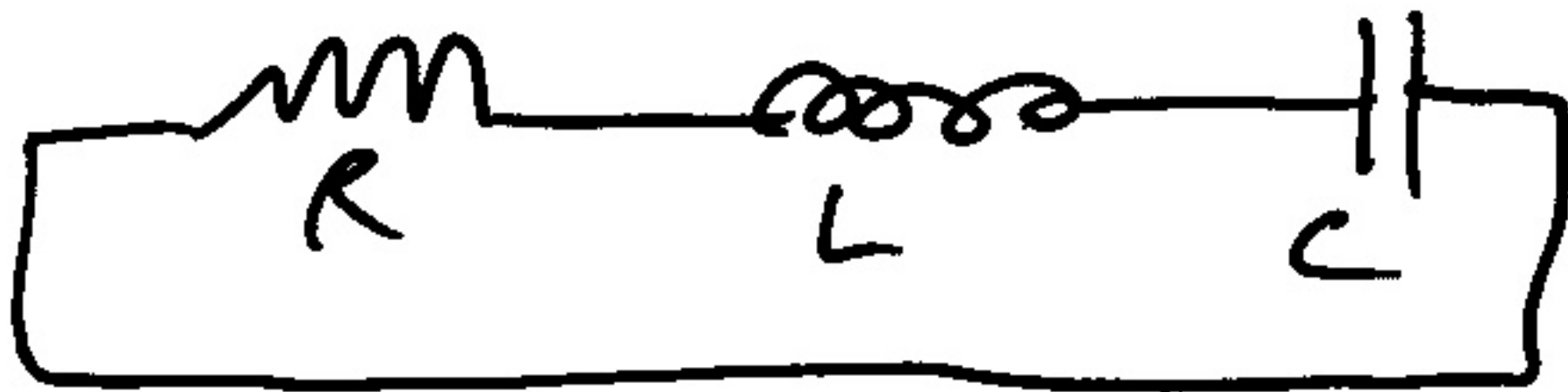

Q/Q_0 after 5, 10, 100 cycles


$$Q/Q_0 = e^{-tR/2L}$$

$$T = \frac{2\pi}{\omega} = 2\pi\sqrt{LC}$$

$$\text{so } Q/Q_0 = e^{-2\pi N \sqrt{LC} R/2L} = e^{-\pi N \sqrt{C/L} R}$$


C/L small so falls slowly

MS:

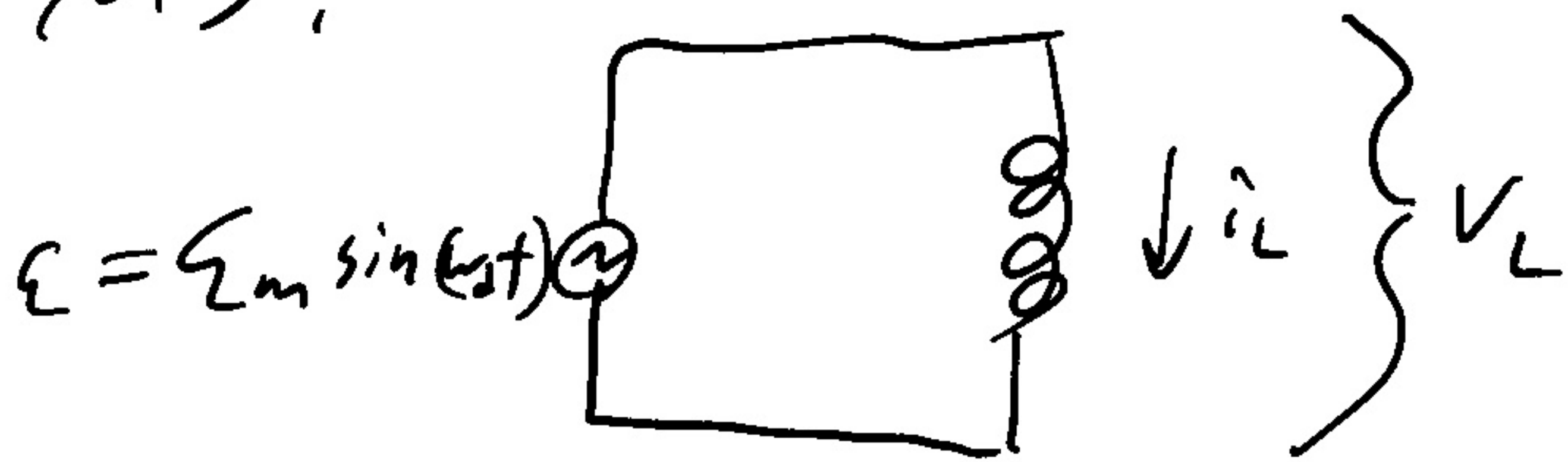

a. $\hat{i}_{\max} = I = \mathcal{E}_m / X_L = \mathcal{E}_m / \omega L$

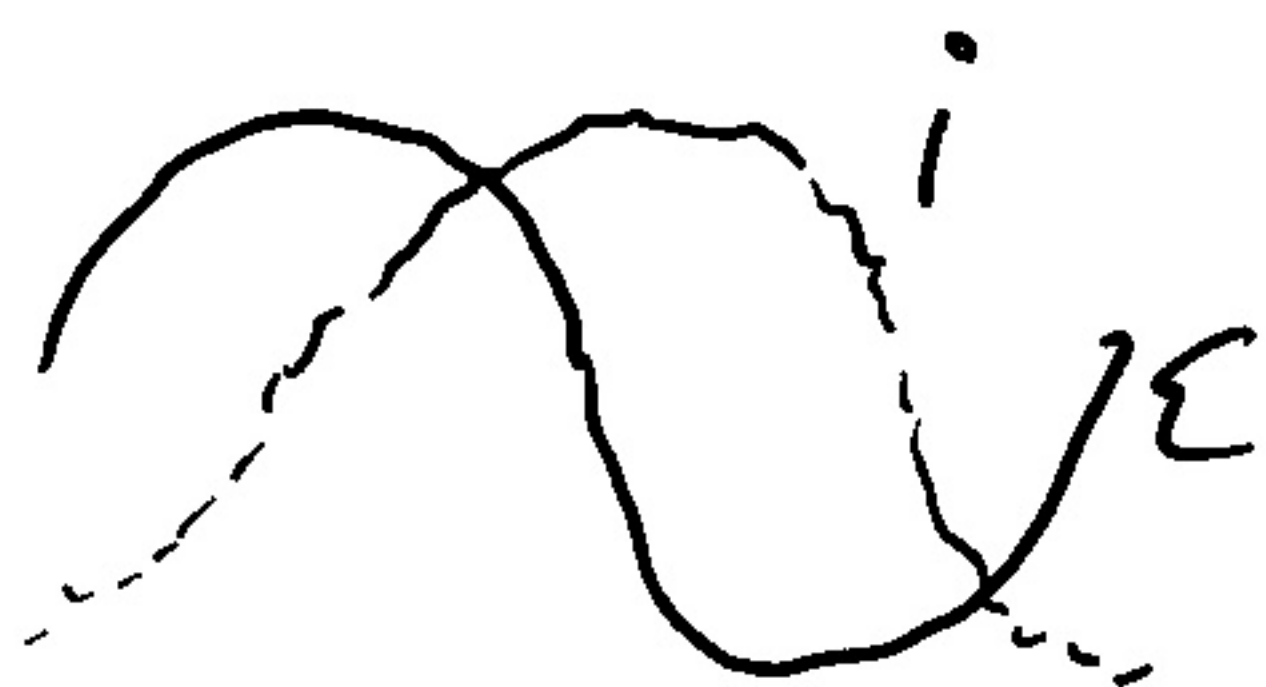b. \mathcal{E} when $\hat{i} = \hat{i}_{\max} = 0$



\mathcal{E} leads i
for inductor

c. $i = -\mathcal{E}_m / X_L \cos(\omega t)$
 $= \mathcal{E}_m / X_L \sin(\omega t - \pi/2)$

solve $\mathcal{E} = \mathcal{E}_m \sin(\omega t)$
for t and plug in