
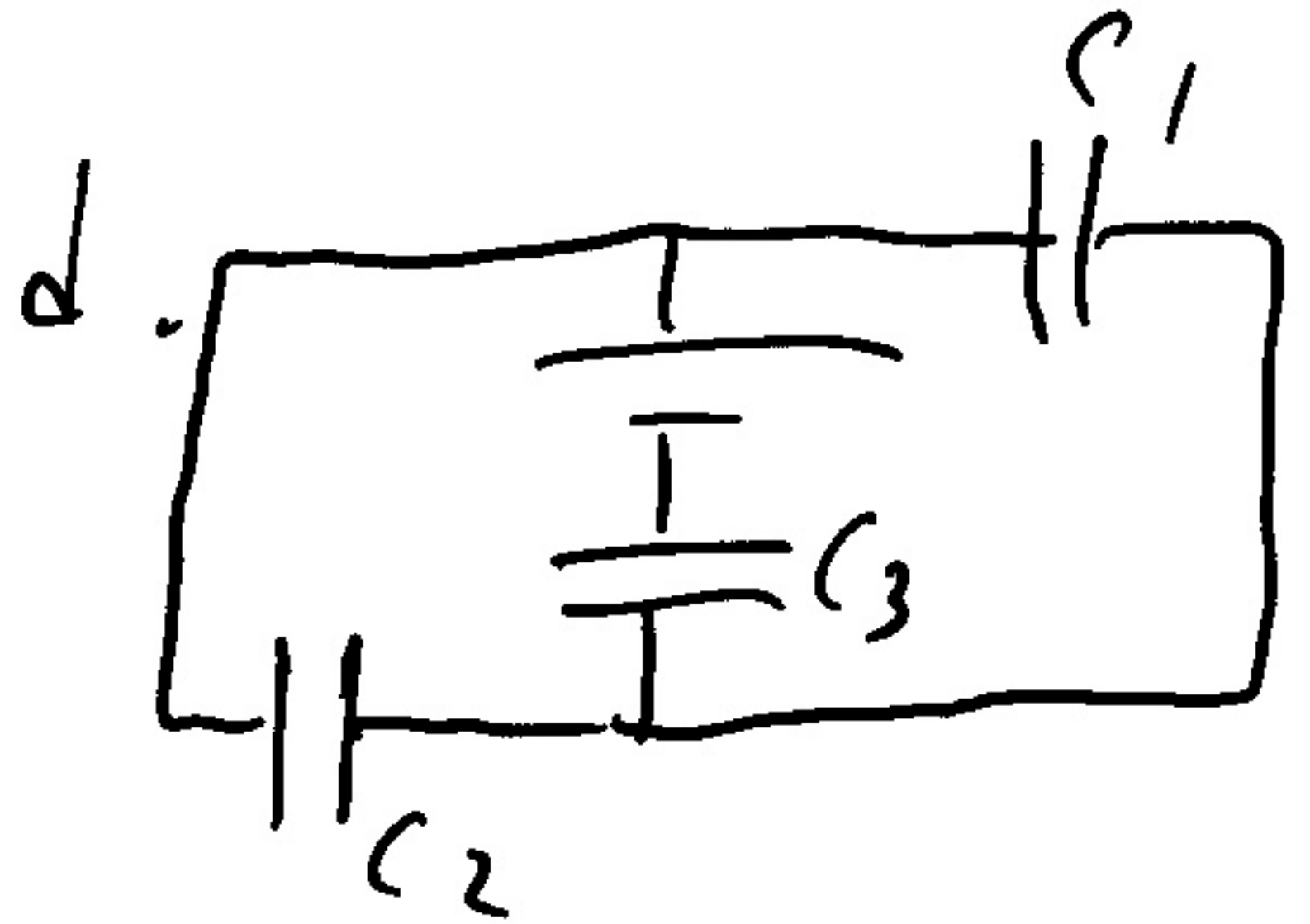
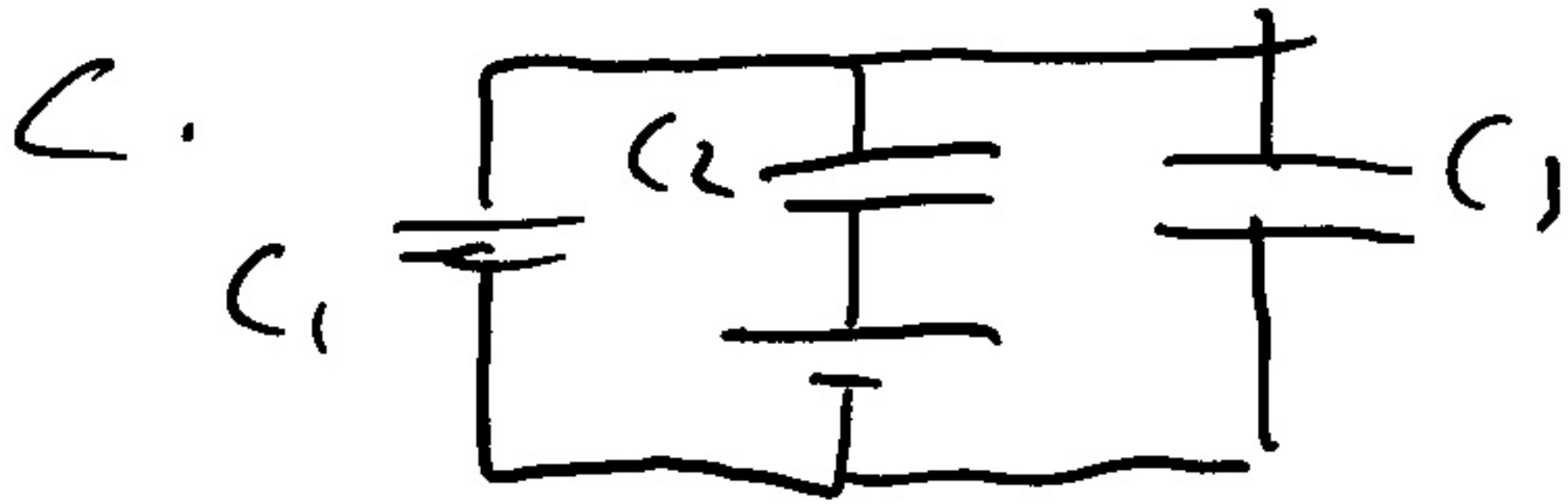
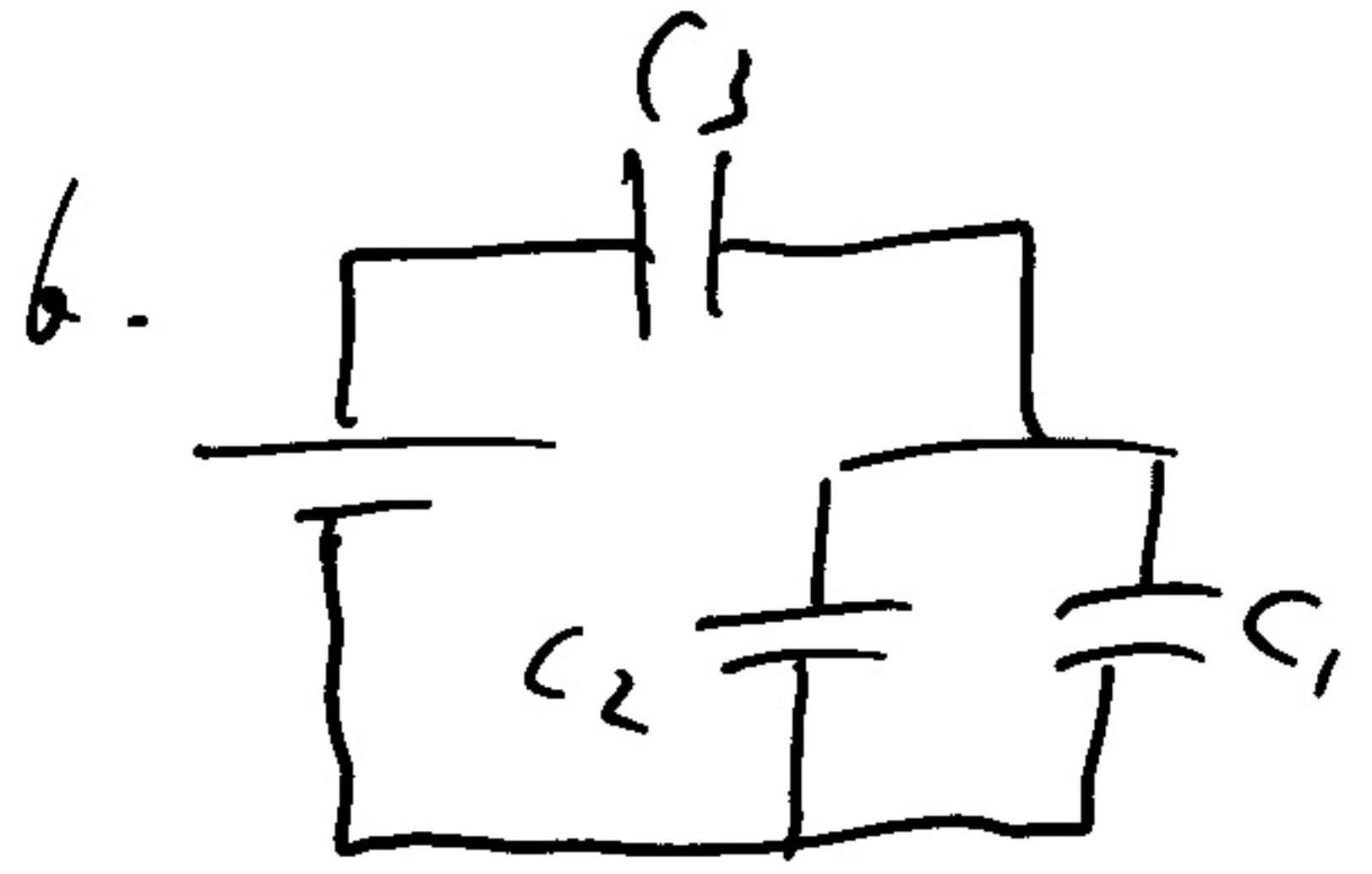





HW C 1:

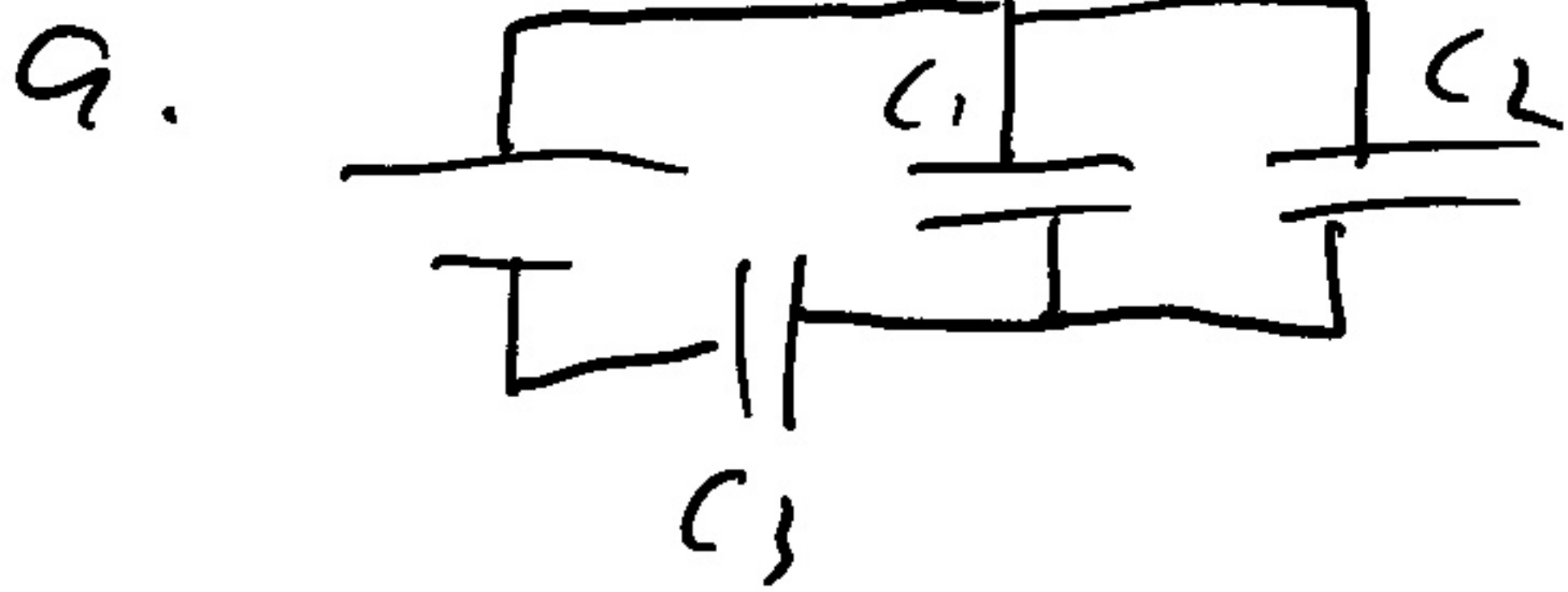


All same circuit!

HW C 2:

Need $|\Delta V_1| = |\Delta V_2|$
 so $Q_1/C_1 = Q_2/C_2$

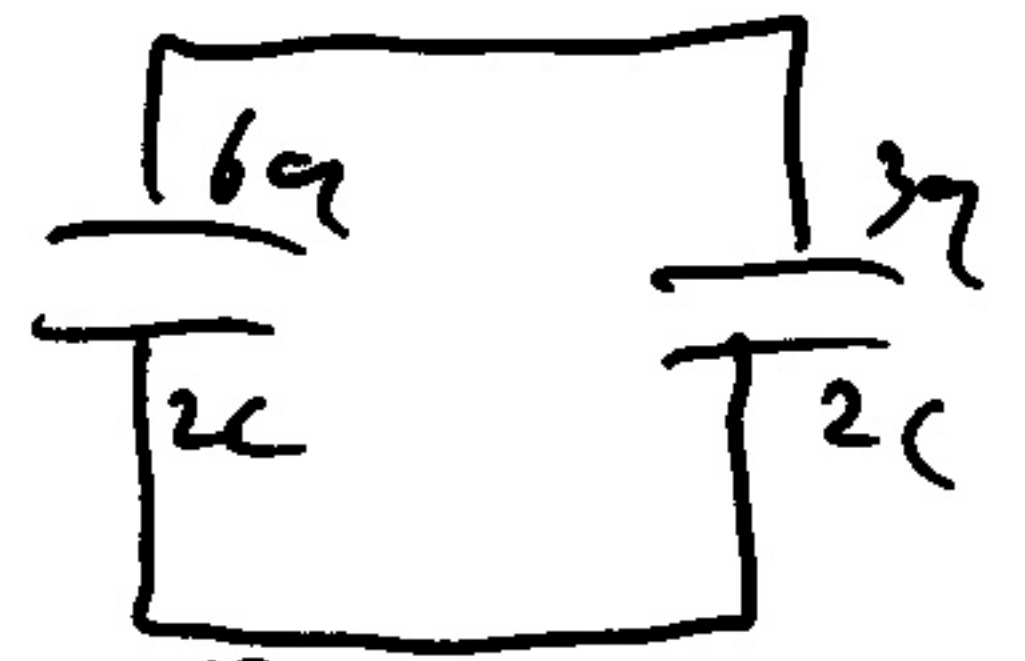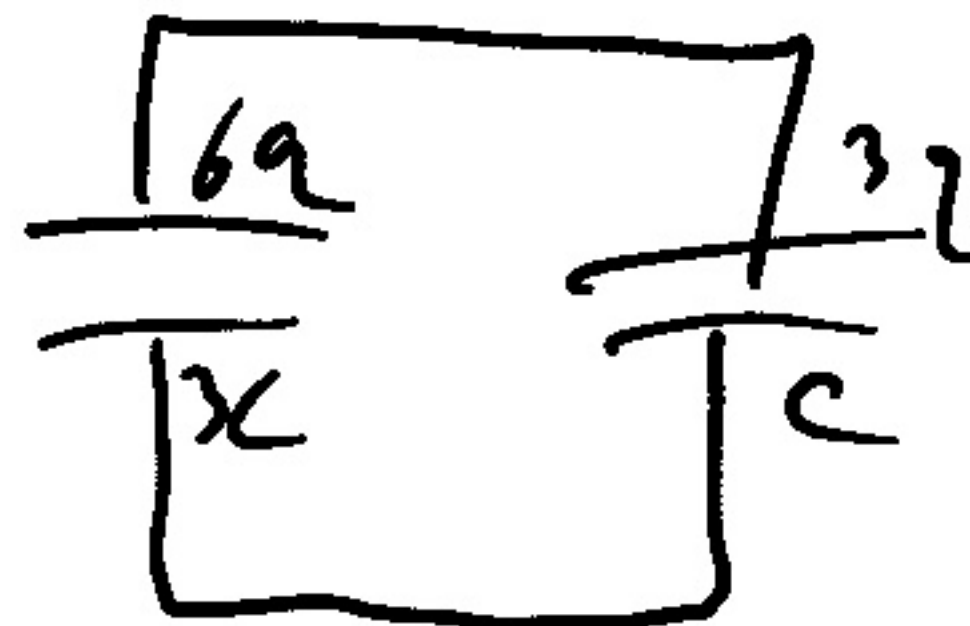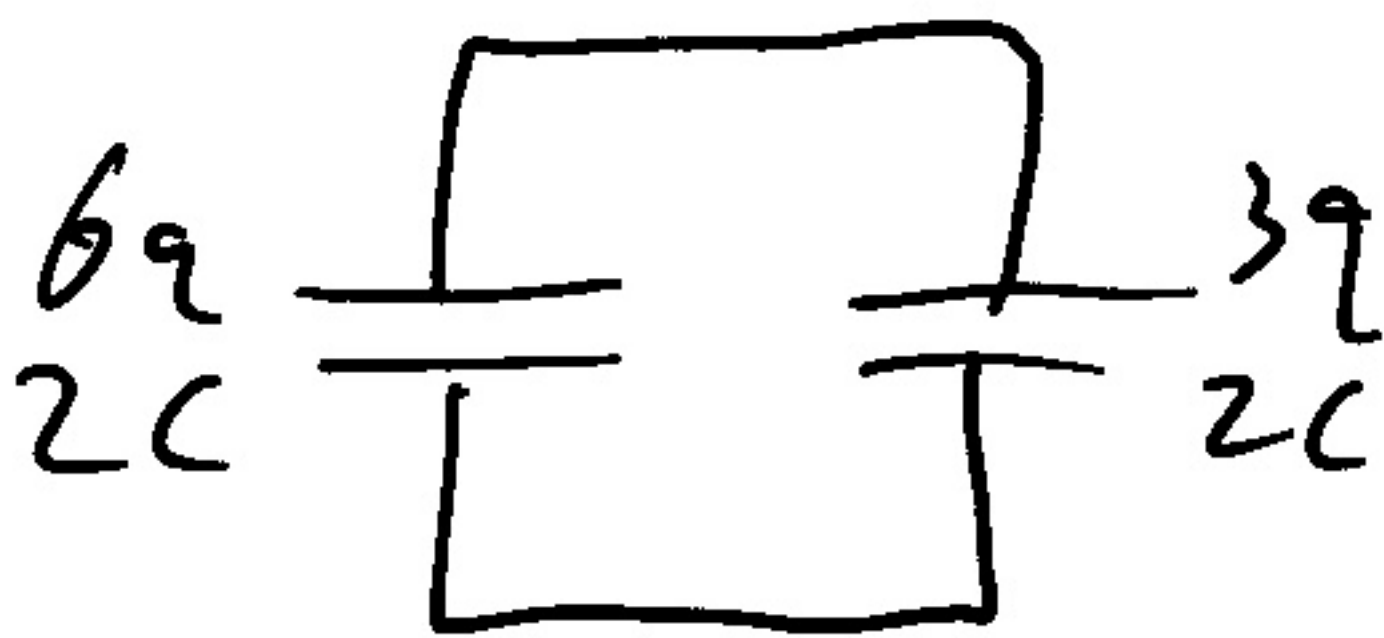

HW C 3:

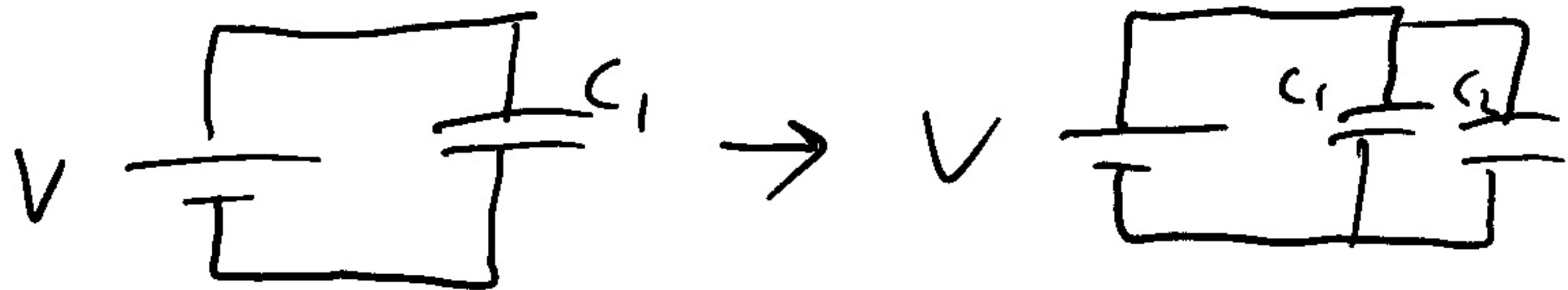


$\Delta V_1 \rightarrow$

$Q_1 \rightarrow$

$C_{tot} \uparrow$

$Q_{tot} \uparrow$

HWCY:

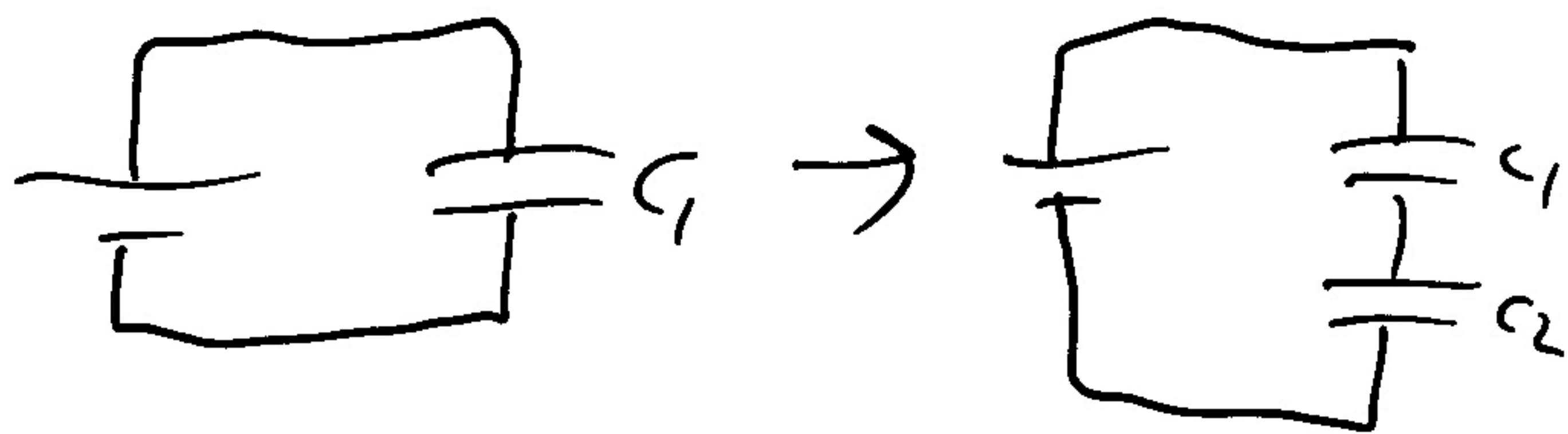


$\Delta V_1 \downarrow$

$Q_1 \downarrow$

$C_{tot} \downarrow$

$Q_{tot} \downarrow$

HWCS:

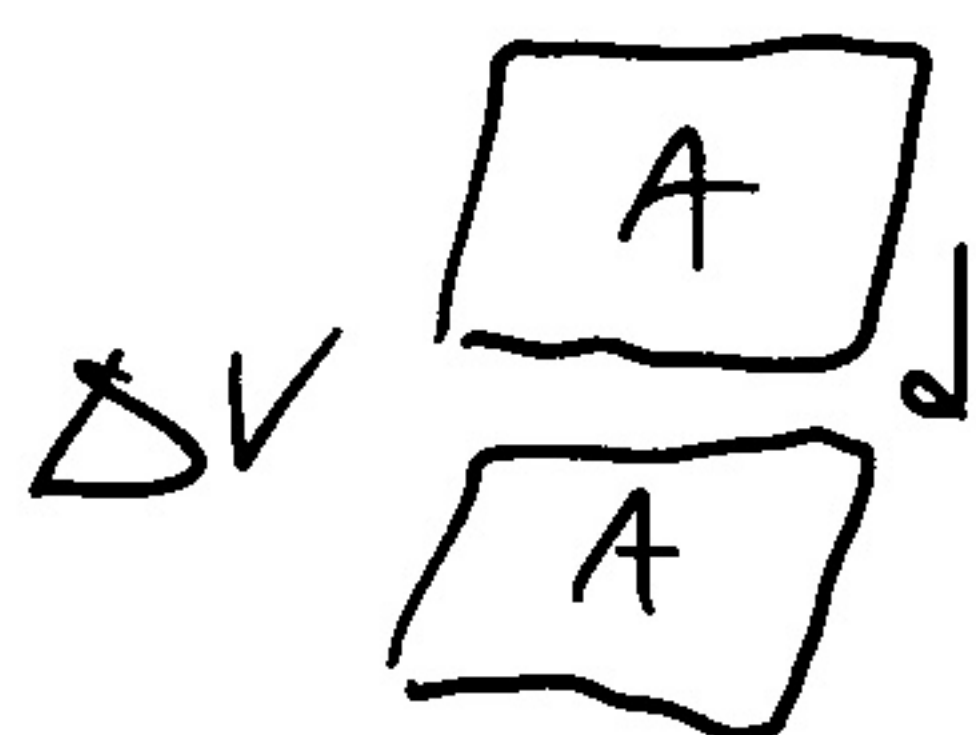

If d decreases

$C \uparrow$

$Q \uparrow$

$E \uparrow$

$\Delta V \rightarrow$

$U = \frac{Q^2}{2C} \uparrow$


$u_E \uparrow$

HWMI: $C = \epsilon_0 A / d$

$\Rightarrow d = \epsilon_0 A / C$
 $\sim 10^{-11} \text{ m}$

tough to build

HW M 2;

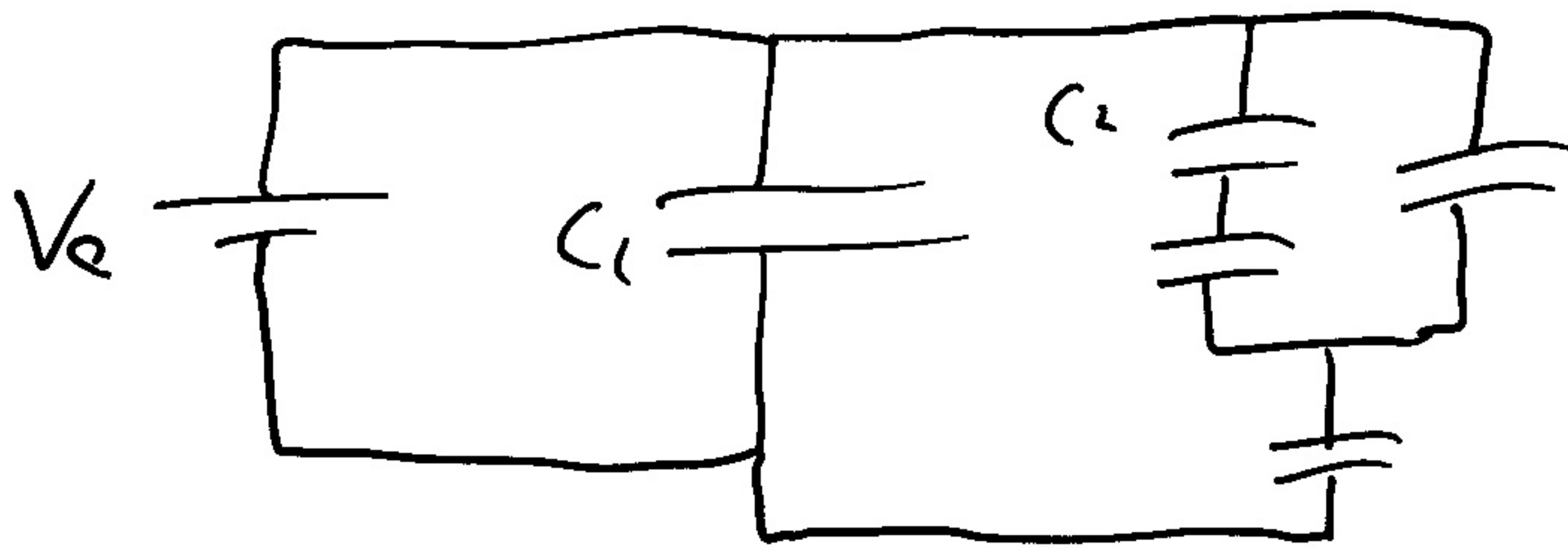

$$C_1 = C \quad Q_1 = C_1 V_0$$

$$C_{2345} = \frac{1}{\left(\frac{1}{C} + \frac{1}{\left(C + \frac{1}{\left(\frac{1}{C} + \frac{1}{C}\right)}\right)}\right)}$$

$$= \frac{1}{\left(\frac{1}{C} + \frac{1}{\left(C + \frac{2}{3}C\right)}\right)}$$


$$= \frac{1}{\left(\frac{1}{C} + \frac{2}{3}C\right)}$$

$$= \frac{1}{\left(\frac{5}{3}C\right)}$$

$$= \frac{3}{5}C$$

so $Q_{tot} = \frac{3}{5} Q_1$

\Rightarrow

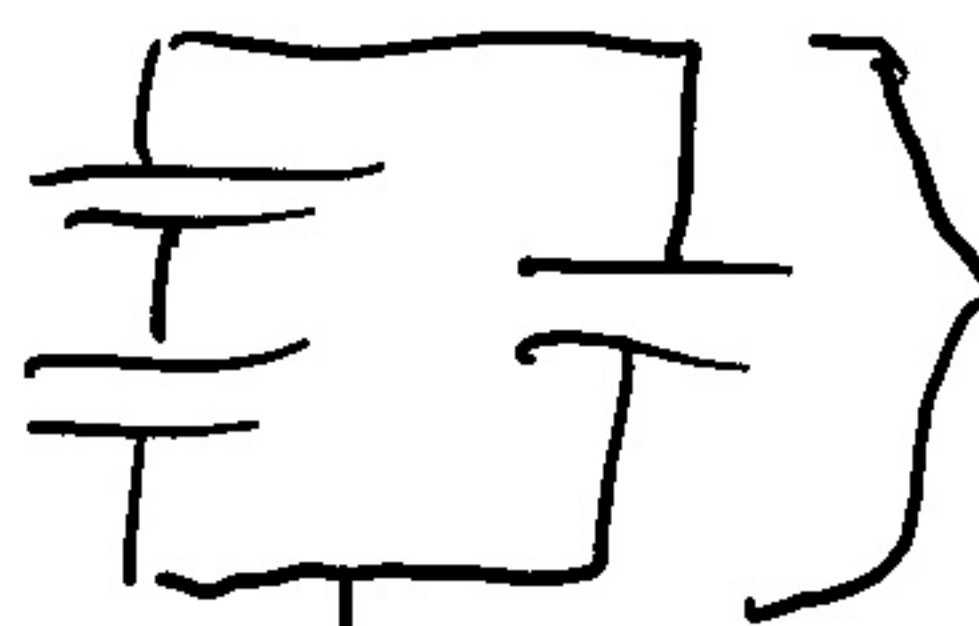


$$\Delta V = \frac{Q_{tot}}{C} = \frac{3}{5} \frac{Q_1}{C} = \frac{3}{5} V_0$$

- which leaves $\frac{2}{5} V_0$ across here
- half of that across $C_2 \Rightarrow V_2 = \frac{1}{5} V_0$
- $Q_2 = (2V_2 = \frac{1}{5} Q_1)$

HW M3:

$$Q = C_1 V = Q_{tot}$$

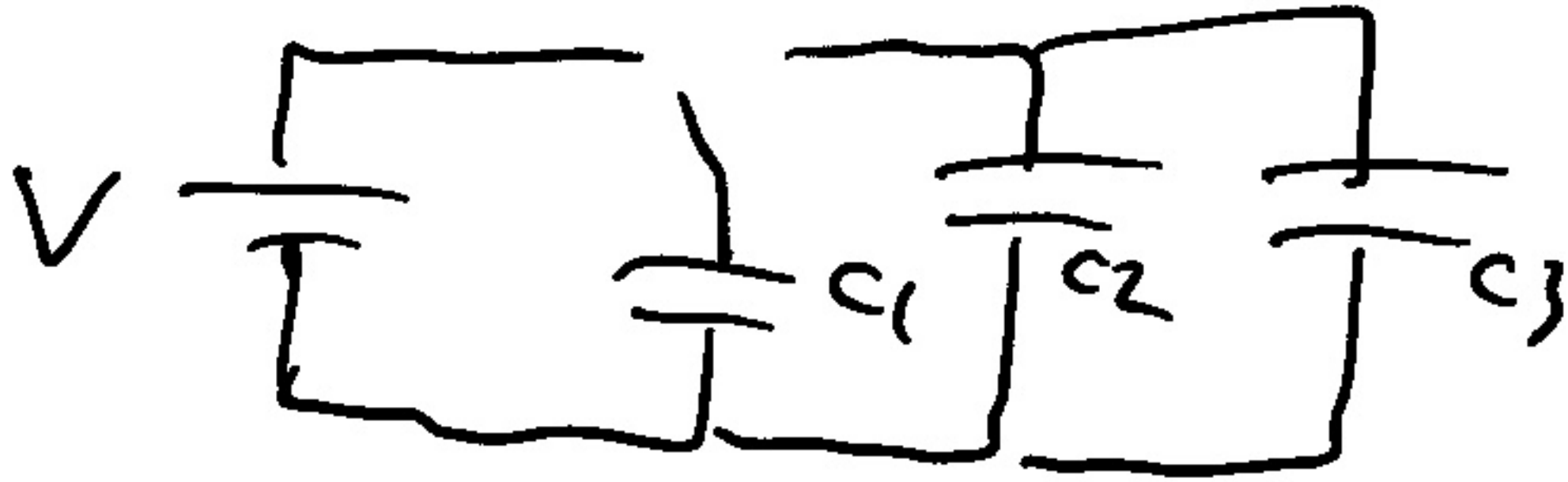

$$C_{tot} = C_1 + C_2 + C_3$$

$$V_f = Q_{tot} / C_{tot}$$

$$Q_{1f} = C_1 V_f = \frac{C_1}{C_{tot}} Q_{tot}$$
$$= \frac{C_1 V}{C_1 + C_2 + C_3}$$