

HW C2:  $P = V^2/R$   
 $R = \rho L/A$

so  $P \propto 1/(L)$

- $\rho, L$  (2)
- $1.2 \rho, 1.2 L$  (3)
- $0.2 \rho, L$  (1)




HW C3:  $I = V/R_{eq}$

$R_{eq-par} = 1/(1/R_1 + 1/R_2)$

$R_{eq-ser} = R_1 + R_2$

$I_{parallel} > I_{R_2} > I_{series}$

HW C4:

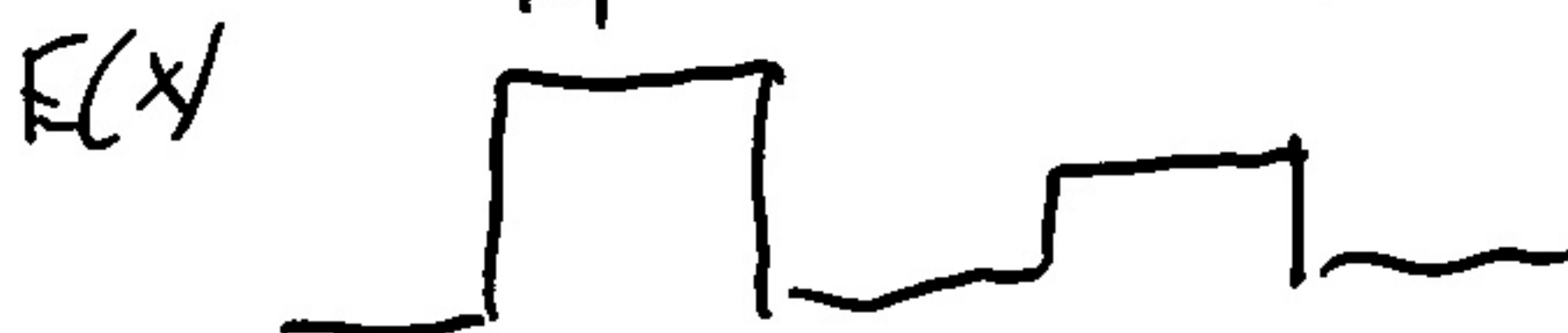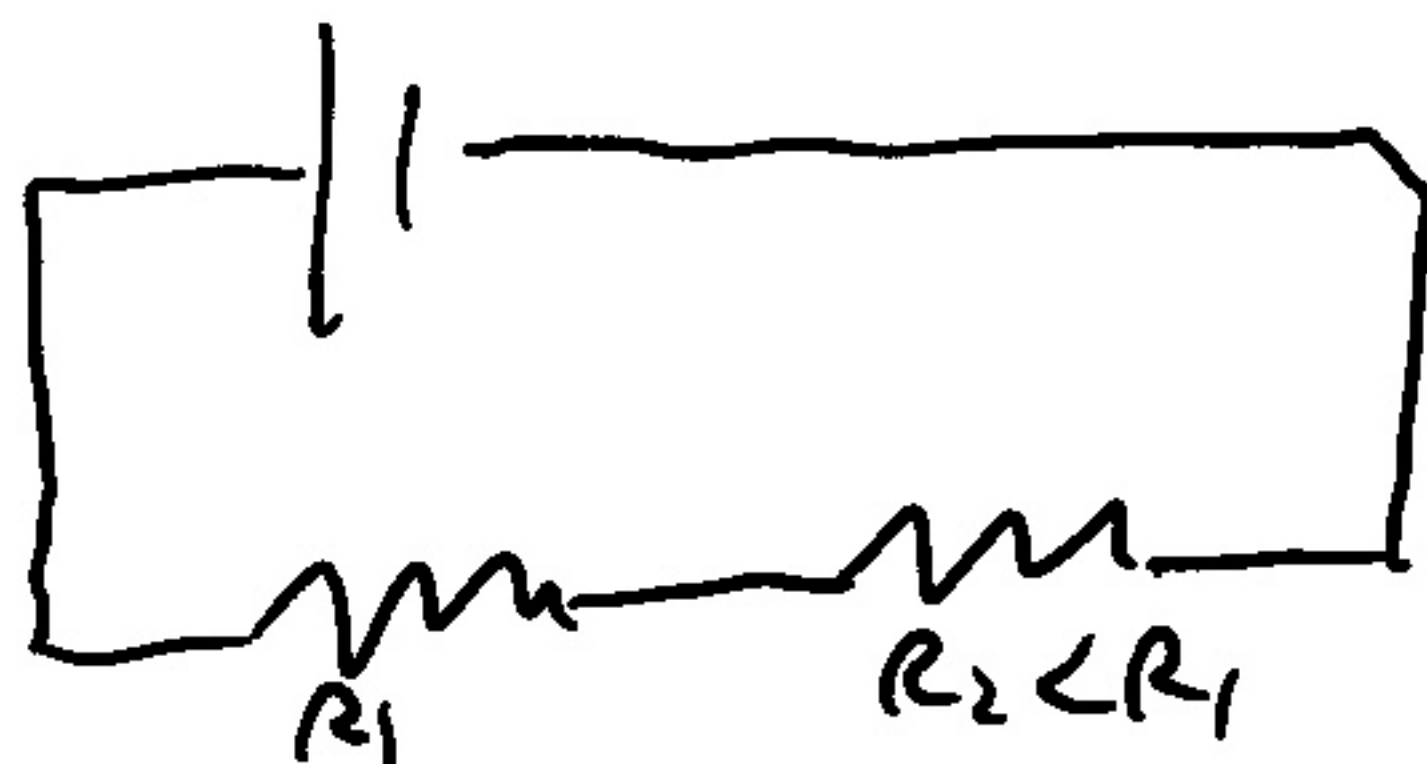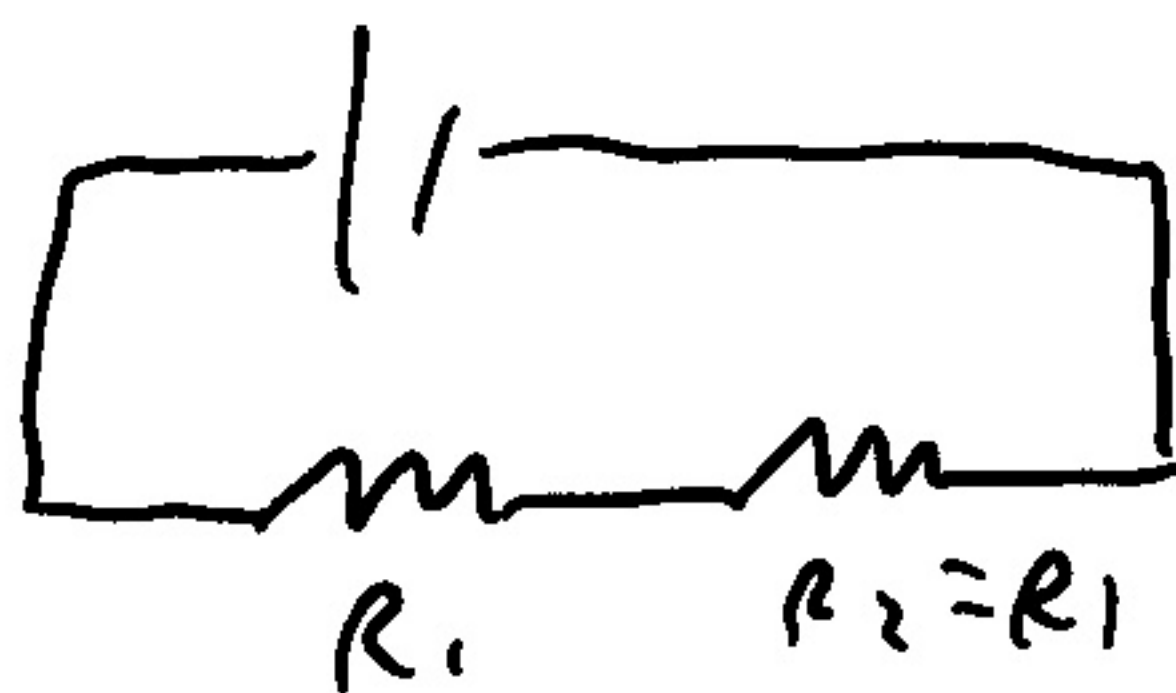


$$E = \rho V$$

$$= \frac{\rho A}{L} V$$

$$= \rho I / L$$

HW M1:

$E(x)$

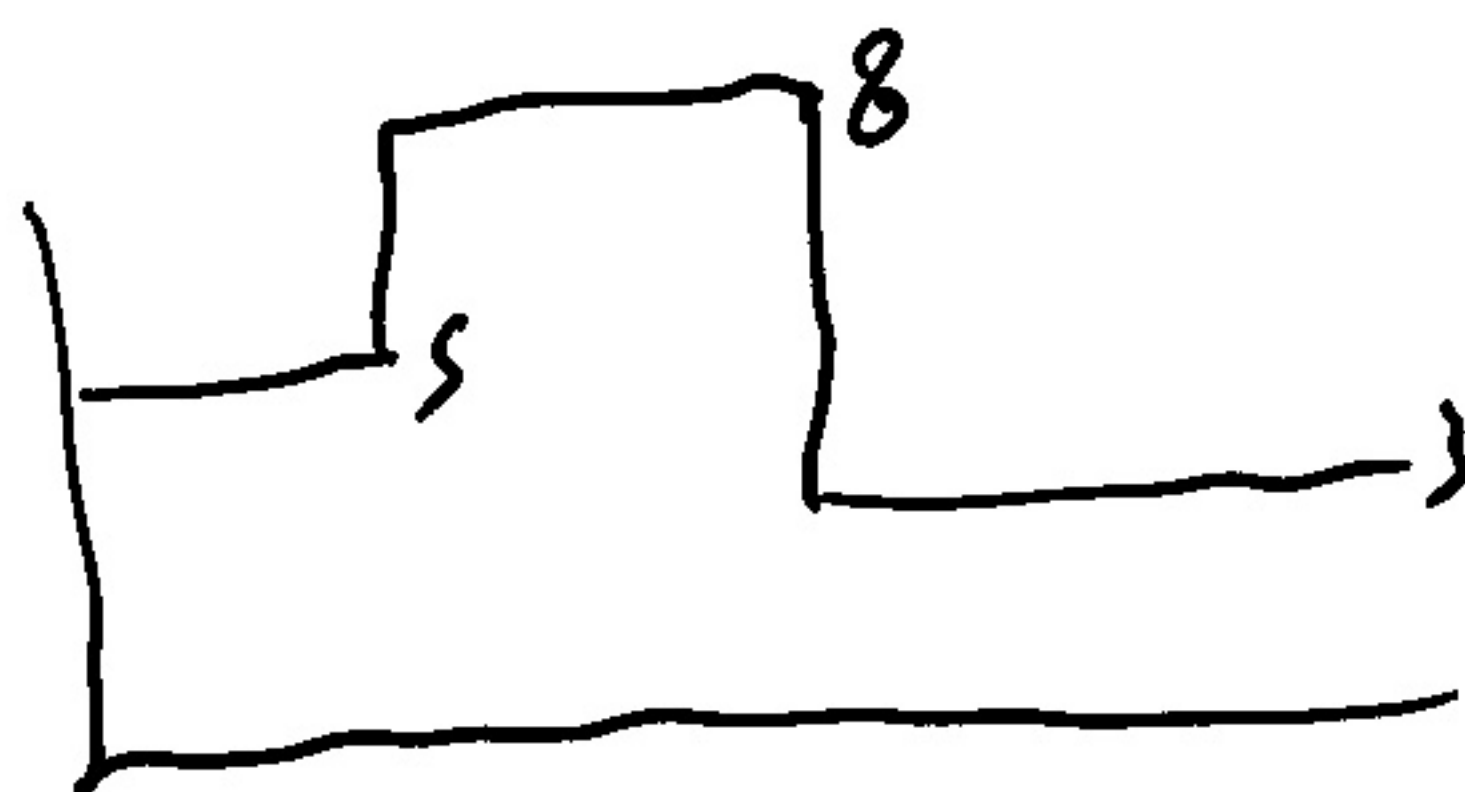

-  $I$  same throughout

$$I = JA$$

$$= \frac{EA}{\rho} = \text{const.}$$

$$\Rightarrow EA = E \cdot \pi r^2 = \text{const.}$$

$$\Rightarrow r_1 = r_3 \cdot \sqrt{\frac{E_3}{E_1}} = r_3 \sqrt{1/5}$$

$$r_2 = r_3 \cdot \sqrt{\frac{E_2}{E_1}} = r_3 \sqrt{3/8}$$

HW M2:  $R = \rho L/A$

$$\rho = v^2/R = v^2 A / \rho L$$

$$I = v/R = vA / \rho L$$

$$vcl = A \cdot L = \text{const.} = Z$$

$$\Rightarrow A = Z/L$$

$$\Rightarrow \rho = v^2 Z / \rho L^2$$

$$I = vZ / \rho L^2$$

$$\rho/I = v \Rightarrow \text{ratio of } v\text{'s} \\ \text{same as } \rho/I$$

$$\rho = \frac{v^2 \tau}{\rho L^2}$$


$$\Rightarrow \frac{\rho_2}{\rho_1} = \frac{V_2^2}{V_1^2} \frac{L_1^2}{L_2^2}$$

$$\Rightarrow L_2/L_1 = \sqrt{\frac{V_2^2}{V_1^2} \frac{\rho_1}{\rho_2}}$$

since volume  $\tau = \text{const.}$

$$A_2/A_1 = L_1/L_2$$

HW 3:

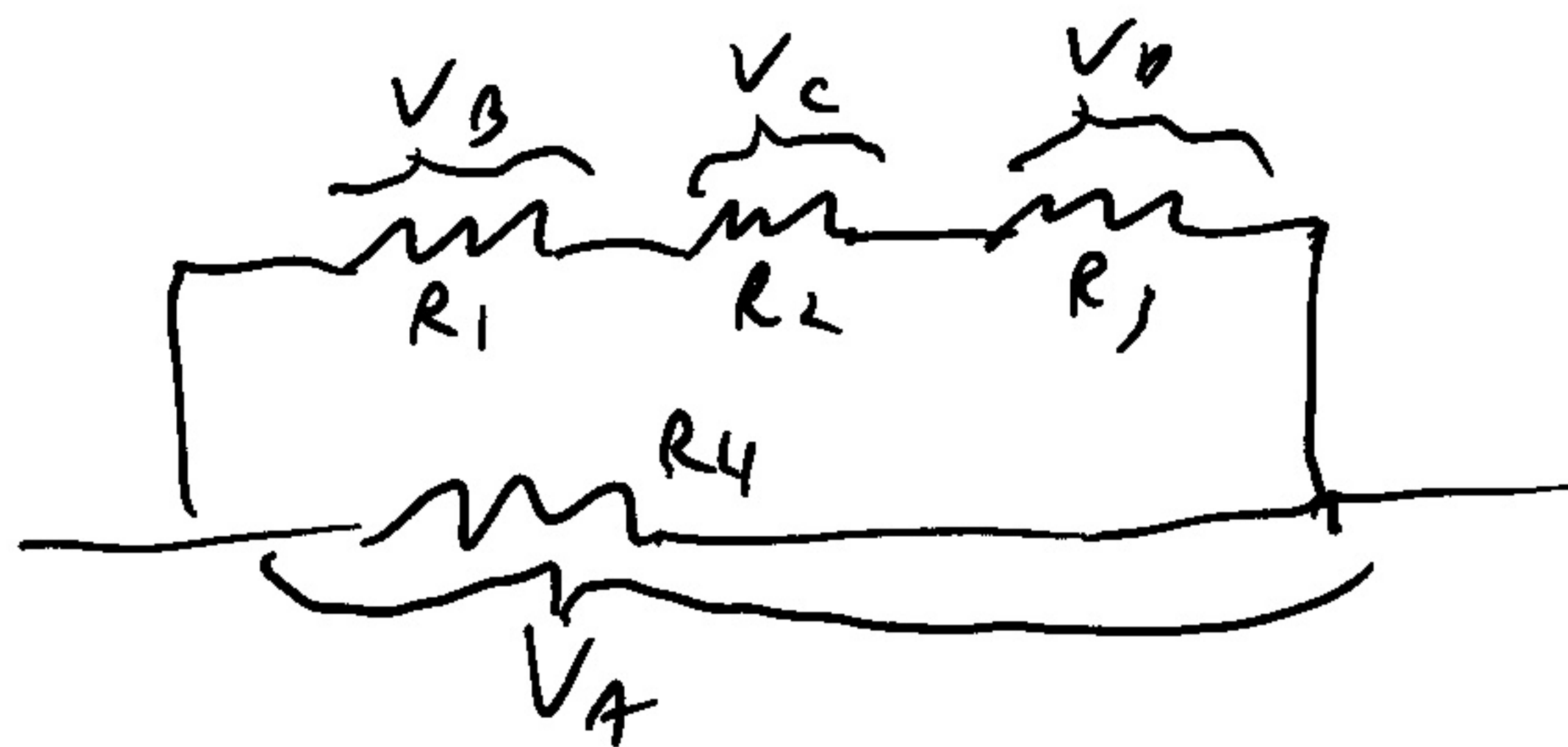

$$V_A = V_B + V_C + V_D$$


$$\Rightarrow V_D = V_A - V_B - V_C$$

$$I = V_D / R_3$$

$$R_1 = V_B / I$$

$$R_2 = V_C / I$$

HW/M4

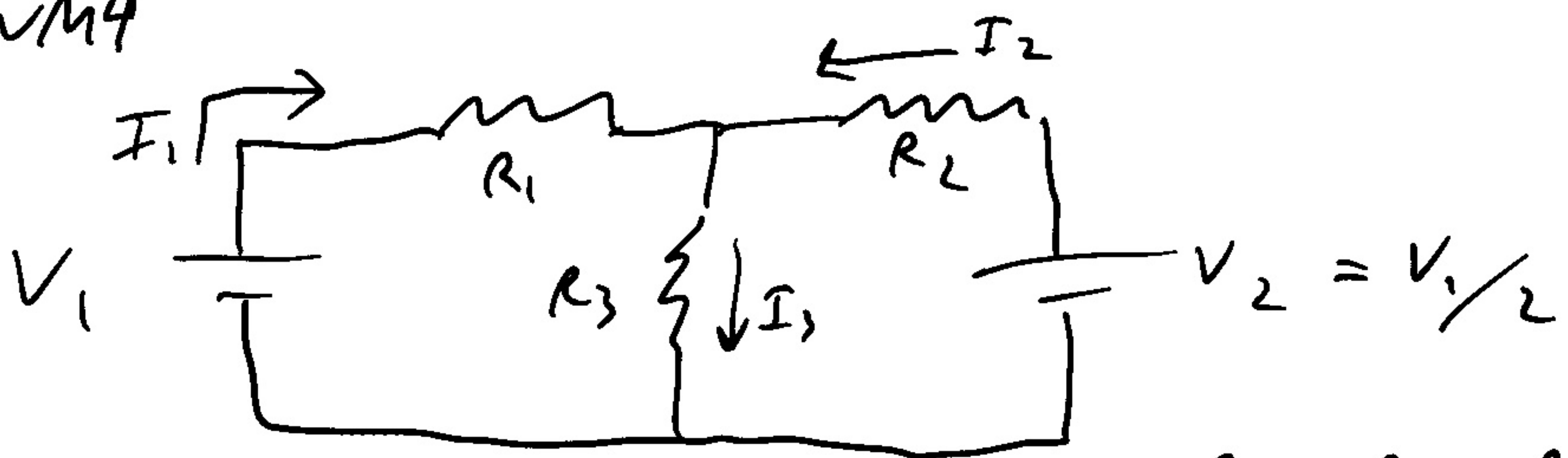

$$R_1 = R_2 = R_3 = R$$

$$I_3 = I_1 + I_2$$

Junction

$$V_1 - I_1 R - I_3 R = 0$$

Left

$$V_2 - I_2 R - I_3 R = 0$$

Right

$$\Rightarrow V_1/2 - I_2 R - I_3 R = 0$$

$$I_2 = I_3 - I_1$$

$$\Rightarrow V_1/2 - I_3 R + I_1 R - I_3 R = 0$$

$$\text{or } V_1 + 2I_1 R - 4I_3 R = 0$$

$$\text{but } V_1 = I_1 R + I_3 R \text{ from right}$$

$$\Rightarrow 3I_1 R - 3I_3 R = 0$$


$$\Rightarrow I_1 = I_3 = I$$

$$\Rightarrow \boxed{I_2 = 0}$$

$$V_1 = I_1 R + I_3 R \\ = 2IR$$

$$\Rightarrow \boxed{I = V_1/2R}$$

HWMS

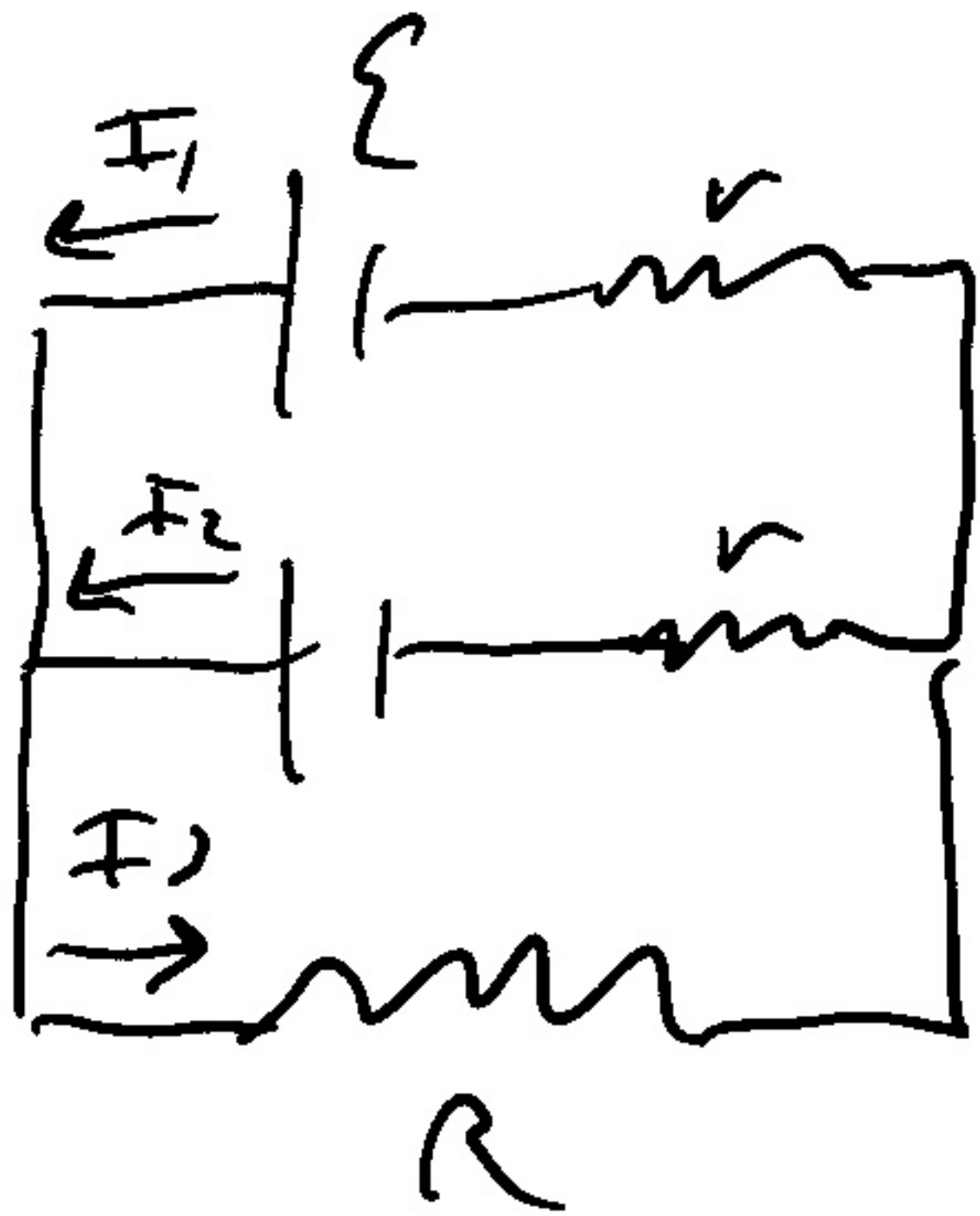

$$\begin{cases} -I_1 r - I_3 R = 0 \\ I_3 = I_1 + I_2 \\ I_1 = I_2 \text{ by symmetry} \end{cases}$$

$$I_3 = I_1 + I_2$$


$I_1 = I_2$  by symmetry

$$\text{so } I_3 = 2I_1$$

$$\text{so } \begin{cases} -I_3/2 r - I_3 R = 0 \end{cases}$$

$$\Rightarrow I_3 = \frac{\epsilon}{r/2 + R}$$

$$= \frac{\epsilon}{r/2 + 2r}$$

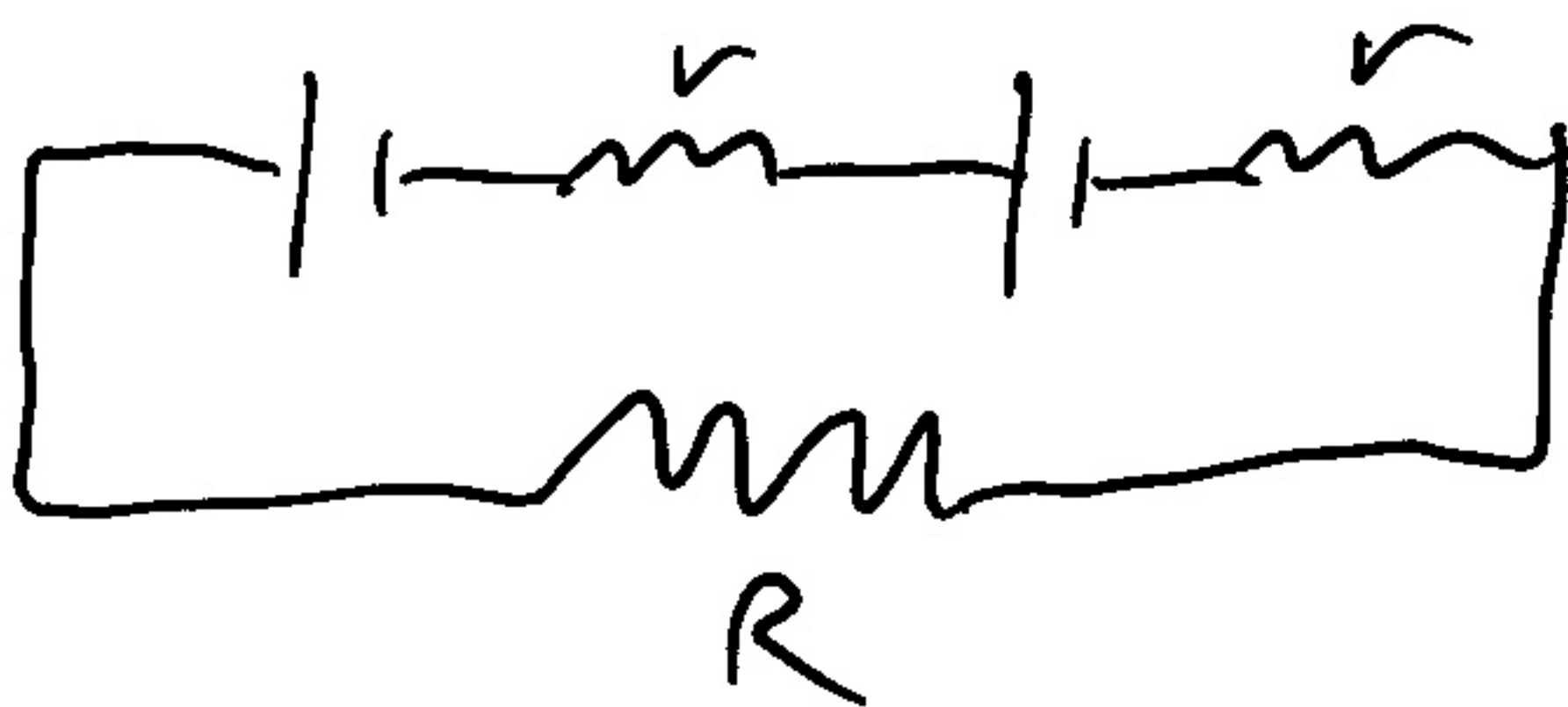

$$\epsilon - I r + \epsilon - I r - I R = 0$$

$$I = \frac{2\epsilon}{2r + R} = \frac{\epsilon}{2r}$$

bigger in series