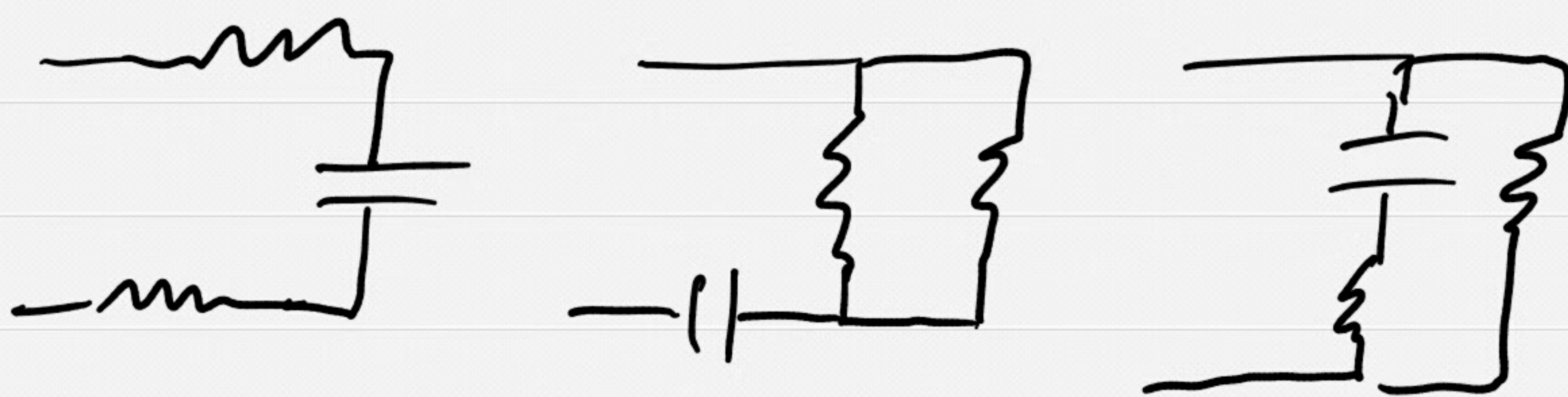


HW C1:  $I_0 = V/R$   
 - so higher curves have lower R

$\tau = RC$

so curves w/ higher RC fall faster

HW C2: Final equilibrium w/ no current through C




- In all 3, all V across capacitor once current stops

- For charging look @ Req in series w/ C.


$R_{1eq} = 2R$ ,  $R_{2eq} = R/2$ ,  $R_{3eq} = R$



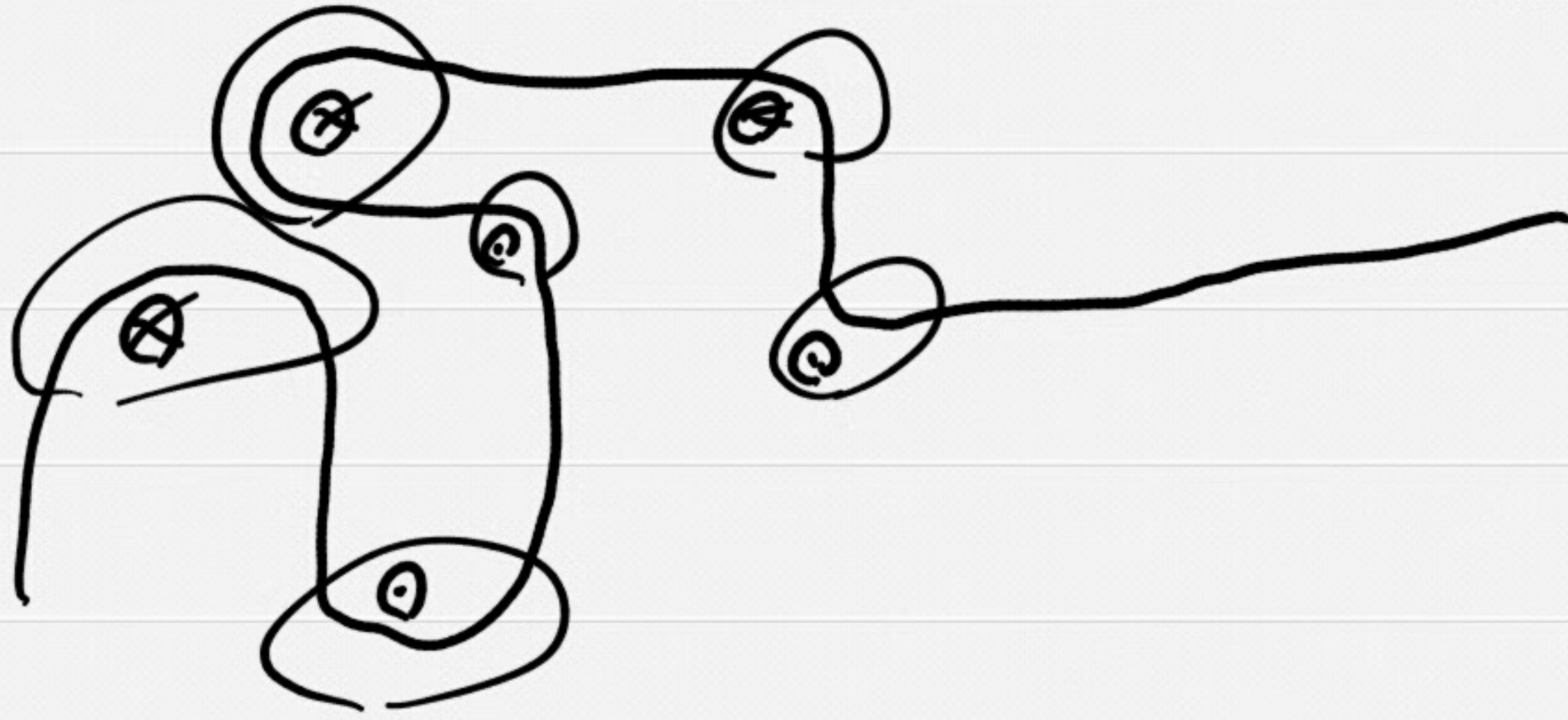HW C4: - Def toward higher potential so  $q = -$   
 - Means deflection in  $B$  is CCW (R-handed)



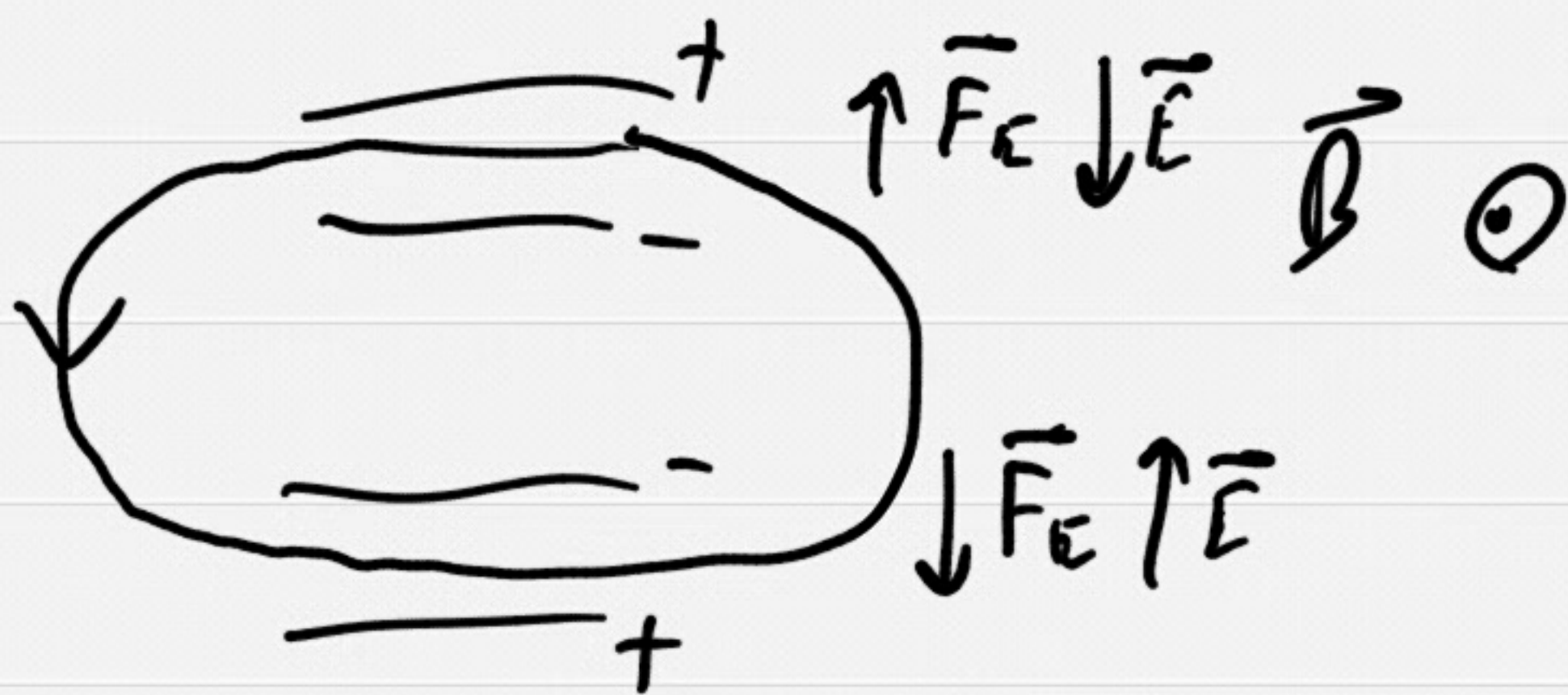HWCS: Need  $\vec{E}, \vec{D}$  to balance in straight sections



HW M1:  $T = RC$   
 $Q_{max} = CV$   
 solve  $Q = CV(1 - e^{-t/RC})$

HW M2: Until lamp flashes  
this is just an RC  
circuit'

$$V_C = Q/C = \mathcal{E} (1 - e^{-t/\tau})$$

Discharge instantaneous since  $R_{\text{lamp}} = 0$

Need  $V_C = V_L$  @  $t = 0.25 \text{ s}$

$$\text{So } V_L = \mathcal{E} (1 - e^{-0.25/\tau})$$

$$V_L/\mathcal{E} = 1 - e^{-0.25/\tau}$$


$$e^{-0.25/\tau} = (1 - V_L/\mathcal{E})$$

$$-0.25/\tau = \ln(1 - V_L/\mathcal{E})$$

$$\tau = -0.25 / \ln(1 - V_L/\mathcal{E})$$

$$R = \tau/C$$

HW M3:

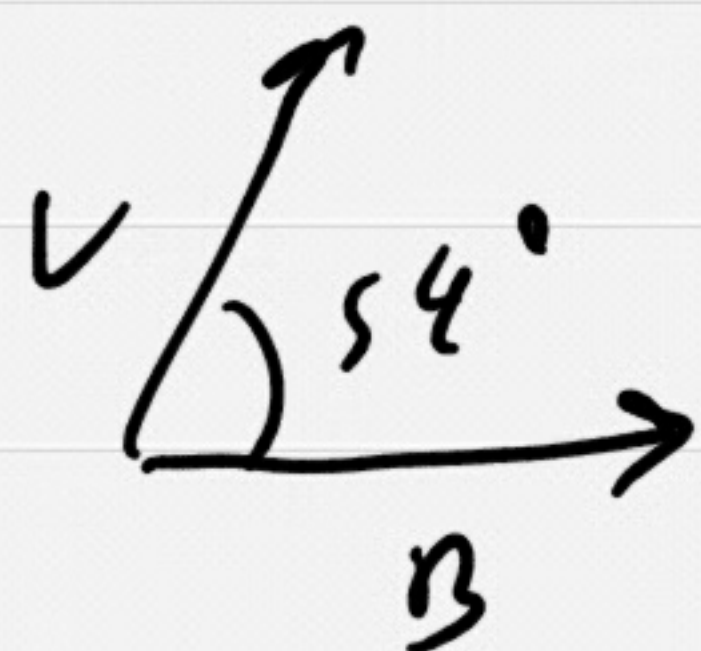

$$\vec{F} = q \vec{v} \times \vec{B}$$

$$|\vec{F}| = q v B \sin \theta$$

$$a = |\vec{F}|/m$$

since  $\vec{F}, \vec{a}$  perpendicular,  $|\vec{v}| = \text{const.}$

HW M4:


$$\vec{B} = B_x \hat{i} + B_y \hat{j} + B_z \hat{k}$$
$$\vec{v} = v_x \hat{i} + v_y \hat{j} + v_z \hat{k}$$

$$\vec{F} = q \vec{v} \times \vec{B}$$

$$F_x = q (v_y B_z - v_z B_y)$$

$$F_y = q (v_z B_x - v_x B_z)$$

HW M5:

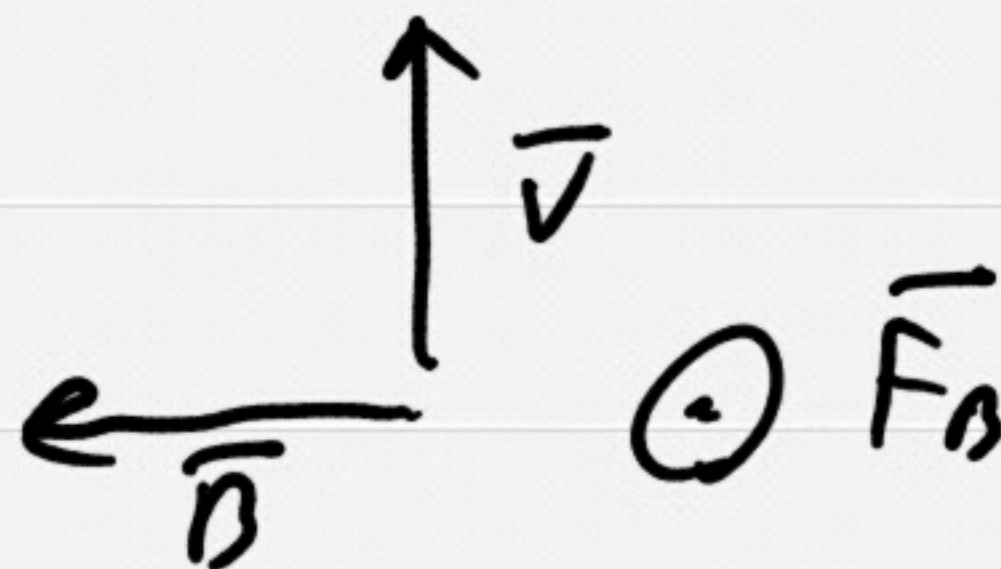

Solve  $\vec{F} = q\vec{v} \times \vec{B}$

say  $\vec{v}(t) = [v_x(t), v_y(t), 0]$

$$\vec{B}(t) = [0, 0, B_z]$$

$$\vec{v} \times \vec{B} = v_y B_z \hat{i} - v_x B_z \hat{j}$$

$$\vec{F} = m \frac{d\vec{v}}{dt}$$

$$= m \left[ \frac{dv_x}{dt}, \frac{dv_y}{dt}, 0 \right]$$

$$= m \frac{dv_x}{dt} \hat{i} + m \frac{dv_y}{dt} \hat{j}$$

$$\Rightarrow m \frac{dv_x}{dt} = q v_y B_z$$

$$m \frac{dv_y}{dt} = -q v_x B_z$$

differentiate:

$$m \frac{d^2 v_x}{dt^2} = q \frac{dv_y}{dt} B_z$$

$$= -\frac{q^2}{m} B_z^2 v_x$$

$$\text{or } \frac{d^2 v_x}{dt^2} = -\left(\frac{qB}{m}\right)^2 v_x$$

$$\text{similarly } \frac{d^2 v_y}{dt^2} = -\left(\frac{qB}{m}\right)^2 v_y$$

solutions are

$$A \cos \omega t, \quad B \sin \omega t$$

$$\omega = qB/m$$

Match initial conditions to solve

say  $\vec{v}(0) = [v_0, 0, 0]$

$$v_x(t) = v_0 \cos \omega t$$

$$v_y(t) = -v_0 \sin \omega t$$

↑ sign to satisfy  
 $dv_y/dt = -\omega v_x$

or  $\vec{v} = v_0 [\cos \omega t, -\sin \omega t, 0]$

- This is a circle w/  $\theta = \omega t = \frac{qB}{m}t$

- Agrees w/  $qvB = mv^2/r$

$$\Rightarrow r = mv/qB = \text{"gyro-radius"}$$

$$\omega = v/r = qB/m$$

$$f = \omega/2\pi = qB/2\pi m = \text{"gyro-frequency"}$$