

Physics II: 1702


Gravity, Electricity, & Magnetism

Professor Jasper Halekas


Van Allen 70 [Clicker Channel #18]

MWF 11:30-12:30 Lecture, Th 12:30-1:30 Discussion

Capacitors In Parallel

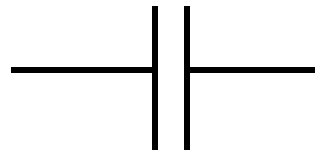

Circuit symbol for a capacitor

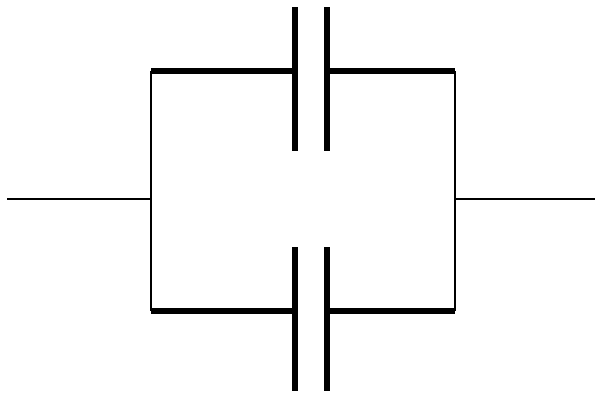


Two capacitors in parallel

$$C_{tot} = C_1 + C_2$$

Think about them like one giant capacitor with the area of 1 and 2 together.

Capacitors in Series

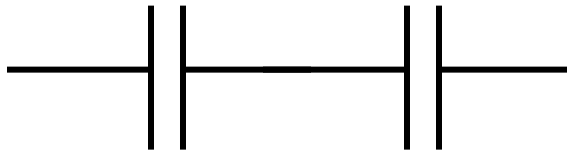


Two capacitors in series

$$C_{tot} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$

One can easily extend these rules to more than two capacitors and more complex combinations.

Capacitors in series

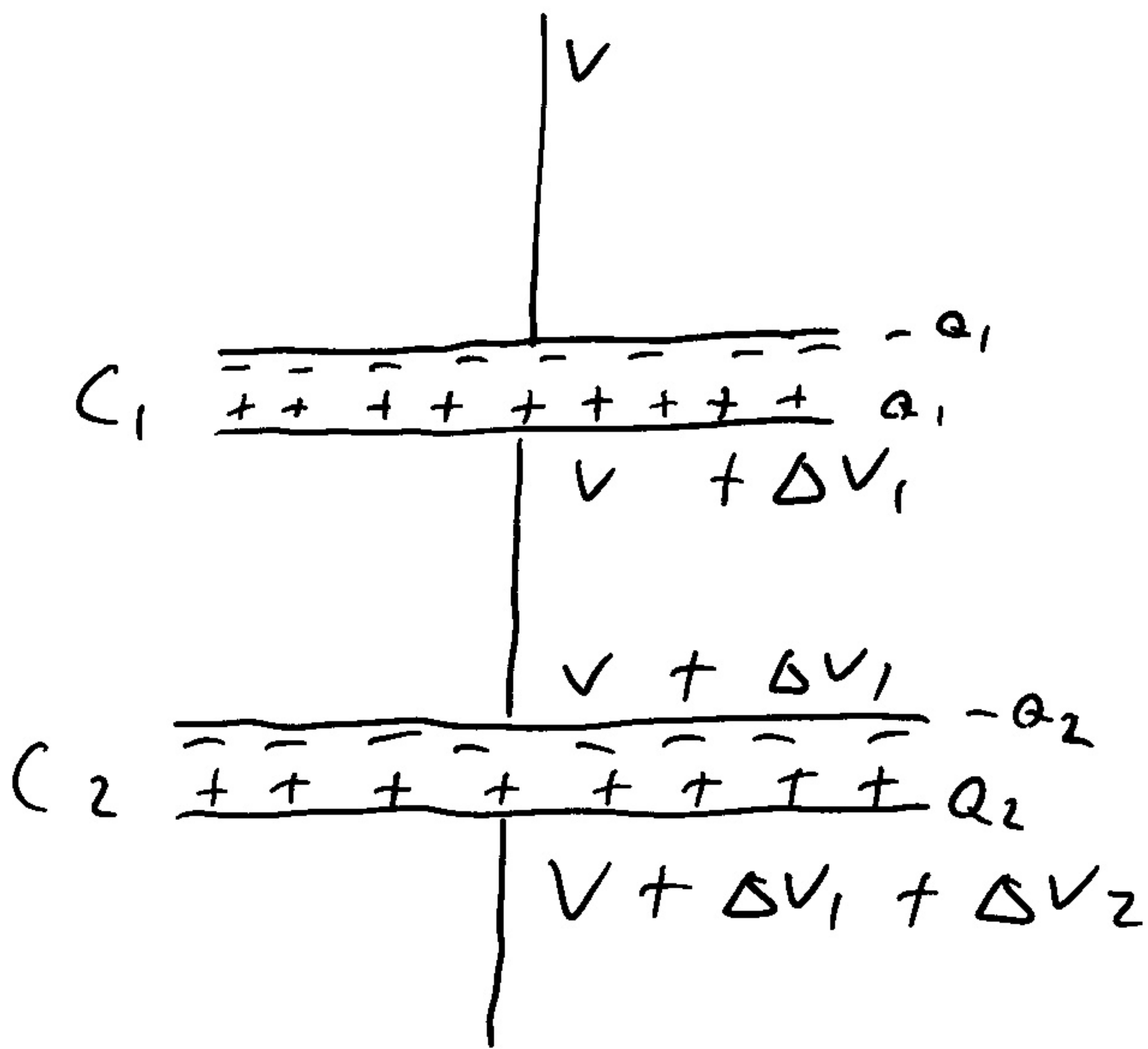

$$C_1 = Q_1 / \Delta V_1$$

$$C_2 = Q_2 / \Delta V_2$$

- But $Q_1 + -Q_2 = 0$
since the region between capacitors is an uncharged conductor before voltage is applied

$$\therefore Q_1 = Q_2 = Q$$

$$C_{tot} = Q / \Delta V_{tot} = Q / (\Delta V_1 + \Delta V_2)$$

$$= Q / (Q_1 / C_1 + Q_2 / C_2)$$


$$= \frac{1}{\left(\frac{1}{C_1} + \frac{1}{C_2} \right)}$$


$$= \frac{C_1 C_2}{C_1 + C_2}$$

- Note that only the charge on the ends of the series capacitors are really "stored". All the charge between capacitors just flows to cancel E in conductors.

Concept Check

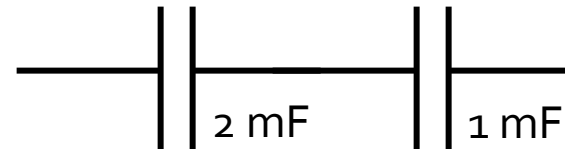- A 2-mF and a 1-mF capacitor are connected in series and a potential difference is applied across the combination. The 2-mF capacitor has:
 1. twice the charge of the 1-mF capacitor
 2. half the charge of the 1-mF capacitor
 3. twice the potential difference of the 1-mF capacitor
 4. half the potential difference of the 1-mF capacitor
 5. none of the above



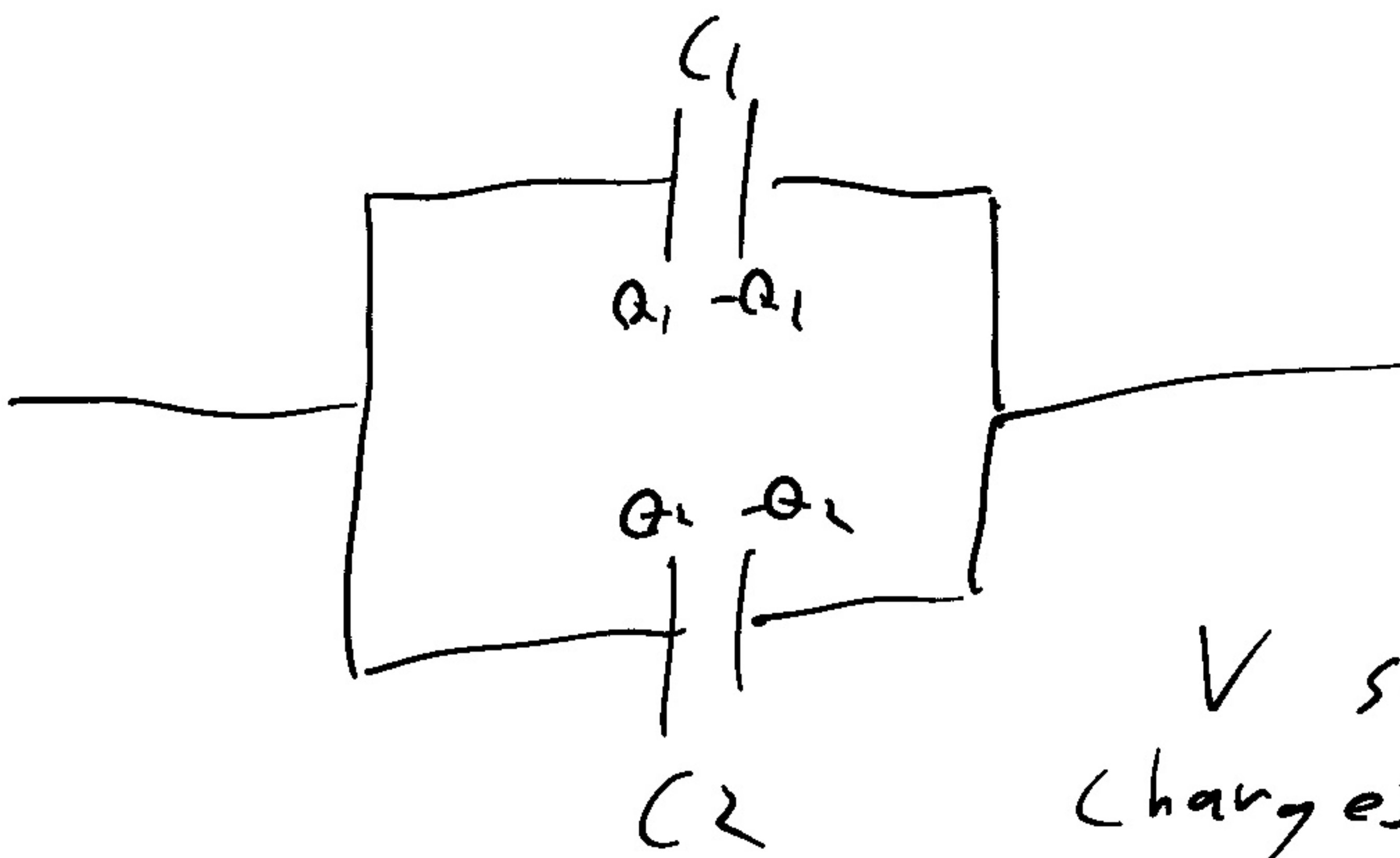


V same
Charges add

$$C_{total} = C_1 + C_2$$

$$Q_{total} = Q_1 + Q_2$$

$$Q_{total} = C_{total} V$$

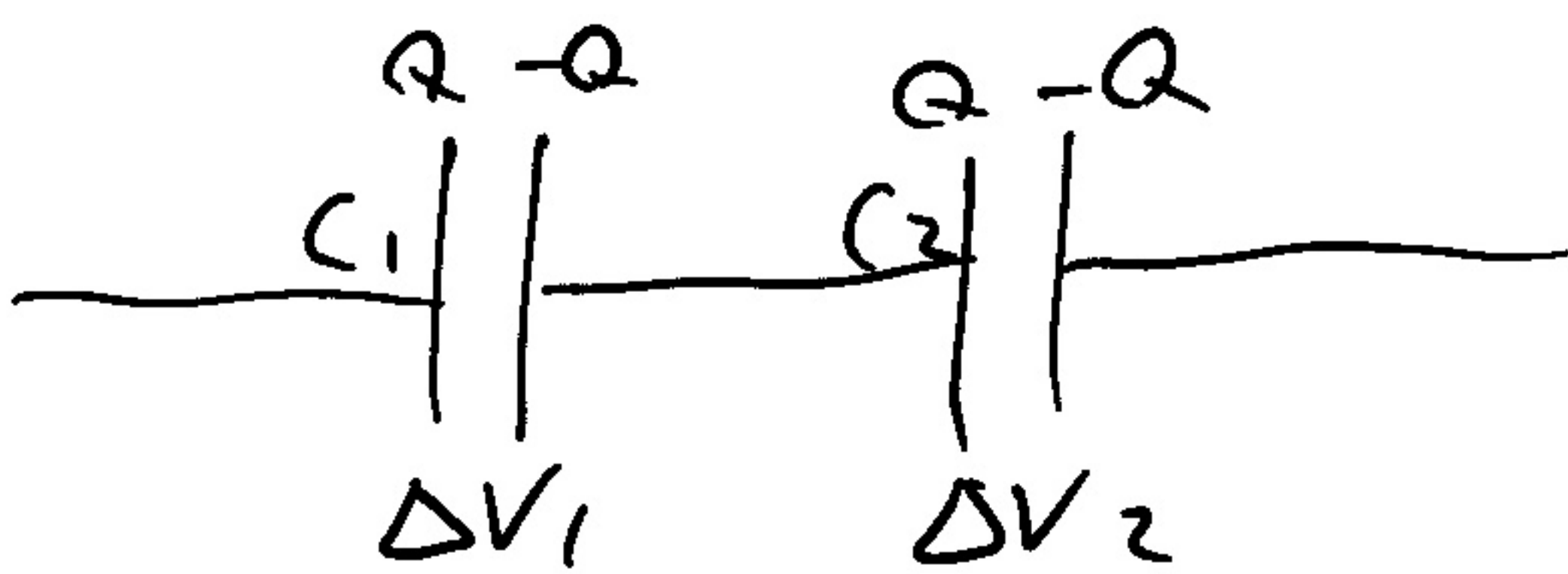

Q same
 ΔV 's add

$$\Delta V_{total} = \Delta V_1 + \Delta V_2$$


$$Q_1 = Q_2 = Q$$

$$C_{total} = Q / \Delta V_{total} = Q / (\Delta V_1 + \Delta V_2)$$

$$= Q / (Q/C_1 + Q/C_2)$$

$$= \frac{1}{(1/C_1 + 1/C_2)}$$

- More complicated
Capacitor Networks

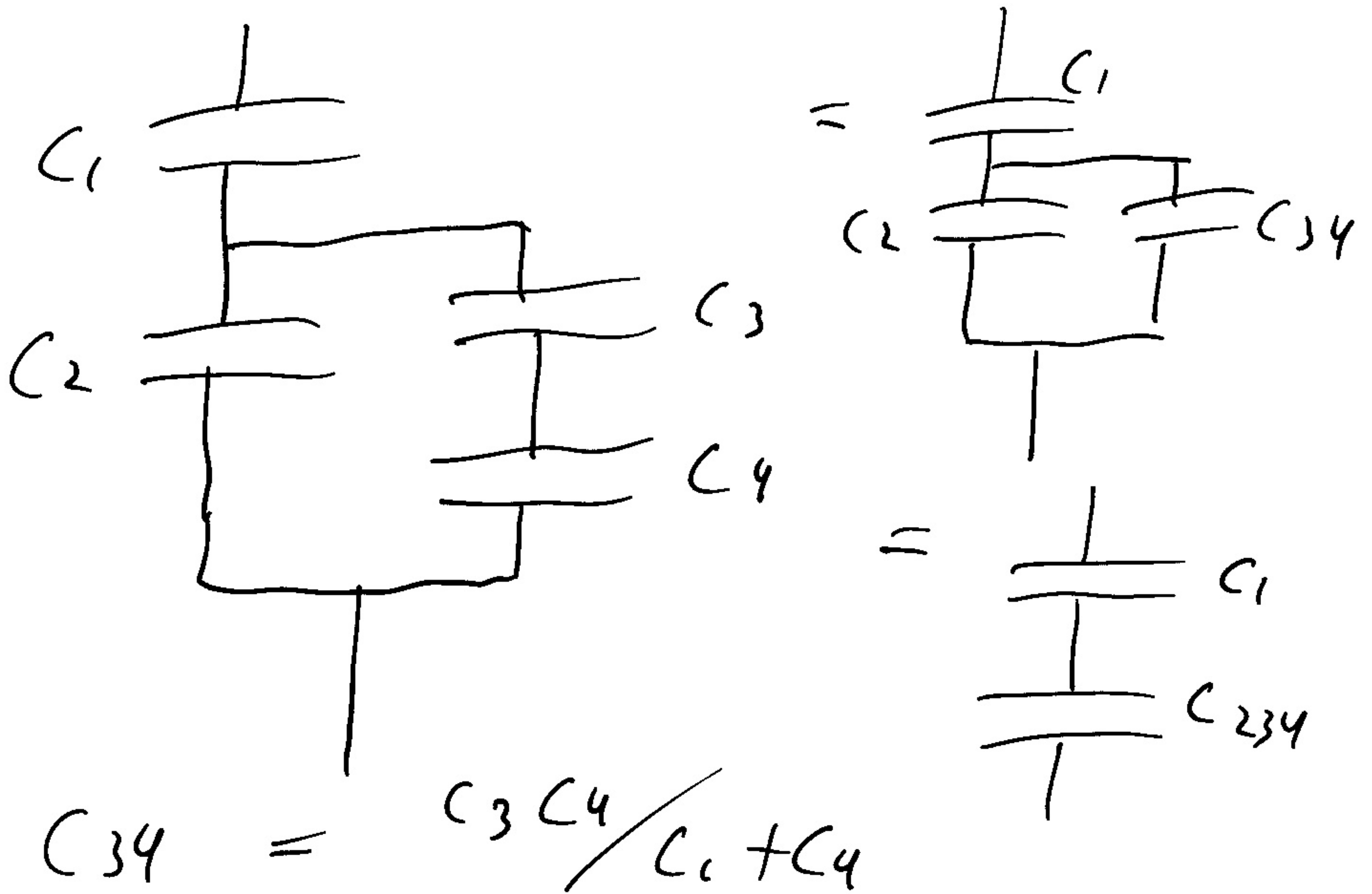

$$C_{234} = C_2 + C_{34}$$


$$C_{1234} = \frac{1}{\left(\frac{1}{C_1} + \frac{1}{C_{234}}\right)}$$

$$= \frac{1}{\left(\frac{1}{C_1} + \frac{1}{\left(C_2 + \frac{C_3 C_4}{C_3 + C_4}\right)}\right)}$$

$$= \frac{C_1 \cdot \left[C_2 + \frac{C_3 C_4}{C_3 + C_4}\right]}{C_1 + C_2 + \frac{C_3 C_4}{C_3 + C_4}}$$

- Energy in Capacitor

- Start w/ uncharged capacitor

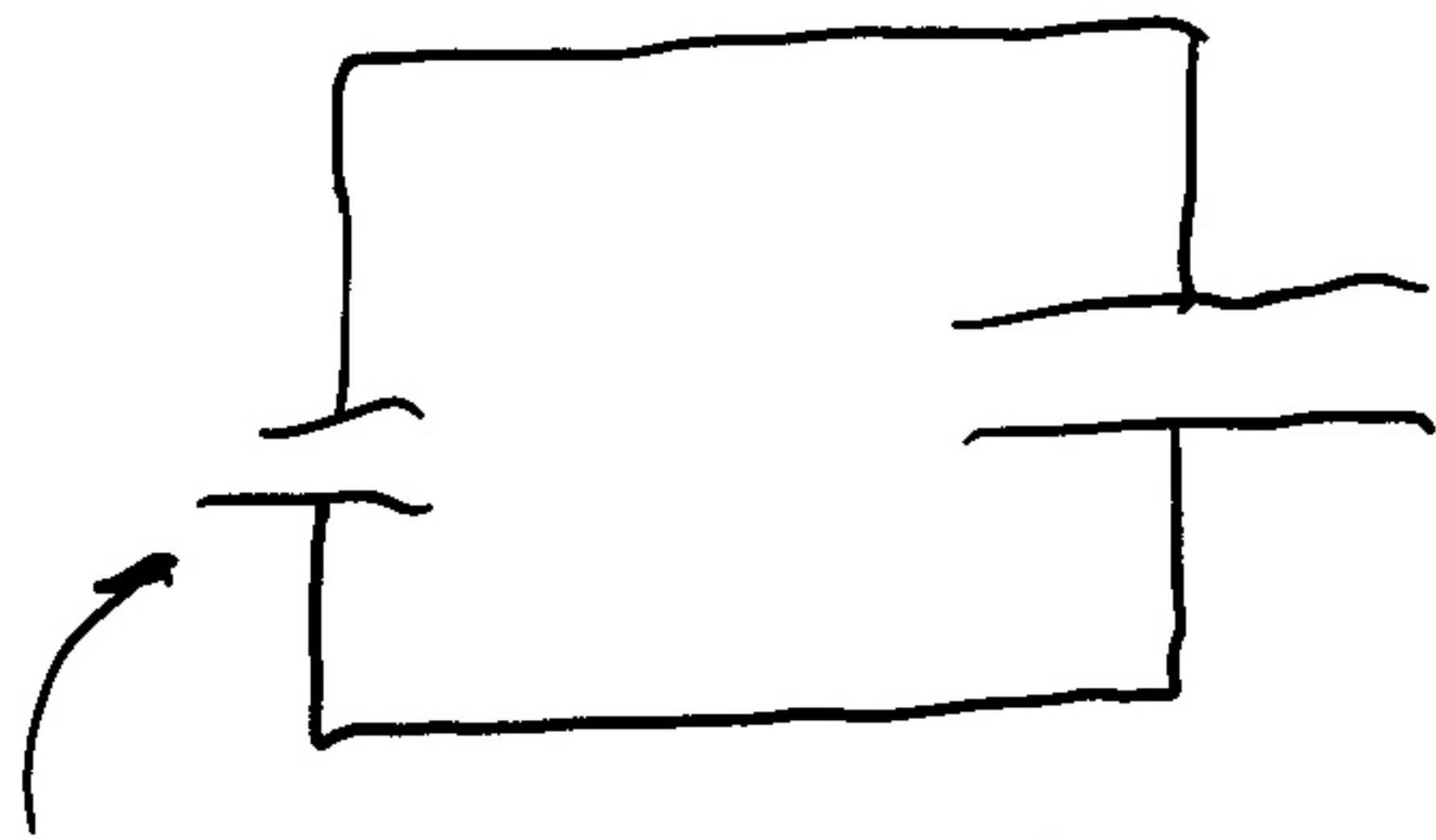

- Turn on battery

- Work must be done to move charge from one plate to the other

$$V = Q/C$$

(like calculating potential of group of charges)

$$\Delta W_{\text{field}} = \int \vec{F} \cdot d\vec{x}$$

$$\begin{aligned} \Delta W_{\text{battery}} &= -\Delta W_{\text{field}} = V \Delta Q \\ &= \Delta Q \cdot Q/C \end{aligned}$$

$$W_{\text{total}} = \int dW = U_{\text{total}}$$

$$= \int_0^Q q dq / C = q^2 / 2C \Big|_0^Q$$

$$= \boxed{\frac{Q^2}{2C}}$$
$$= \frac{1}{2} C V^2$$

Note $U \neq QV$ which would be energy of point charge in potential V

$$E = \sigma / \epsilon_0 = Q / \epsilon_0 A$$

$$\text{So } U = Q^2 / 2C$$

$$= (E \epsilon_0 A)^2 / 2C$$

$$= E^2 \epsilon_0^2 A^2 / 2 \epsilon_0 A / d$$

$$= \frac{\epsilon_0 E^2}{2} \cdot A \cdot d$$

$$= \frac{\epsilon_0 E^2}{2} \cdot \text{Volume}$$

$U/\text{volume} = \text{energy density}$

$$= u = \boxed{\frac{1}{2} \epsilon_0 E^2}$$

True for any electric field in free space!


Energy Stored in a Capacitor

- Storing charge on a capacitor also implies storing energy, since it takes work to put the charge on a capacitor
- Generally speaking, the energy density stored in an electric field is:


$$u_{ES} = \frac{1}{2} \epsilon |\mathbf{E}|^2$$

Adding a Dielectric

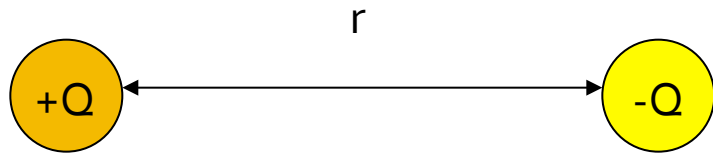Dielectric Material – what if the gap between the capacitor plates is not empty?




$$|\vec{F}| = + \frac{1}{4\pi\epsilon_0} \frac{QQ}{r^2}$$

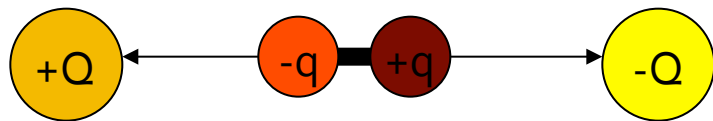

$$|\vec{F}| = + \frac{1}{4\pi\epsilon_0} \frac{QQ}{r^2} - \frac{1}{4\pi\epsilon_0} \frac{1}{2} \frac{qqd}{(r/2)^3}$$

Weakens the force (screening)!

Adding a Dielectric

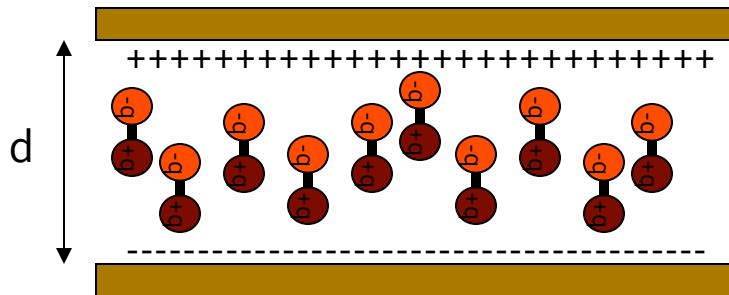


Add a dielectric material.

One parameter – κ (Kappa) the dielectric constant – can describe the modifications.

$$|\vec{F}| = + \frac{1}{4\pi\kappa\epsilon_0} \frac{QQ}{r^2}$$

Concept Check

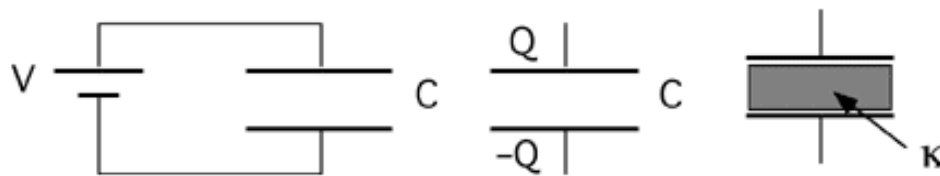Q37) A capacitor with capacitance C is connected to a battery until charged, then disconnected from the battery. A dielectric having constant κ is inserted in the capacitor. What changes occur in the charge, potential and stored energy of the capacitor after the dielectric is inserted?



- 1) V stays same, Q increases, U increases
- 2) V stays same, Q decreases, U stays same
- 3) V increases, Q decreases, U increases
- 4) V decreases, Q stays same, U decreases
- 5) None of the above

$$U = \frac{1}{2} CV^2$$

$$= \frac{1}{2} \frac{Q^2}{C}$$

Q same
C goes up by factor κ

$$\frac{\epsilon_0 A}{d} \rightarrow \kappa \epsilon_0 \frac{A}{d}$$

$U = \frac{Q^2}{C}$ goes down by factor κ

$V = \frac{Q}{C}$ goes down by factor κ

$$U = \frac{Q^2 d}{2 \epsilon_0 A} \rightarrow \frac{Q^2 d}{2 \kappa \epsilon_0 A}$$

in dielectric

$$E \rightarrow \frac{\sigma}{\kappa \epsilon_0} \text{ in dielectric}$$

$$= \frac{Q}{\kappa \epsilon_0 A}$$

$$U = \frac{E^2 \kappa \epsilon_0 A d}{2}$$

$$u = \frac{U}{\text{volume}} = \frac{E^2 \kappa \epsilon_0}{2} = \boxed{\frac{1}{2} \epsilon E^2}$$

w/ $\epsilon = \kappa \epsilon_0$

Dielectric Constant

Easy rule to remember...

Everywhere there is an ϵ_0 , change it to $\kappa\epsilon_0$.

$$|\vec{F}| = + \frac{1}{4\pi\kappa\epsilon_0} \frac{QQ}{r^2}$$

$$\oint \kappa\vec{E} \cdot d\vec{a} = \frac{Q}{\epsilon_0}$$

$$C = \frac{\epsilon_0 A}{d} \Rightarrow \frac{\kappa\epsilon_0 A}{d}$$

Increases the capacitance!

Dielectric Constant

- κ = dielectric constant
 - κ is the degree to which a dielectric is polarized by an external electric field
- Multiply ϵ_0 by κ in every equation to get correct equations in dielectric
- Could also just write $\epsilon = \kappa\epsilon_0$
- In this case ϵ is the permittivity of the dielectric
 - Recall ϵ_0 is the permittivity of free space

Dielectric Constants

A few values:

Vacuum	$K = 1.00000000$
Air	$K = 1.00054$
Paper	$K = 3.5$
Water	$K = 80$
Titanium Ceramic	$K = 130$
Perfect Conductor	$K = \infty$

Electric Fields in an Insulator

A dielectric in an electric field becomes polarized; this allows it to reduce the electric field in the gap for the same potential difference.

