

Physics II: 1702

Gravity, Electricity, & Magnetism

Professor Jasper Halekas

Van Allen 70 [Clicker Channel #18]

MWF 11:30-12:30 Lecture, Th 12:30-1:30 Discussion

Announcements

- HW5 Due On Wiley Plus Tonight

Dielectrics (Insulators)

Easy rule to remember...

Everywhere there is an ϵ_0 , change it to $\epsilon = \kappa\epsilon_0$.

$$|\vec{F}| = + \frac{1}{4\pi\kappa\epsilon_0} \frac{QQ}{r^2}$$

$$C = \frac{\epsilon_0 A}{d} \Rightarrow \frac{\kappa\epsilon_0 A}{d}$$

$$\oint \vec{E} \cdot d\vec{a} = \frac{Q_{enc}}{\kappa\epsilon_0}$$

$$u_{ES} = \frac{1}{2} \epsilon |\mathbf{E}|^2$$

Vacuum

$\kappa = 1.0000000$

Air

$\kappa = 1.00054$

Paper

$\kappa = 3.5$

Water

$\kappa = 80$


Titanium Ceramic

$\kappa = 130$

Perfect Conductor

$\kappa = \infty$

Capacitor

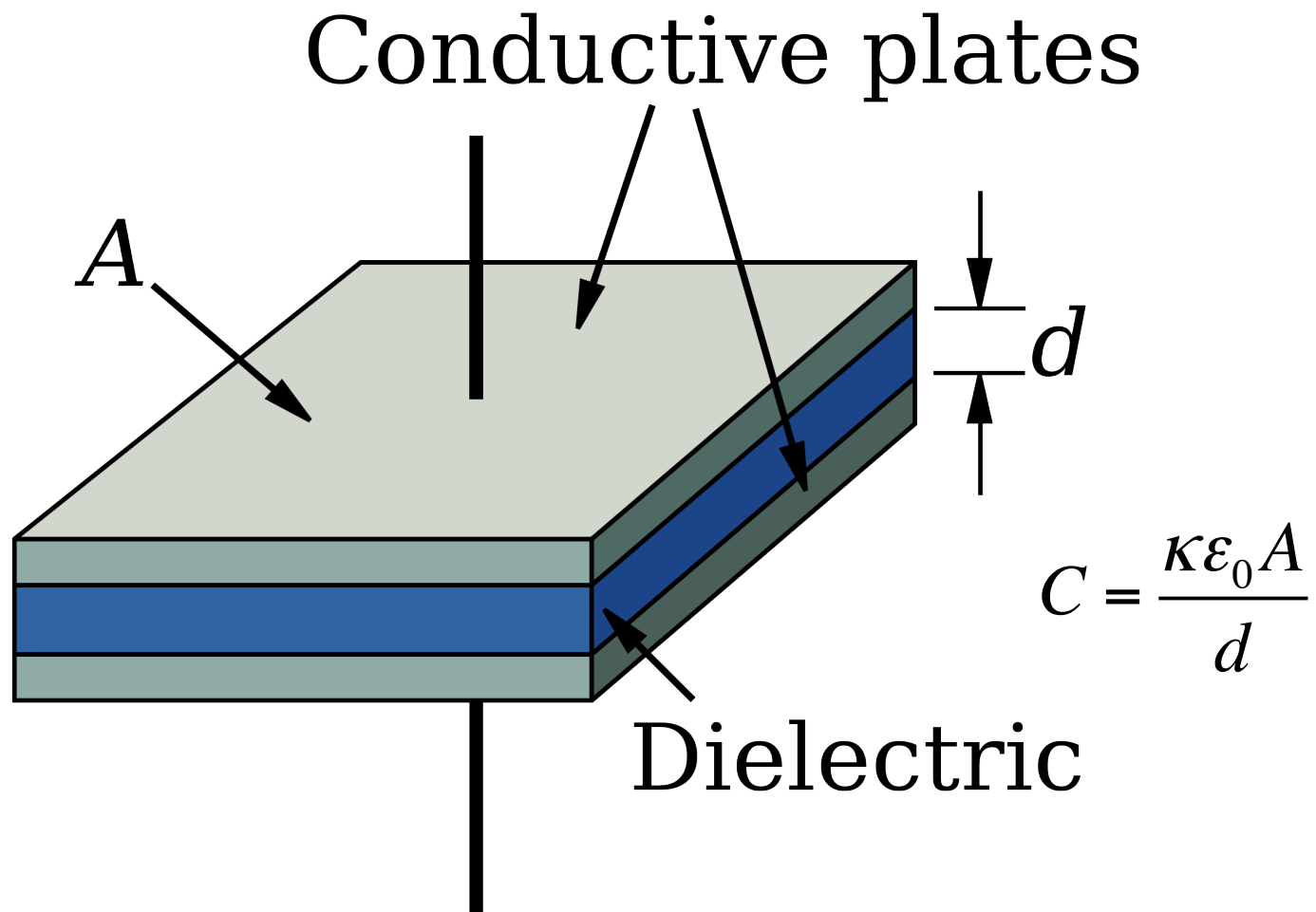

What About Conductors?

- Why can't you make an awesome capacitor with a conductor in the center?
- Given an infinite dielectric constant, you would think you could store an infinite amount of charge per voltage ($C = Q/V$)
- But, the voltage across a conductor is always zero
- So, the charge is $\infty \times 0$
 - Indeterminate, but in this case 0 wins

Conductors Make Bad Capacitors

- Even an almost-conductor makes a poor dielectric, because it conducts current
- This means that any charge stored on the capacitor will leak through
- This can happen gradually, or very suddenly, in the form of a breakdown




EMF

- EMF = ElectroMotive Force
 - Not actually a force!



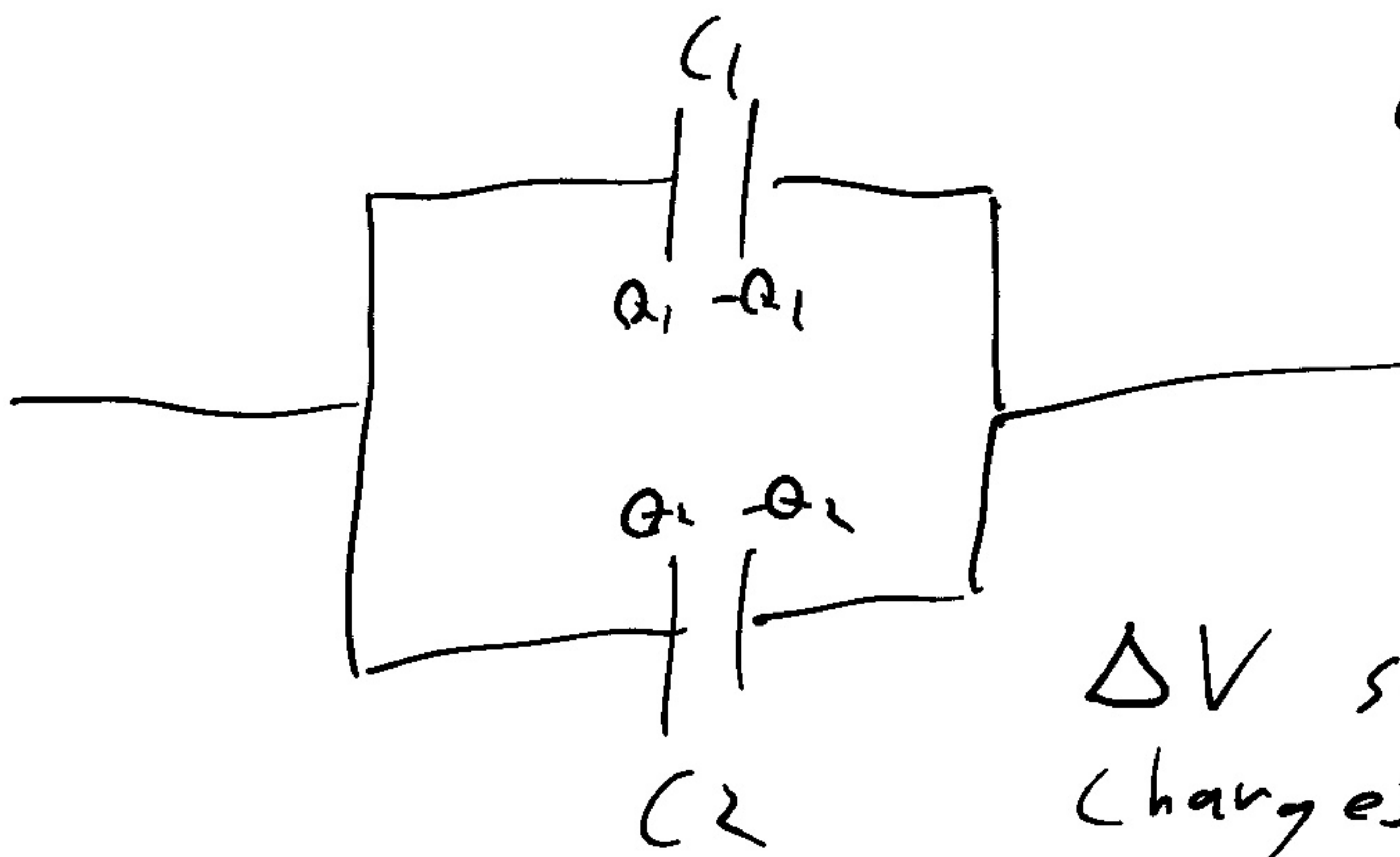- Think of the EMF as something that produces a voltage difference
 - Could be a battery
 - Could be an electromagnetic power supply
 - Could be a changing magnetic field




$$C = Q/V$$

ΔV same
Charges add

$$Q_{total} = Q_1 + Q_2$$

$$C_{total} \Delta V = C_1 \Delta V + C_2 \Delta V$$

$$C_{total} = C_1 + C_2$$

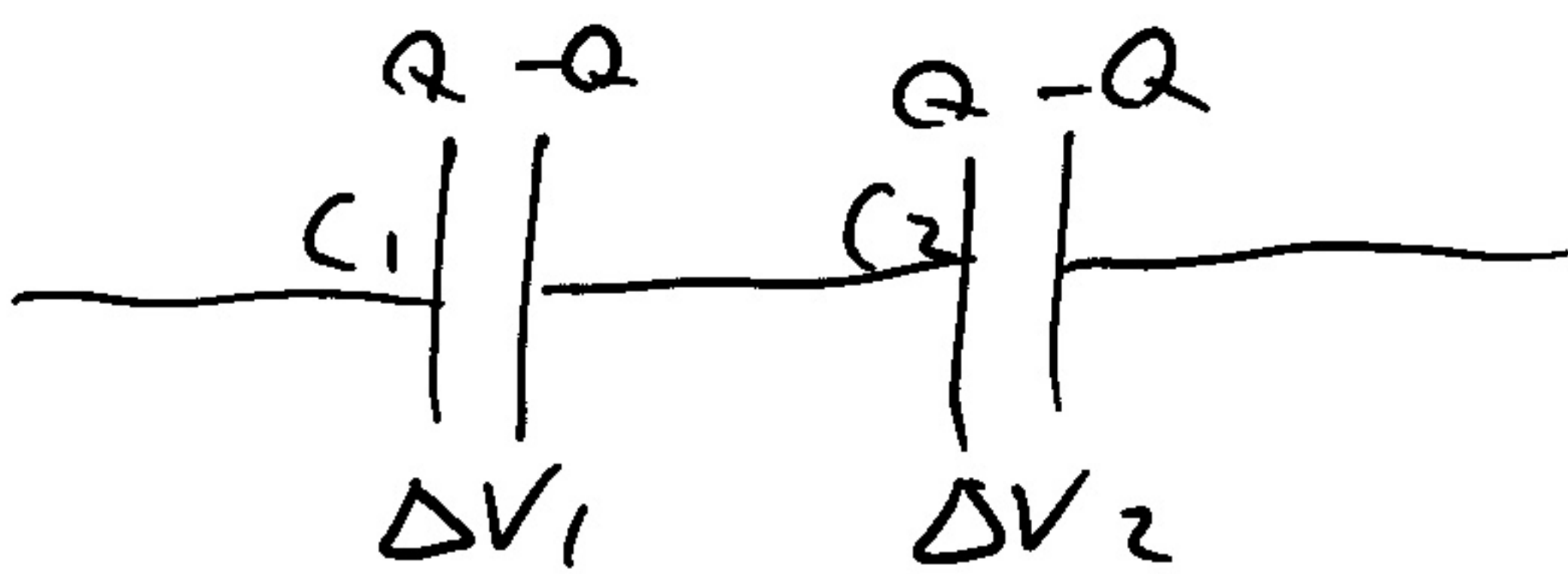

Q same
 ΔV 's add


$$\Delta V_{total} = \Delta V_1 + \Delta V_2$$

$$Q/C_{total} = Q/C_1 + Q/C_2$$


$$C_{total} = \frac{1}{(1/C_1 + 1/C_2)}$$

Concept Check

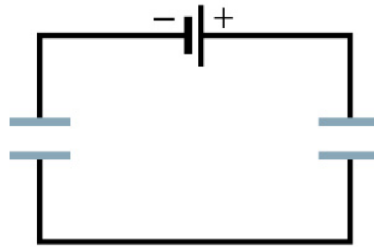
Q16) For each circuit in the figure, are the capacitors connected in series, parallel, or neither?



(a)

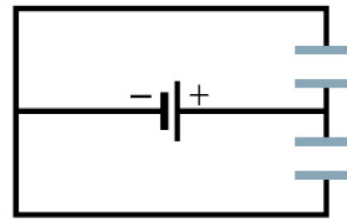

(b)

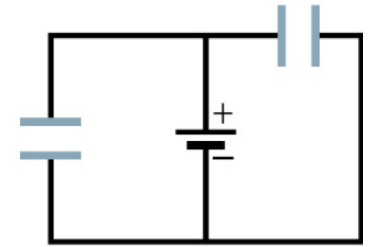


(c)

- 1) (a) series (b) parallel (c) parallel
- 2) (a) series (b) parallel (c) neither
- 3) (a) series (b) neither (c) parallel
- 4) (a) series (b) neither (c) neither
- 5) (a) parallel (b) parallel (c) parallel




How Do You Charge a Capacitor?

1. Apply a voltage across the capacitor
 2. Causes charge to flow to the terminals of the capacitor until it is “fully charged”
- How long does this take?
 - How do we represent the flow of charge?

Charging a Capacitor

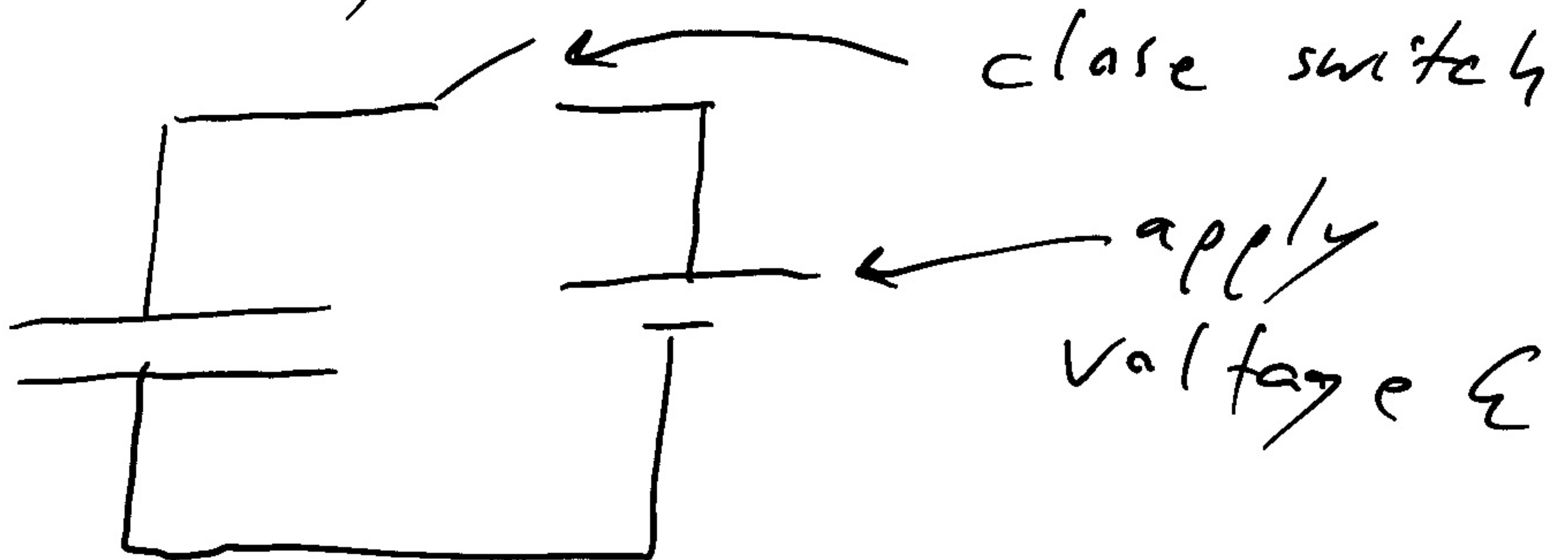

charge flows

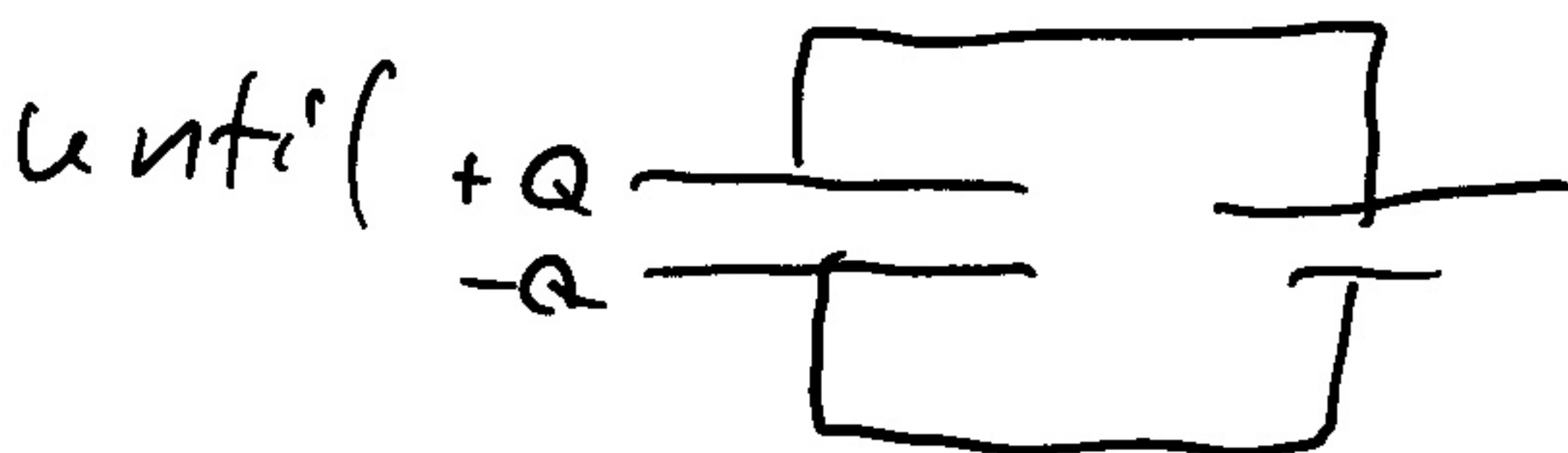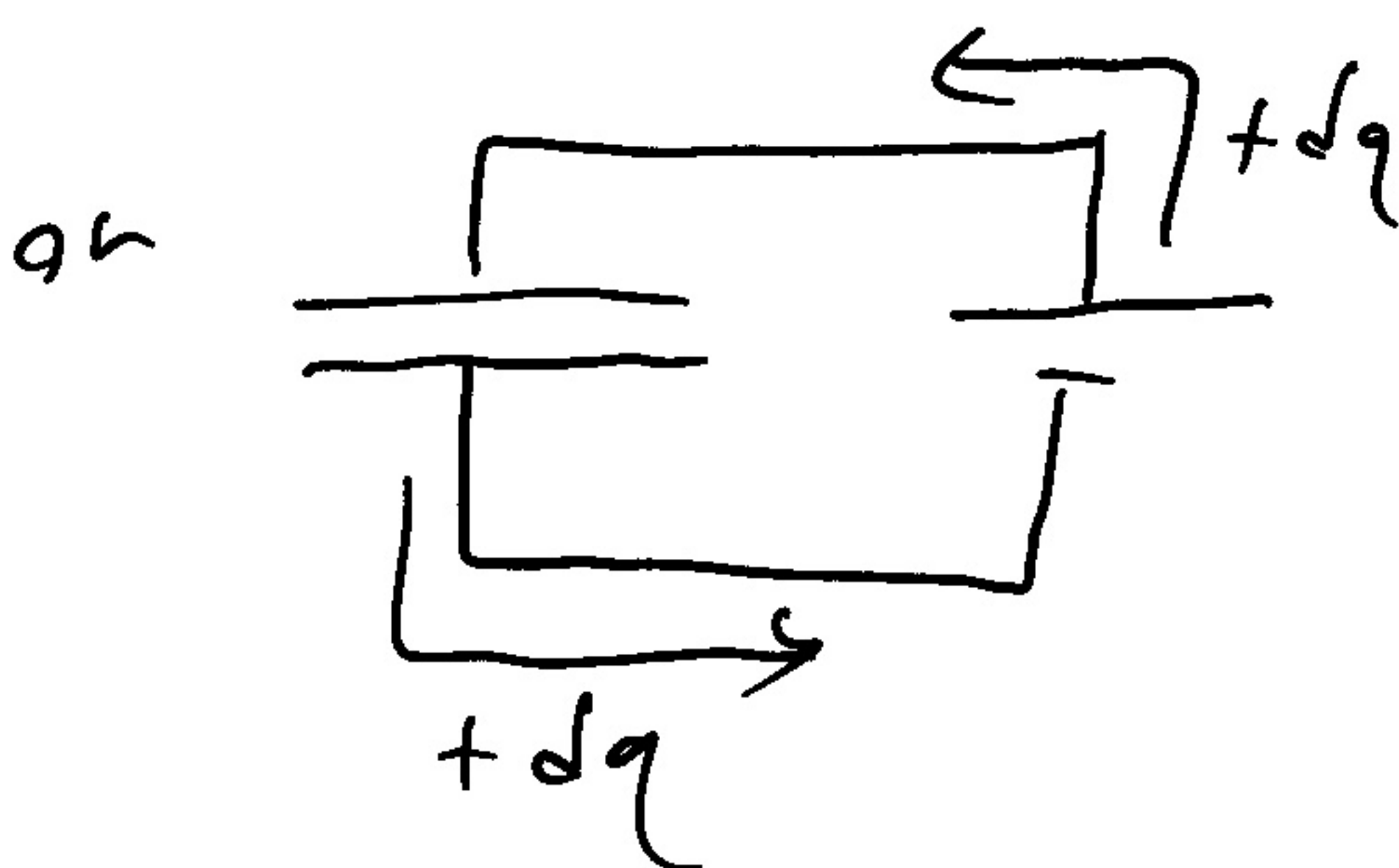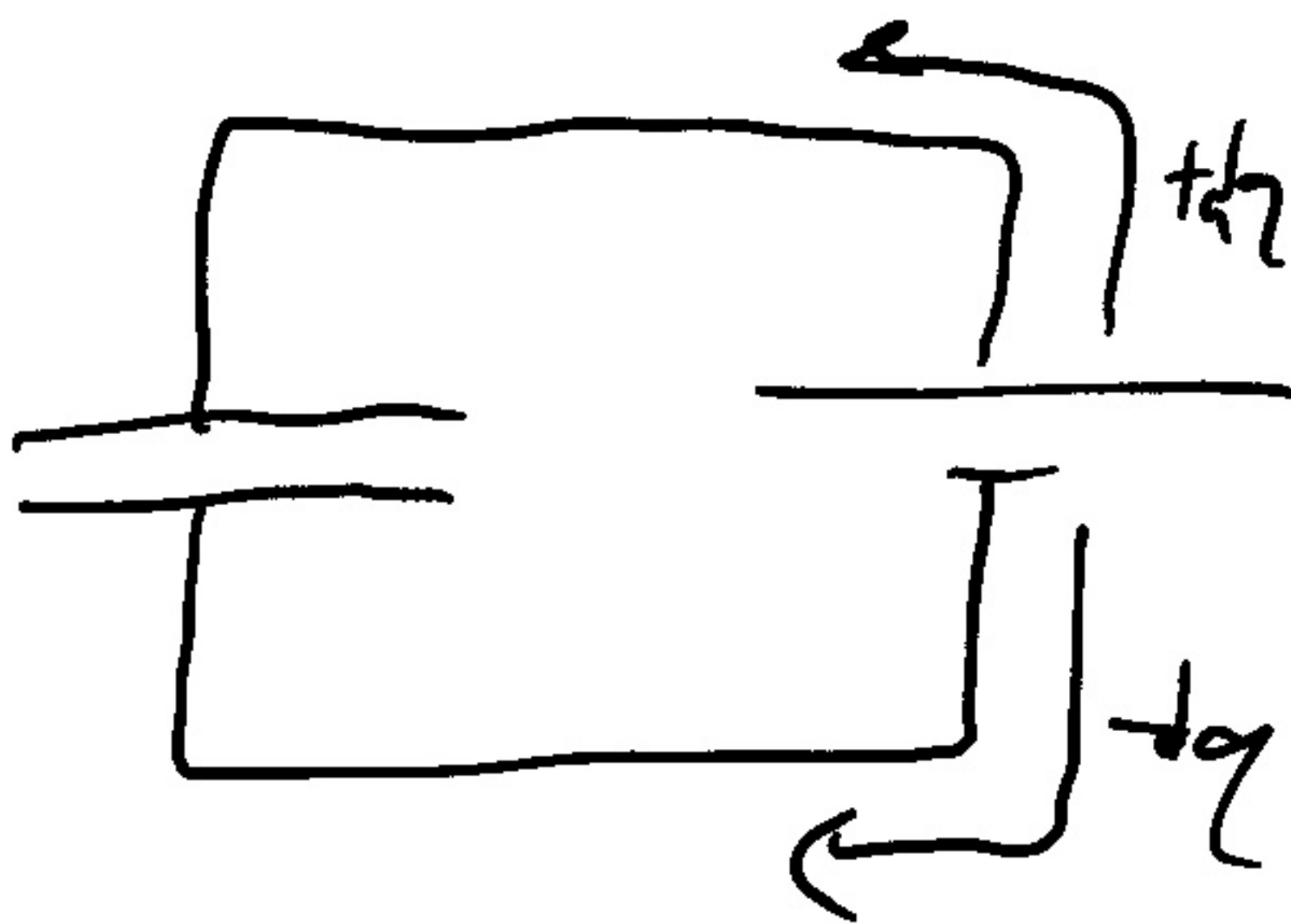

$$Q = CV$$
$$= C\epsilon$$

- Very fast unless C is big.
- Can slow this down with a resistor


Current

Electric Current



$$I = i \equiv \frac{\Delta Q}{\Delta t} = \frac{dQ}{dt} = \text{Rate of flow of net charge past a point}$$

Units [i] = Coulombs/second = Ampere (A) or “Amp”

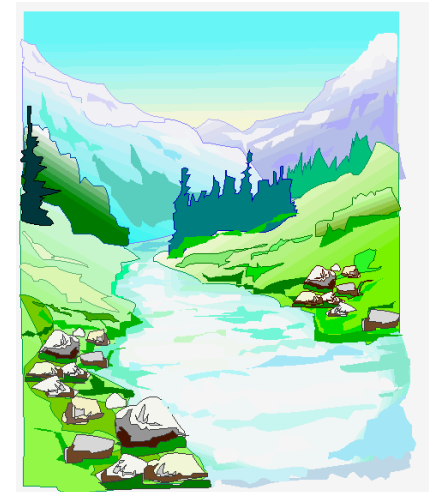- Note that having a finite current does not imply that the net charge at a given point has to change – it just means there is a net charge flowing past that point.



Current Charging Up a Capacitor

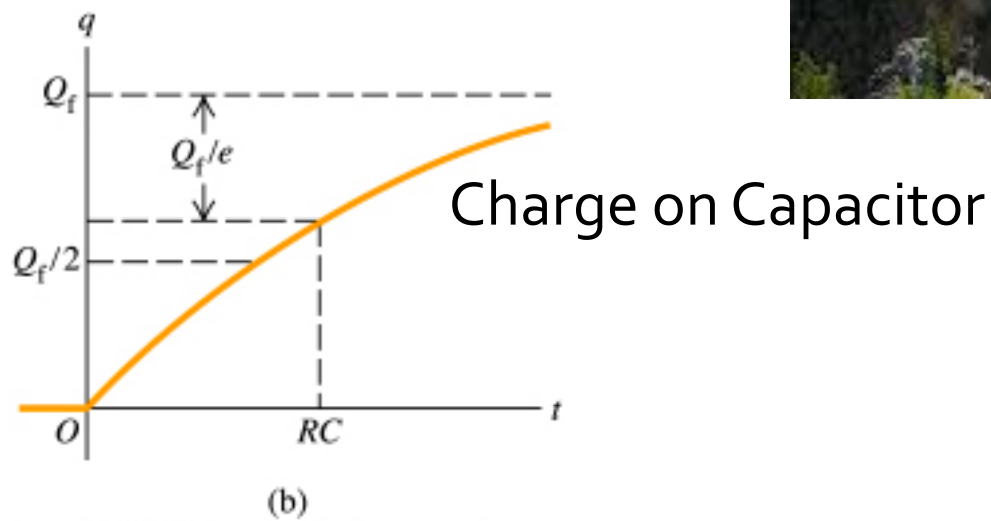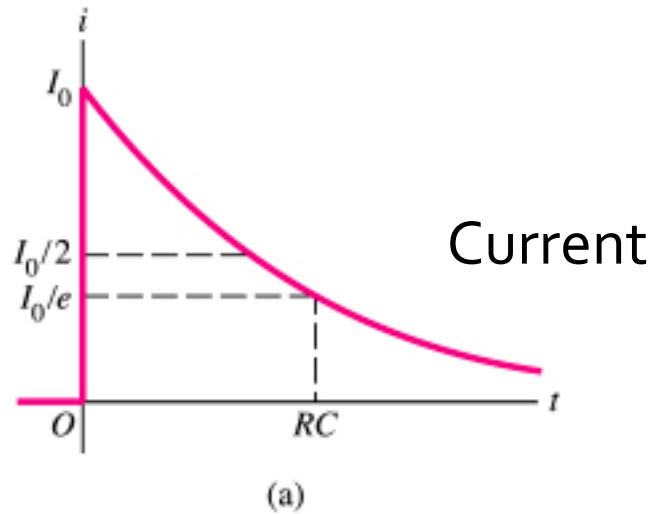


Current Flow

- Current through a capacitor stops once you finish charging it
 - No charge can flow “through” the capacitor – unless it breaks down
- However, there are other electrical components that can support a constant flow of charge through them
 - Example 1: Wire (really easy to make charge flow)
 - Example 2: Resistor (hard to make charge flow)

Concept Check

Q1) The figure below shows four situations in which positive and negative charges move horizontally through a region and gives the rate at which each charge moves. Rank the situations according to the effective current through the regions, greatest first.

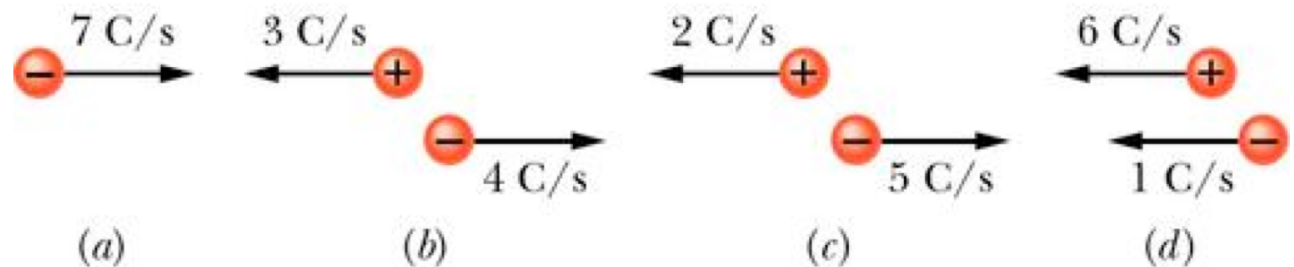- 1) $a = d$, c , b
- 2) a , d , b , c
- 3) $a = b = c$, d
- 4) all tie
- 5) none of the above



Current

Electrons flow in materials, not the protons, so the negative electric charges are moving.



$$\vec{F} = q\vec{E} = -e\vec{E}$$

Electrons go “upstream” against the electric field vector.

Resistors

Resistance R of a material

$$R \equiv \frac{V}{i} = \text{constant}$$


Definition of R

“Ohm’s Law”

$$V = iR$$


This is not really a physical law.
It is true for perfectly Ohmic materials.

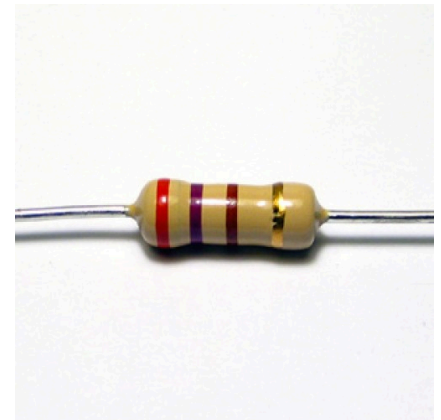Resistance has units of Ohms = Ω = Volts/Amp




Resistor Analogy

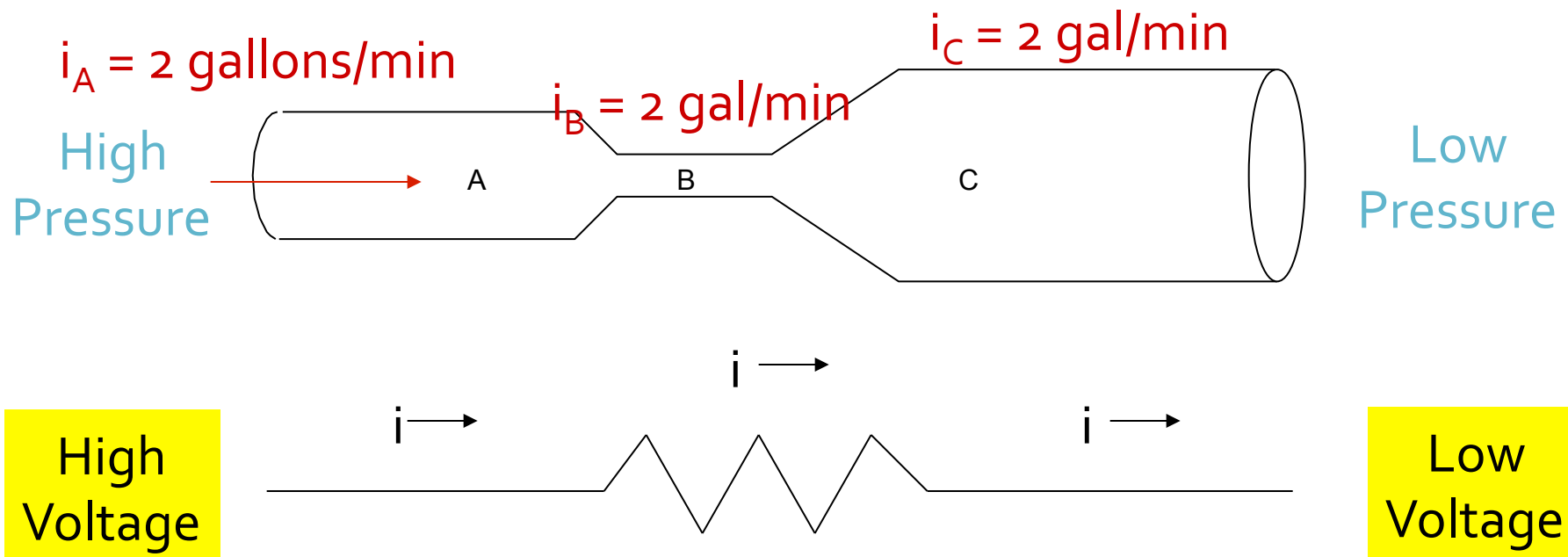
Flow of electrons in wire or resistor is like flow of water in a full pipe (no bubbles or leaks).



Resistor Analogy: Version 2

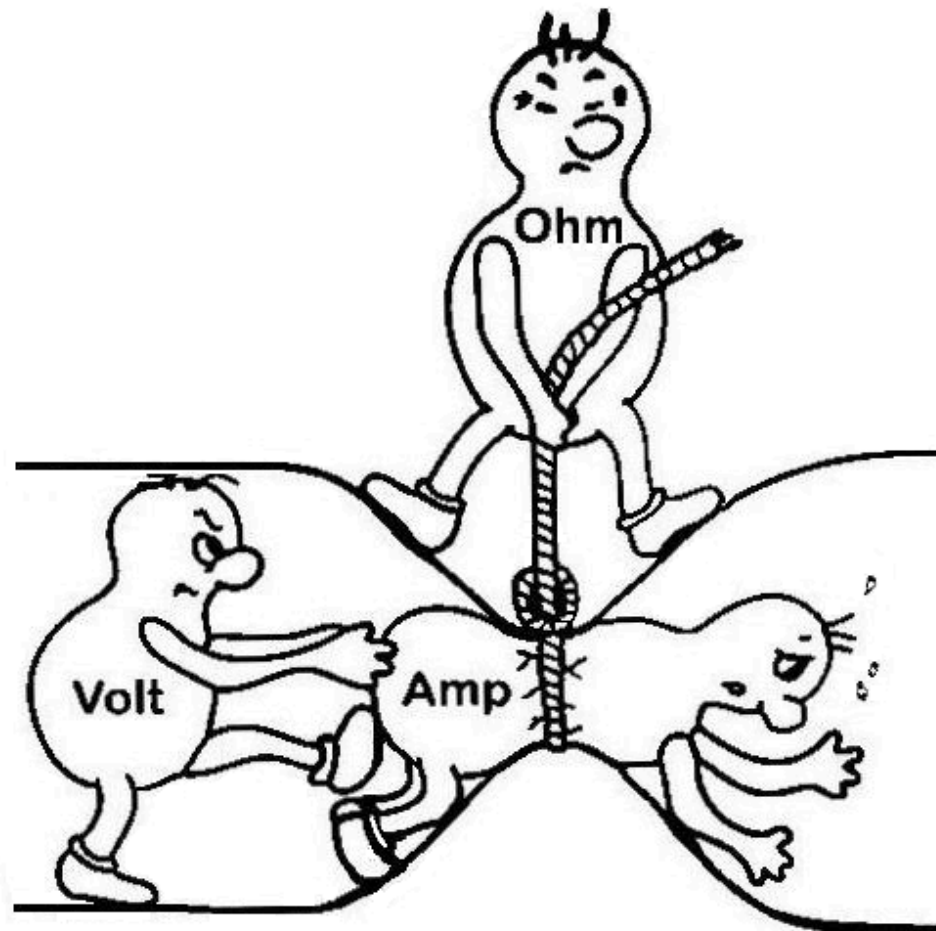

Concept Check

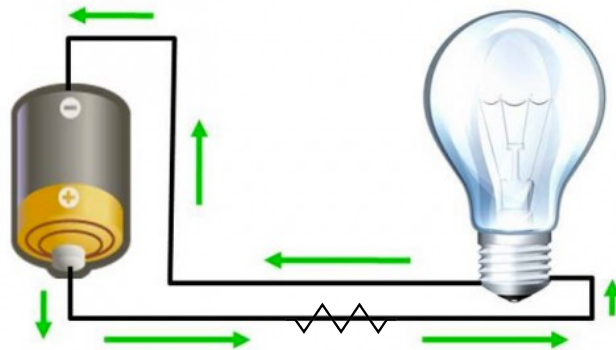

What if I put a resistor in series between the battery and the light bulb?

Does the light bulb:

- A. Get brighter
- B. Get dimmer
- C. Stay the same
- D. Go out
- E. Blow Up!