

Physics II: 1702

Gravity, Electricity, & Magnetism

Professor Jasper Halekas

Van Allen 70 [Clicker Channel #18]


MWF 11:30-12:30 Lecture, Th 12:30-1:30 Discussion

Current

Electric Current

$$I = i \equiv \frac{\Delta Q}{\Delta t} = \frac{dQ}{dt} = \text{Rate of flow of net charge past a point}$$

Current = flow of charge

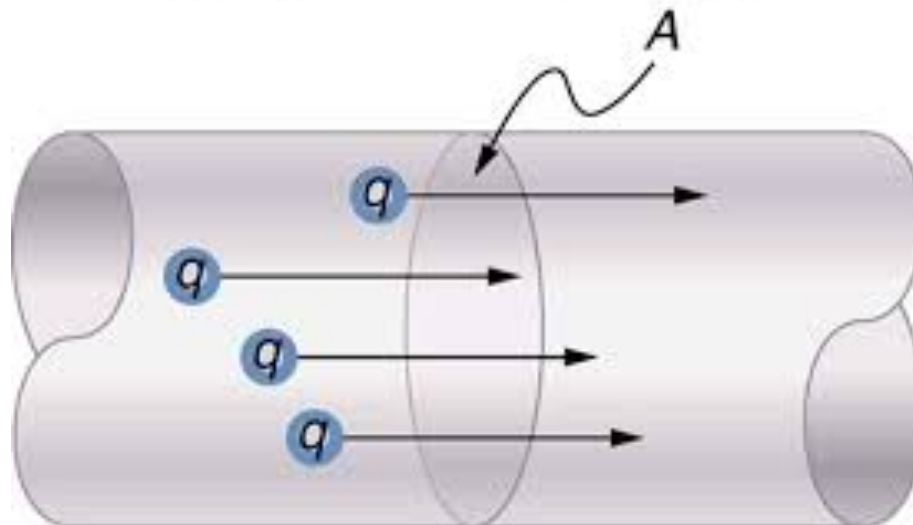

Resistors and Ohm's Law


Resistance R of a material

$$R \equiv \frac{V}{i} = \text{constant (for Ohmic materials)}$$

Definition of R


“Ohm's Law”

$$V = iR$$

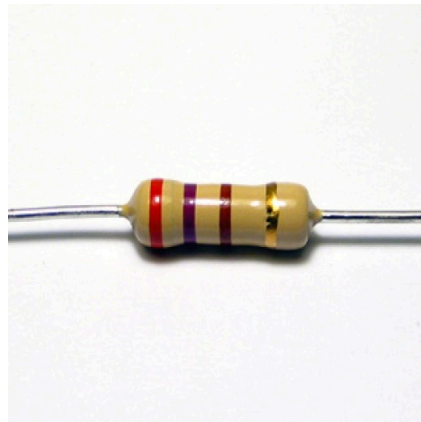

Current Flow in Circuits

Junction Rule

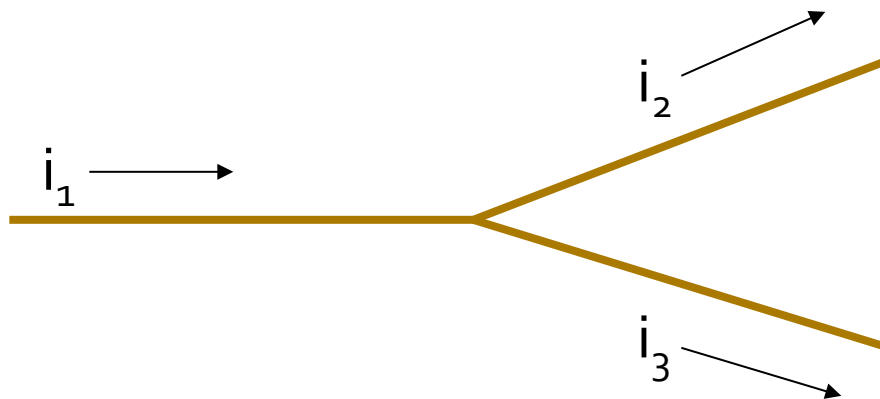

$$i_1 = i_2 + i_3$$

In a steady state, must have $i_{(in)} = i_{(out)}$ at any junction, otherwise charge is building up somewhere, which cannot happen in steady state [Capacitors charging up are non-steady-state].

Current Density

Current Density J

$$\vec{J} = \frac{\vec{i}}{A} = \frac{\text{current}}{\text{area}}$$

J is caused by E, the electric field. In fact,

$$\vec{J} = \frac{1}{\rho} \vec{E} = \sigma \vec{E}$$


Conductivity is the inverse of Resistivity.

Resistivity

Material		Resistivity (Ohm-meter)
Aluminum	Al	2.62×10^{-8}
Copper	Cu	1.72×10^{-8}
Gold	Au	2.44×10^{-8}
Iron	Fe	9.71×10^{-8}
Lead	Pb	21.9×10^{-8}
Mercury	Hg	95.8×10^{-8}
Nickel	Ni	6.9×10^{-8}
Platinum	Pt	10.5×10^{-8}
Silver	Ag	1.62×10^{-8}
Tungsten	W	5.48×10^{-8}
Carbon		$[3-60] \times 10^{-5}$
Glass		$[1-10000] \times 10^9$
Hard Rubber		$[1-100] \times 10^{13}$

Concept Check

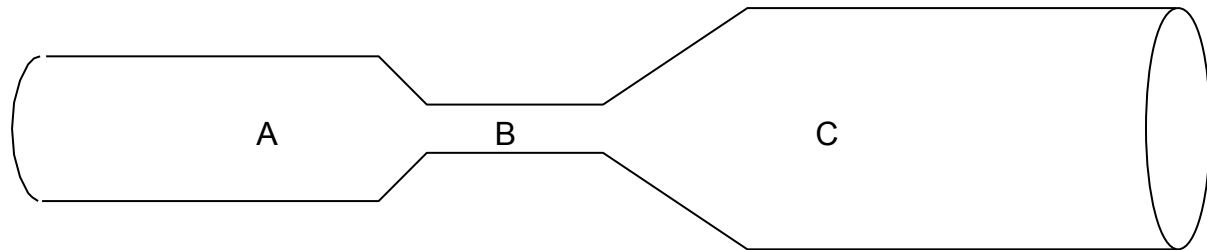A copper cylinder is machined to have the following shape. The ends are connected to a battery so that a current flows through the copper.




Which region A, B, or C has the greatest magnitude current density J ?

- A B C D) all three have the same J .

Region B has the largest current density $J = I/A$. All 3 regions have the same current I , so the region with the smallest A has the largest J .

Square wire

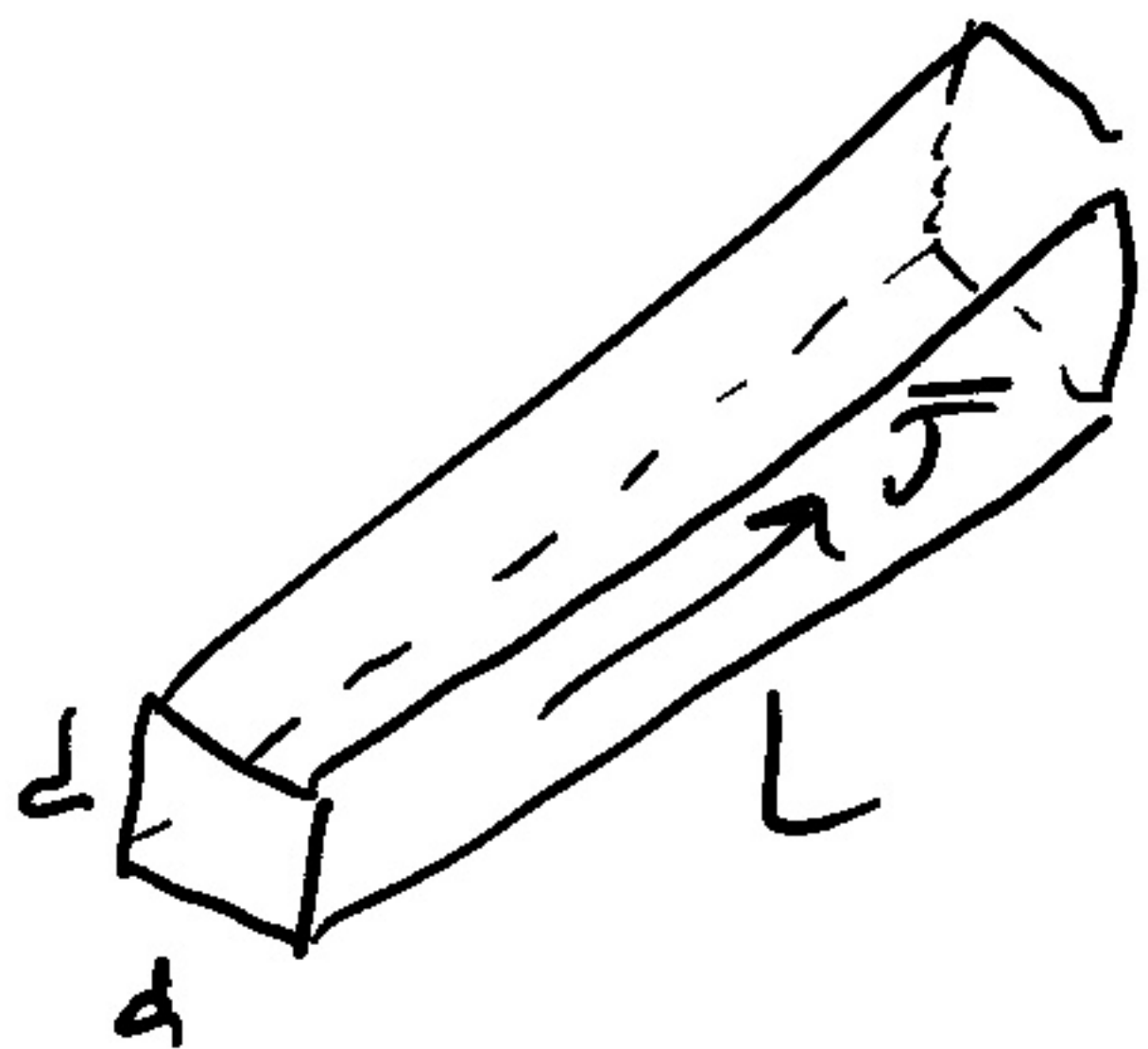

constant current density \vec{J}

$$I = \int \vec{J} \cdot d\vec{A}$$

w/ $d\vec{A}$ the cross-sectional area of wire element

$$= \int J dA \quad \text{since } \vec{J} \parallel d\vec{A}$$

$$= JA$$

$$= Jd^2$$

$$\Delta V = - \int \vec{E} \cdot d\vec{x}$$

$$= -EL$$

$$|\Delta V| = IR \quad \text{By Ohm's Law}$$

$$\Rightarrow EL = Jd^2R$$

$$\Rightarrow E/J = Rd^2/L$$


$$\equiv \rho$$

$$\Rightarrow R = \rho L/A$$

Resistance and Resistivity

Resistance R of a piece of conductor depends on

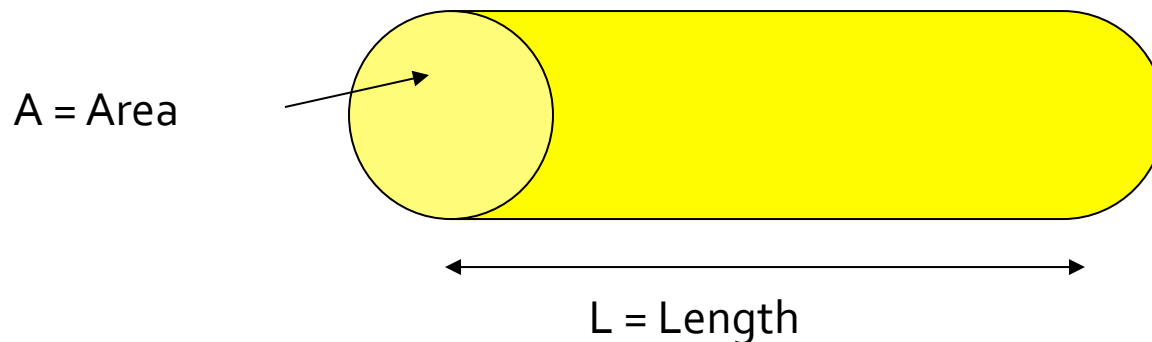- 1) Composition or Material
- 2) Shape and Dimensions



$$R = \rho \frac{L}{A}$$

Where ρ is resistivity – measure of internal friction; dependent on material composition.


Motivating Resistance

- The longer a resistor is, the longer distance the current has to flow through it, and the more it is “slowed down”
- The smaller the cross sectional area of a resistor, the less easily current can flow through it
- Thus, both lengthening and shrinking the cross-sectional area increase the resistance

Concept Check

Two cylindrical resistors are made of the same material (same resistivity ρ). Resistor 2 is twice as long and has twice the diameter of resistor 1. What is the ratio $\frac{R_2}{R_1}$?

- 1) 2
- 2) 4
- 3) 1/2
- 4) 1/4
- 5) 1

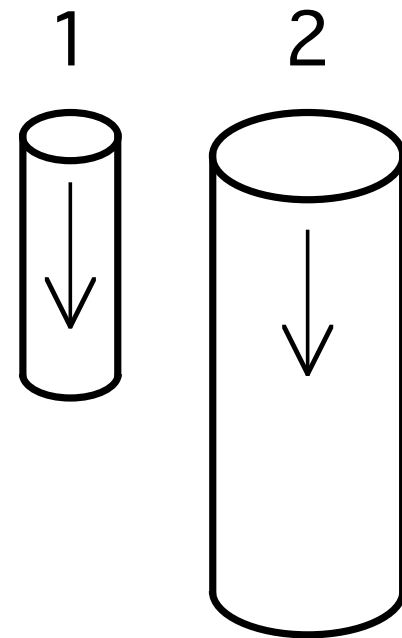


- Recall capacitance addition

$$C_{eq} = C_1 + C_2 \quad (\text{parallel})$$

$$1/C_{eq} = 1/C_1 + 1/C_2 \quad (\text{series})$$

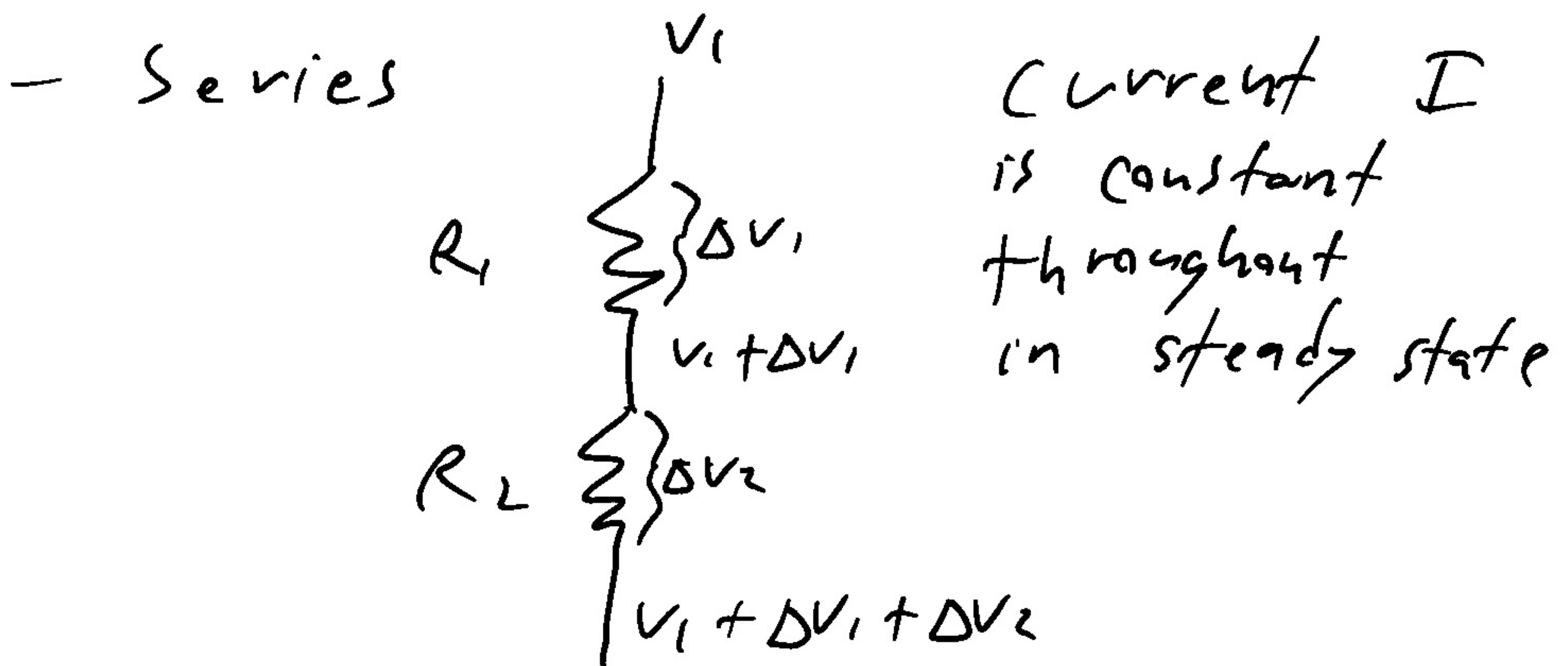- Given resistances different geometric dependence and relationship to Q, V you might guess different addition formulae




$$\Delta V_{tot} = \Delta V_1 + \Delta V_2 = I R_{tot}$$

$$= I R_1 + I R_2$$

$$\Rightarrow R_{tot} = R_1 + R_2$$

Adding resistance in series reduces current, since more energy loss. This is why adding resistance in series eventually turned off our light bulb.

Parallel

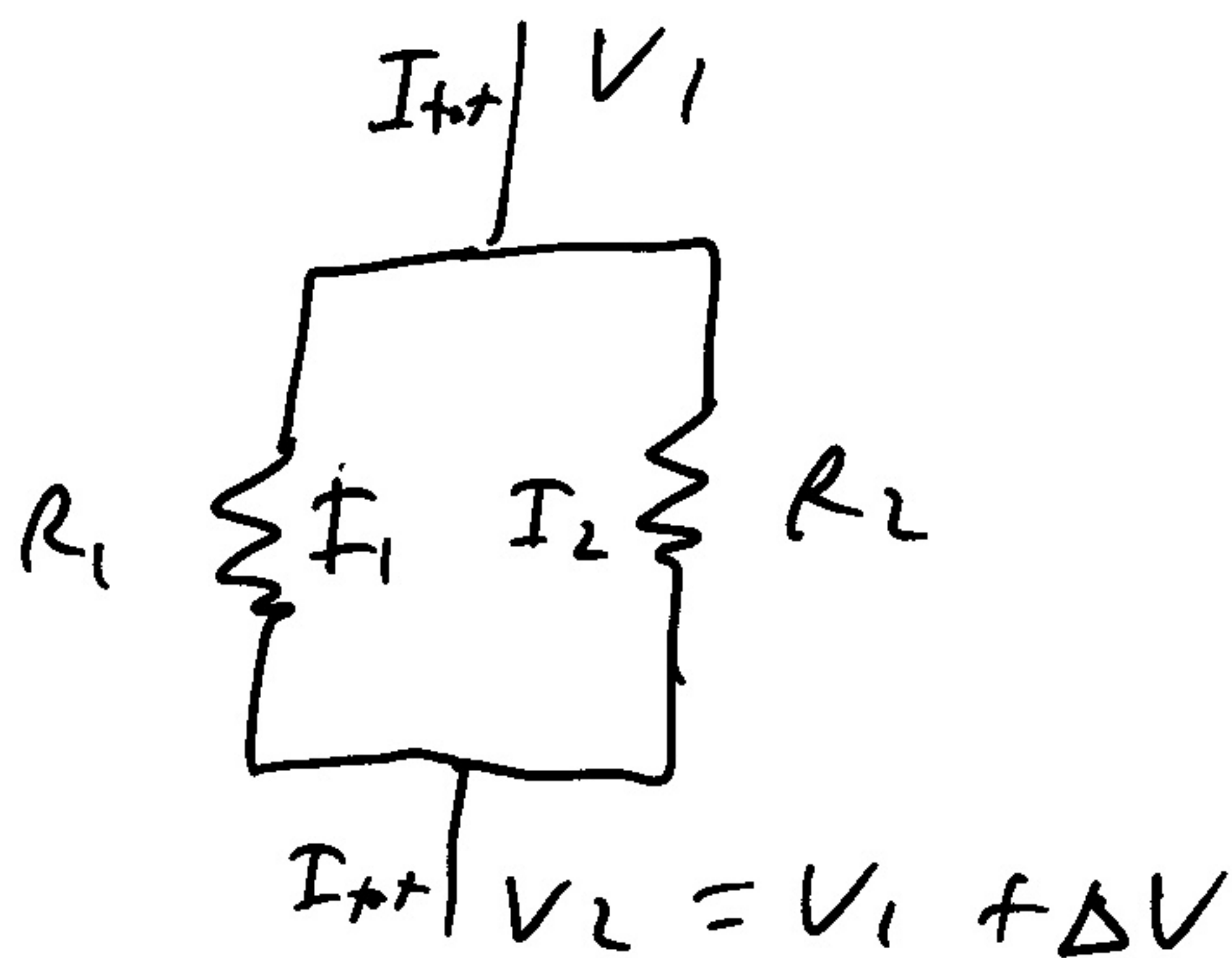

- voltage drop same, but current splits

$$\Delta V_1 = \Delta V_2 = \Delta V = I_1 R_1 = I_2 R_2$$

Junction Rule

$$I_{tot} = I_1 + I_2$$


$$\Rightarrow \Delta V / R_{total} = \Delta V / R_1 + \Delta V / R_2$$

$$\text{or } 1 / R_{total} = 1 / R_1 + 1 / R_2$$

$$\text{or } R_{total} = 1 / (1 / R_1 + 1 / R_2)$$


- series/parallel rules for resistors are inverted from those for capacitors

Series and Parallel Resistors

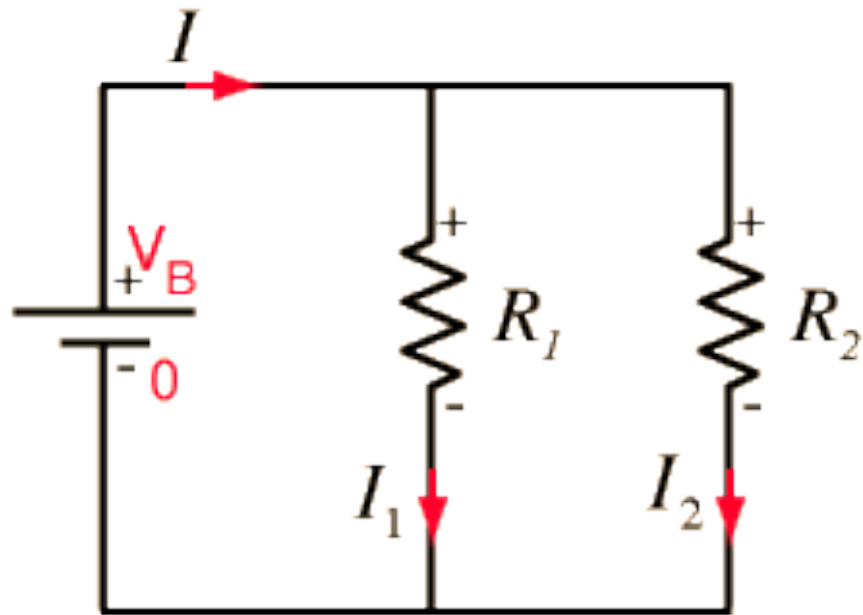

Parallel resistors
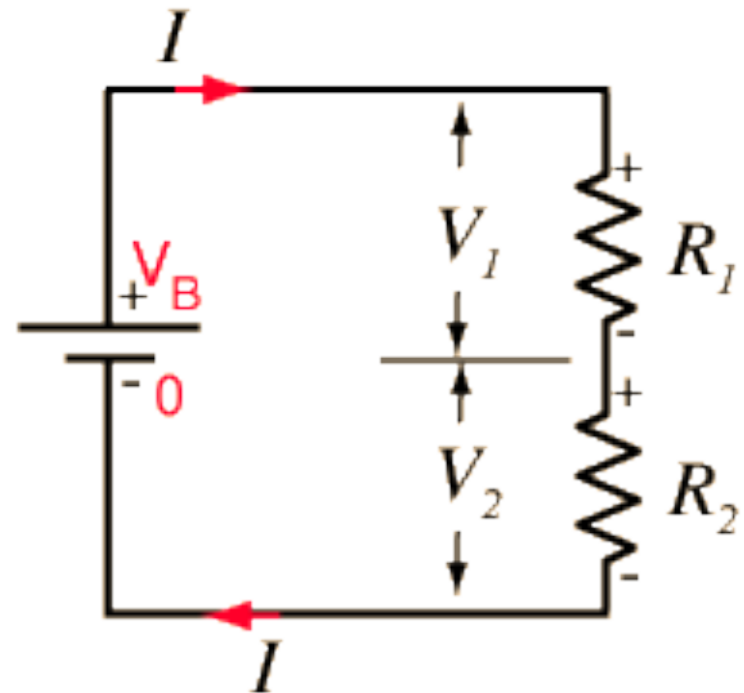
$$\frac{1}{R_{\text{equivalent}}} = \frac{1}{R_1} + \frac{1}{R_2}$$



Series resistors

$$R_{\text{equivalent}} = R_1 + R_2$$

Capacitance vs. Resistance

- Both material & geometrical properties
 - C proportional to A, inversely proportional to d
 - R proportional to L, inversely proportional to A
- $V = IR$ across resistor
- $V = Q/C$ across capacitor