

Physics II: 1702

Gravity, Electricity, & Magnetism


Professor Jasper Halekas

Van Allen 70 [Clicker Channel #18]

MWF 11:30-12:30 Lecture, Th 12:30-1:30 Discussion

Circuit Components

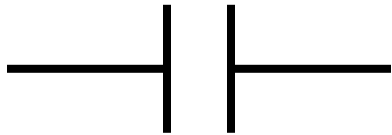Quick Overview of Electric Circuit Components.



Capacitor – stores charge and potential energy. $\Delta V = Q/C$.




Battery – generates a constant electrical potential difference (ΔV) across it.



Resistor – resists flow of charge due to scattering; dissipates energy. $\Delta V = IR$.

Power Dissipation

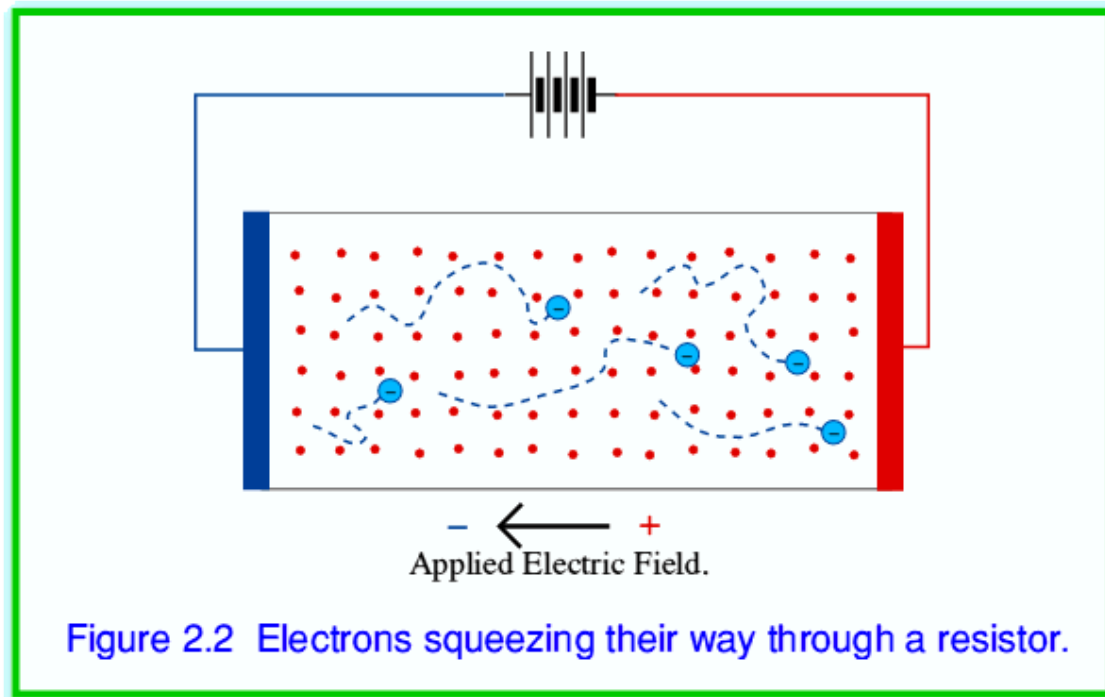


A circuit diagram showing a resistor R with a voltage V across it and a current I flowing through it. The voltage V is indicated by two red arrows pointing outwards from the resistor. The current I is indicated by a green arrow pointing downwards through the resistor.

$$P = VI = \frac{V^2}{R} = I^2 R$$

Junction Rule

Junction Rule

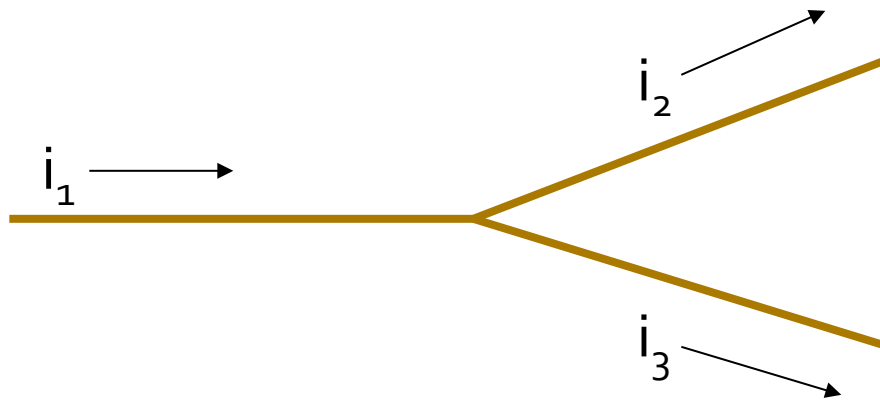

$$i_1 = i_2 + i_3$$

In a steady state, must have $i_{(in)} = i_{(out)}$ at any junction, otherwise charge is building up somewhere, which cannot happen in steady state [Capacitors charging up are non-steady-state].

Loop Rule

- LOOP RULE: The algebraic sum of the changes in potential encountered in a complete traversal of any loop of a circuit must be zero.
 - These changes in potential include those across an EMF device, and those across any electrical components [resistors, capacitors, etc]


$$\sum_{\text{loop}} \Delta V_{\text{rises}} = \sum_{\text{loop}} \Delta V_{\text{drops}}$$


“Conservation of Energy
(per Charge)”

Concept Check

Q27) If in the diagram below, $I_1 = 2 \text{ A}$, what is the potential difference between points a and b, and which point is at the higher potential?

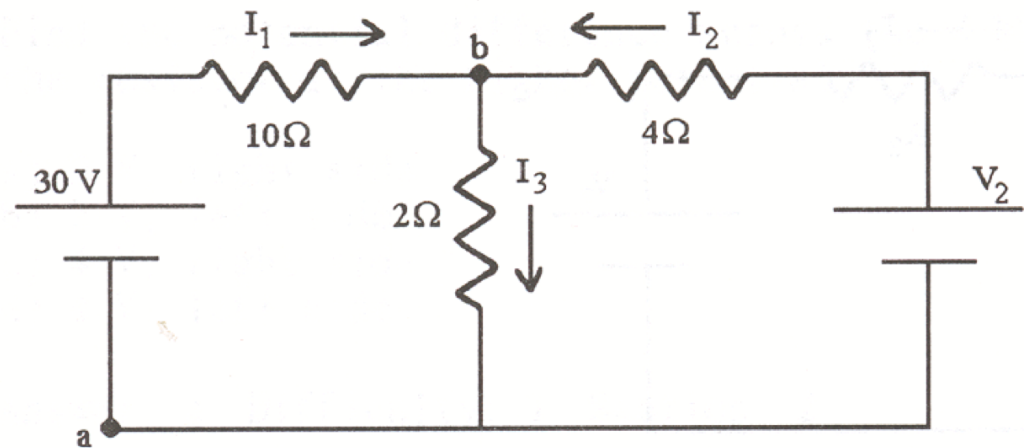- 1) 50 V; point a
- 2) 50 V; point b
- 3) 10 V; point a
- 4) 10 V; point b



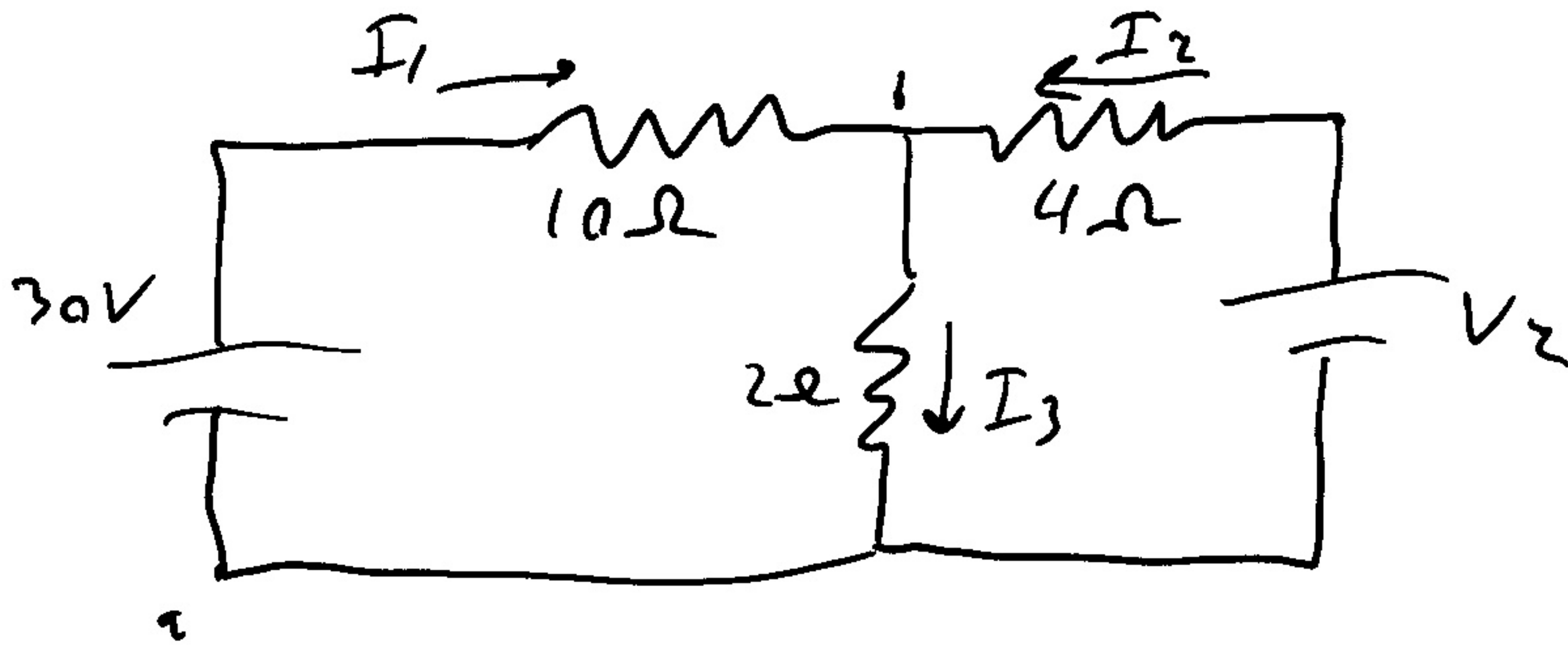

- To answer, use loop rule

$$30 - I_1 \cdot 10 - I_3 \cdot 2 = 0$$

(left loop)

$$\begin{aligned} \text{So } V_b - V_a &= I_3 \cdot 2 \\ &= 30 - I_1 \cdot 10 \\ &= 30 - 2 \cdot 10 \\ &= 10 \text{ V} \end{aligned}$$

- What if we didn't know I₁?

- Look at right loop

and go CCW

$$V_2 - I_2 \cdot 4 - I_3 \cdot 2 = 0$$

- Look @ outer loop and go CW

$$30 - I_1 \cdot 10 + I_2 \cdot 4 - V_2 = 0$$

- solve first two $30 - 10 I_1 = 2 I_3$

$$V_2 - 4 I_2 = 2 I_3$$

subtract to get $30 - 10 I_1 + 4 I_2 - V_2 = 0$

⇒ outer loop gives redundant info.

- If we didn't have I_1 ,

$$30 - 10 I_1 - 2 I_3 = 0$$

$$V_2 - 4 I_2 - 2 I_3 = 0$$

$$I_3 = I_1 + I_2$$

- 3 eqs. in 4 unknowns

- need to know one of

$$I_1, I_2, I_3, V_2$$

Now to solve:

$$I_3 \cdot 2 = 10 \text{ V}$$

$$\Rightarrow I_3 = 5 \text{ A}$$

$$I_3 = I_1 + I_2$$

$$\Rightarrow I_2 = 3 \text{ A}$$

$$V_2 - 4 I_2 - 2 I_3 = 0$$

$$\Rightarrow V_2 = 4 \cdot 3 + 2 \cdot 5$$


$$= 22 \text{ V}$$

$$\text{Check: } 30 - 10 I_1 + 4 I_2 - V_2 = 0 \quad \checkmark$$


$$30 - 20 + 12 - 22 = 0$$

Voltage Drop Across Battery

Critical Sign Convention!

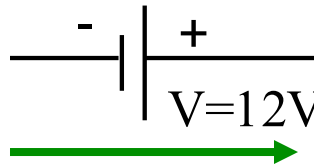

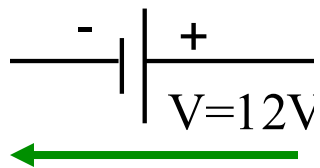If your loop goes through a battery from – to + the Voltage increases (e.g. $\Delta V = +12 V$)



If your loop goes through a battery from + to – the Voltage decreases (e.g. $\Delta V = -12 V$)

Voltage Drop Across Resistors

- If your loop goes in the direction of current, the voltage drop across a resistor is negative
- If your loop goes opposite to the direction of current, the voltage drop across a resistor is positive

Concept Check

Two light bulbs, A and B, are in series, so they carry the same current. Light bulb A is brighter than B.


Which bulb has higher resistance?

A) A

B) B


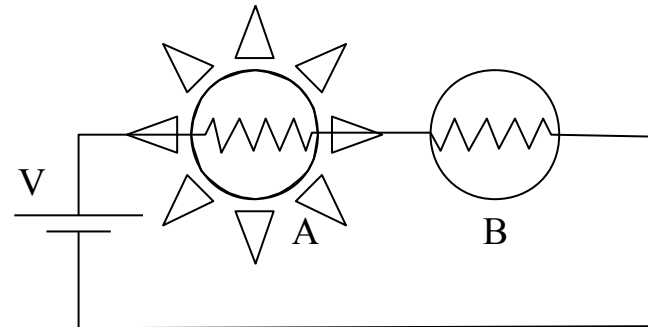
C) Same resistance.

Answer: Bulb A has higher resistance. Since the resistors are in series, they have the same current I . According to $P = I^2 R$, if $I = \text{constant}$, then higher R gives higher P .



Concept Check

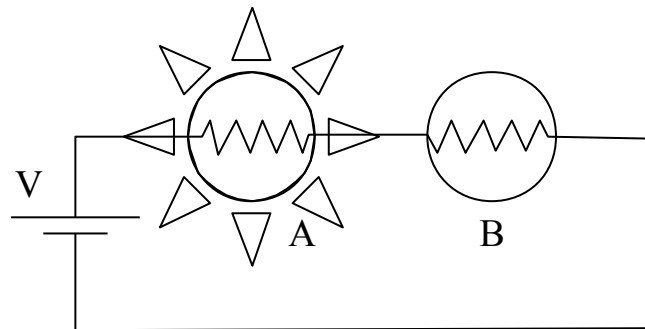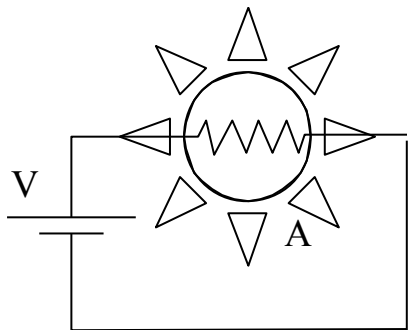
We start with the left circuit with one lightbulb (A). The brightness of the bulb directly reflects the power. If we add a second bulb (B) as shown on the right, what happens to the bulbs?



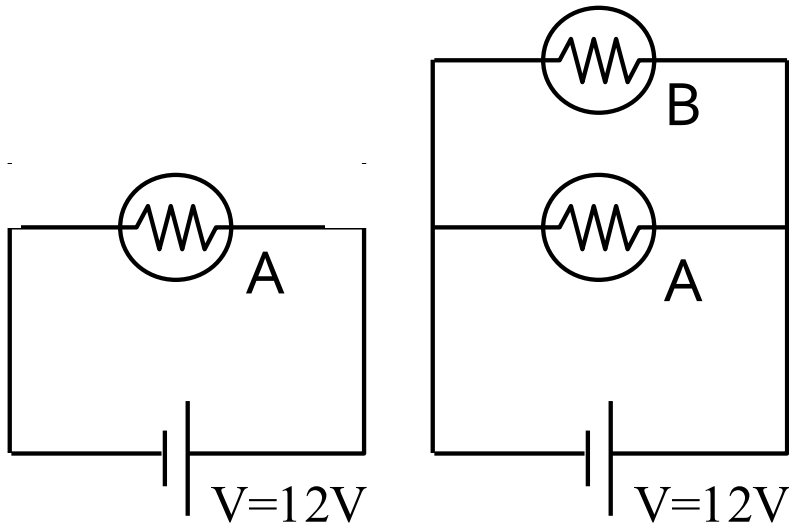- A) Bulb A is equally bright.
- B) Bulb A is dimmer than before**
- C) Bulb A is brighter than before

Concept Check


We start with the left circuit with one lightbulb (A). The brightness of the bulb directly reflects the power. If we add a second bulb (B) as shown on the right, what happens to the bulbs?



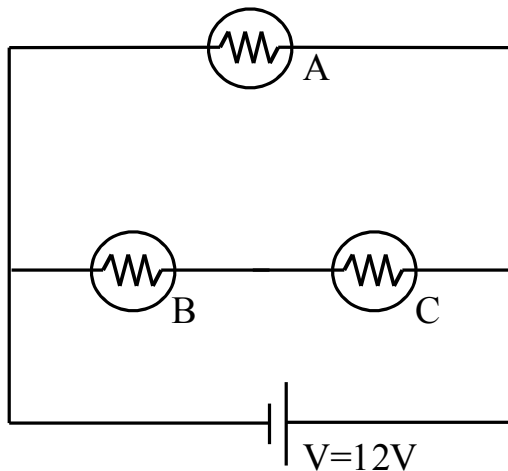- A) Bulb A is equally bright.
- B) Bulb A is dimmer than before
- C) Bulb A is brighter than before

Concept Check

The three light bulbs A, B, and C are identical. How does the brightness of bulbs B and C together compare with the brightness of bulb A?




- A) Total power in B+C = power in A.
- B) Total power in B+C > power in A.
- C) Total power in B+C < power in A.

Answer: Use $P = V^2/R_{\text{tot}}$ For bulbs B and C,
 $R_{\text{tot}} = 2R$.
Total power in B+C < power in A.

Concept Check

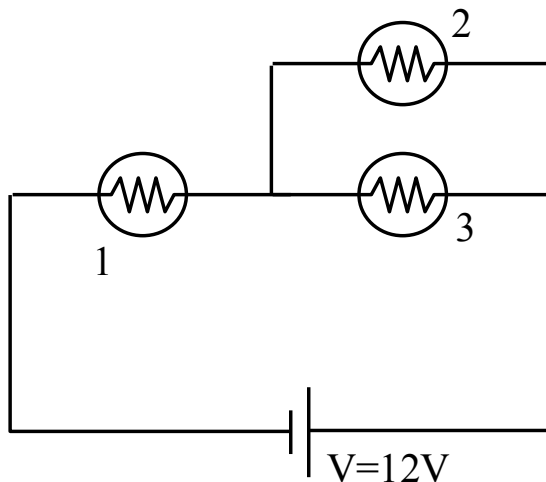In the circuit below, what happens to the brightness of bulb 1, when bulb 2 burns out? (When a bulb burns out, its resistance becomes infinite.)



A) Bulb 1 gets brighter

B) Bulb 1 gets dimmer.

C) It's brightness remains the same.

(Hint: What happens to the current from the battery when bulb 2 burns out.)

Concept Check


A circuit with two batteries is shown below. The directions of the currents have been chosen (guessed) as shown. Which is the correct current equation for this circuit?

A) $I_2 = I_1 + I_3$

B) $I_1 = I_2 + I_3$

C) $I_3 = I_1 + I_2$

D) None of these.

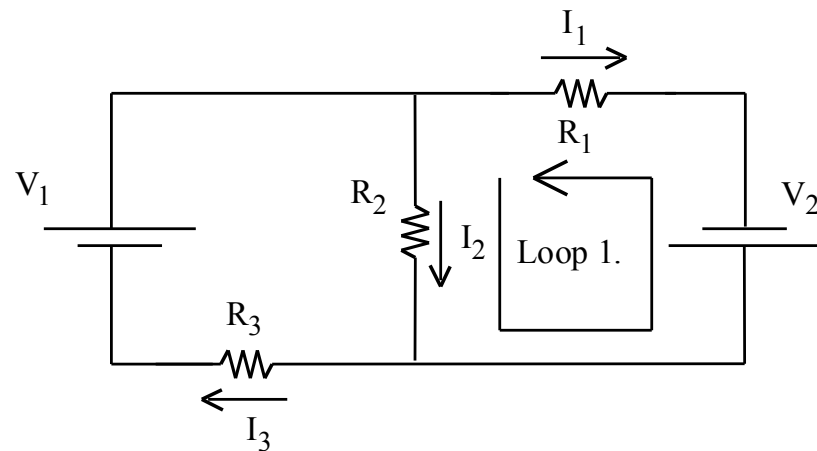

Concept Check

Which equation below is the correct equation for Loop 1?

A) $-V_2 + I_1 R_1 - I_2 R_2 = 0$

B) $V_2 + I_1 R_1 - I_2 R_2 = 0$

C) $-V_2 - I_1 R_1 + I_2 R_2 = 0$

D) $V_2 + I_1 R_1 + I_2 R_2 = 0$

E) None of these.

Answer: $-V_2 + I_1 R_1 - I_2 R_2 = 0$

