

Physics II: 1702

Gravity, Electricity, & Magnetism

Professor Jasper Halekas

Van Allen 70 [Clicker Channel #18]

MWF 11:30-12:30 Lecture, Th 12:30-1:30 Discussion

Last Time's Concept Check


A circuit with two batteries is shown below. The directions of the currents have been chosen (guessed) as shown. Which is the correct current equation for this circuit?

A) $I_2 = I_1 + I_3$

B) $I_1 = I_2 + I_3$

C) $I_3 = I_1 + I_2$

D) None of these.

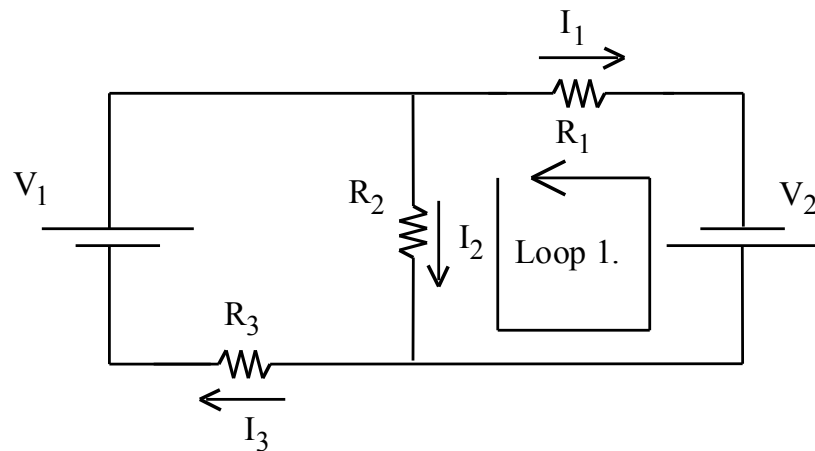

Last Time's Concept Check

Which equation below is the correct equation for Loop 1?

A) $-V_2 + I_1 R_1 - I_2 R_2 = 0$


B) $V_2 + I_1 R_1 - I_2 R_2 = 0$


C) $-V_2 - I_1 R_1 + I_2 R_2 = 0$

D) $V_2 + I_1 R_1 + I_2 R_2 = 0$

E) None of these.

Answer: $-V_2 + I_1 R_1 - I_2 R_2 = 0$

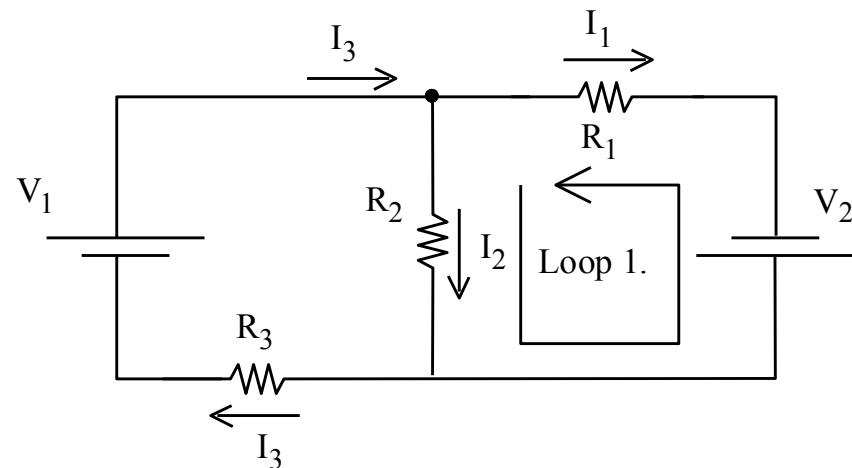

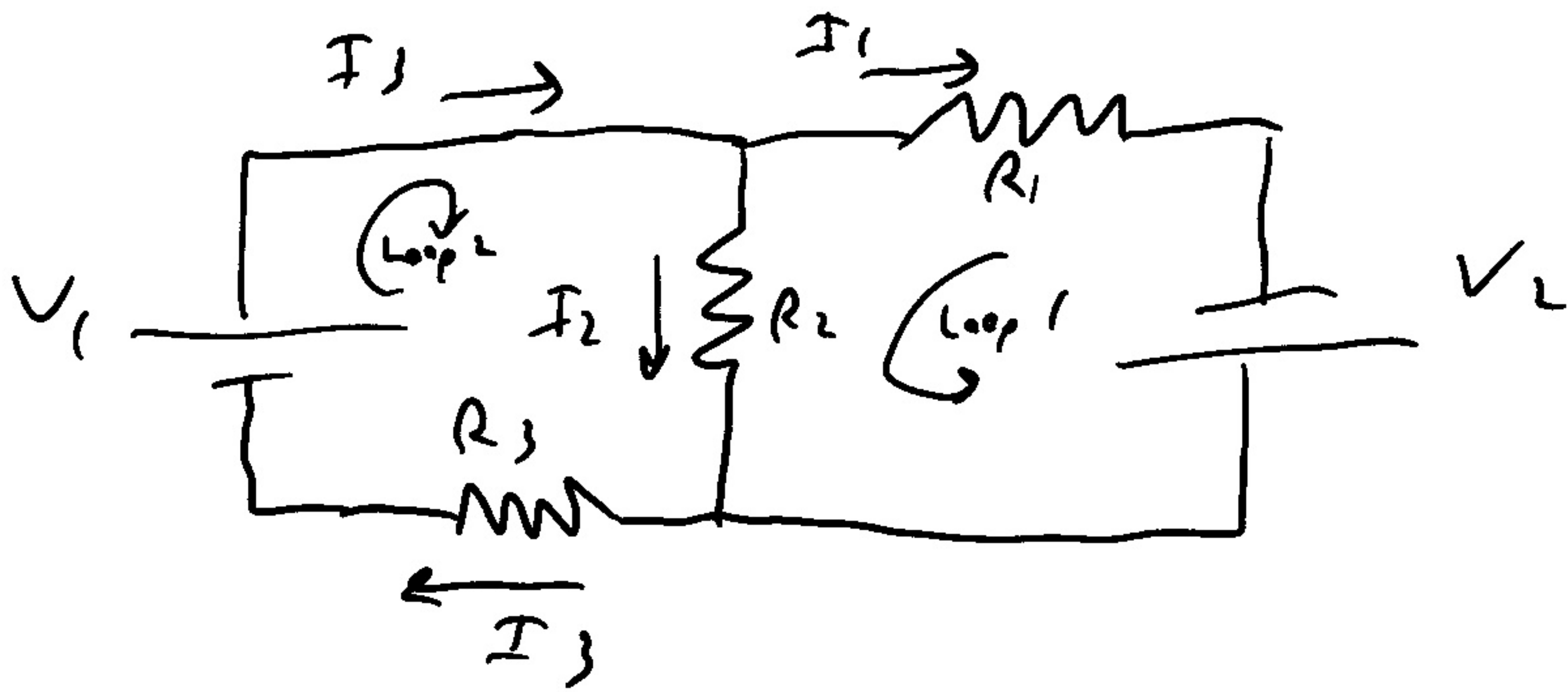

$$-V_2 + I_1 R_1 - I_2 R_2 = 0 \quad \text{Loop 1}$$

$$V_1 - I_2 R_2 - I_3 R_3 = 0 \quad \text{Loop 2}$$

$$I_3 = I_2 + I_1 \quad \text{Junction}$$

- Say $V_1 = 12 \text{ V}$

$$V_2 = 24 \text{ V}$$

$$R_1 = R_2 = R_3 = 1 \Omega$$

$$-24 + I_1 - I_2 = 0$$

$$12 - I_2 - I_3 = 0$$

$$\Rightarrow -24 + I_1 - I_2 = 0$$

$$12 - I_1 - 2I_2 = 0$$

add

$$\hline -12 - I_2 = 0$$

using junction rule

$$\Rightarrow I_2 = -4 \text{ A}$$

- Our guess for current direction was wrong. I_2 actually up! Okay as long as we are consistent.


$$-24 + I_1 - I_2 = 0$$

$$\Rightarrow -24 + I_1 - (-4) = 0$$

$$\Rightarrow I_1 = 20 \text{ A}$$

$$I_3 = I_1 + I_2 = 16 \text{ A}$$


Circuit really looks like

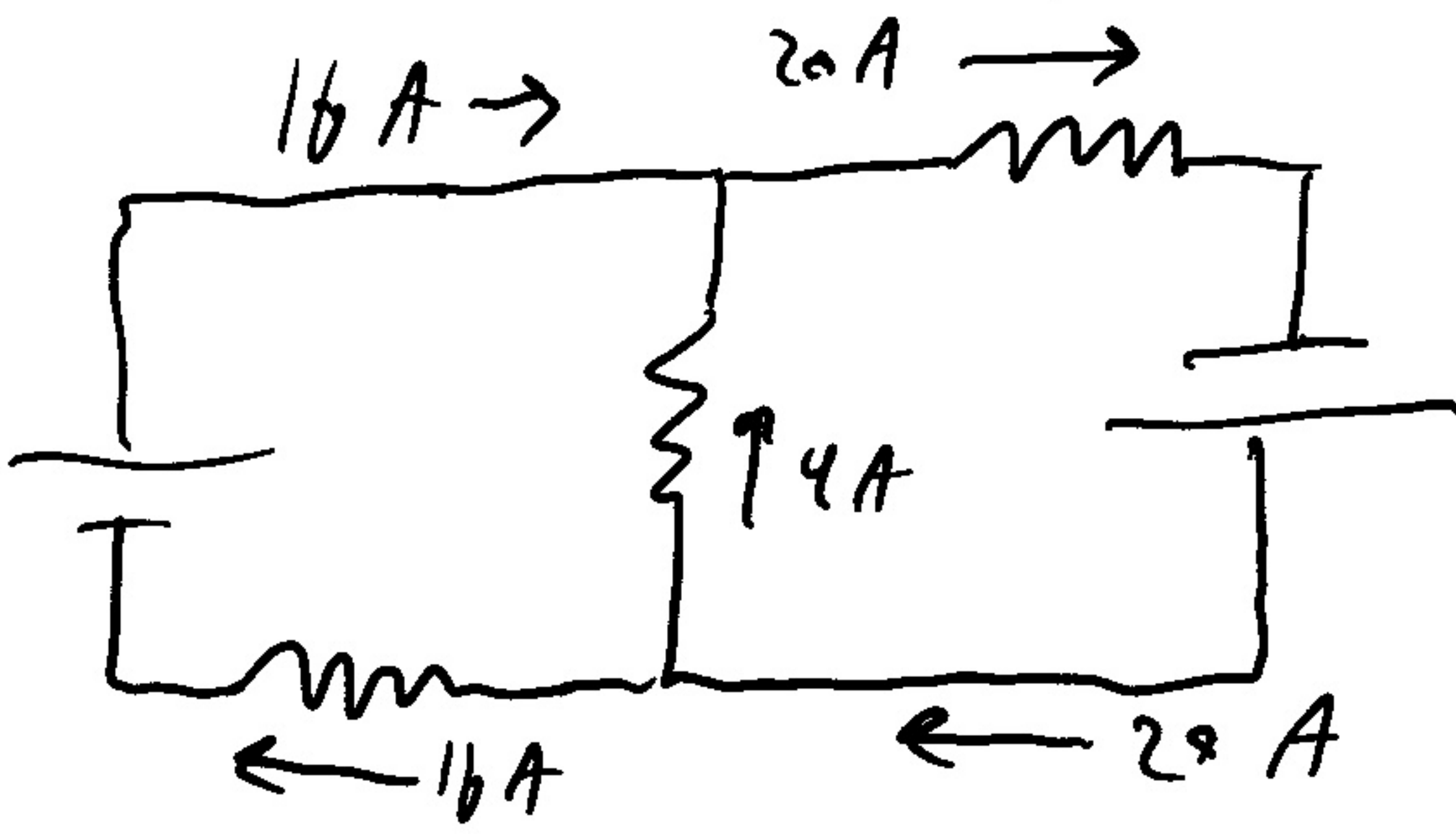

RC Circuits


Now we will discuss circuits with batteries, resistors and capacitors. → “RC Circuits”

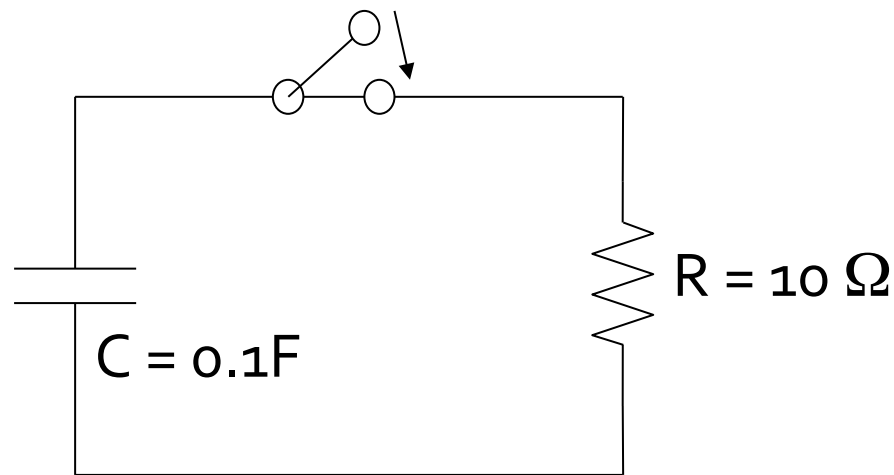Simplest case is just a Capacitor C , charged to a Voltage $V_0 = Q_0/C$, attached to a Resistor R and a switch.




Discharging Capacitor

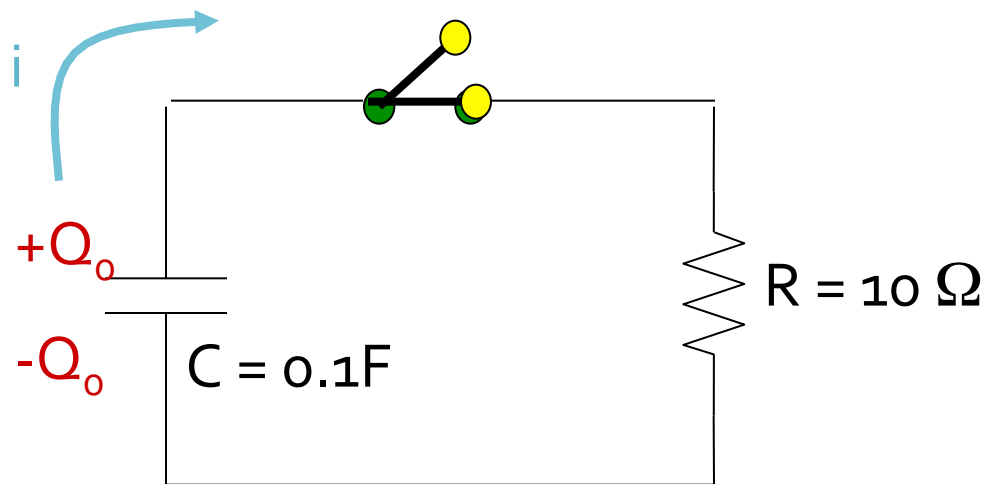Initially one has $+Q_0$ and $-Q_0$ on the Capacitor plates.
Thus, the initial Voltage on the Capacitor $V_0 = Q_0/C$.
What do you think happens when the switch is closed?



Discharging Capacitor

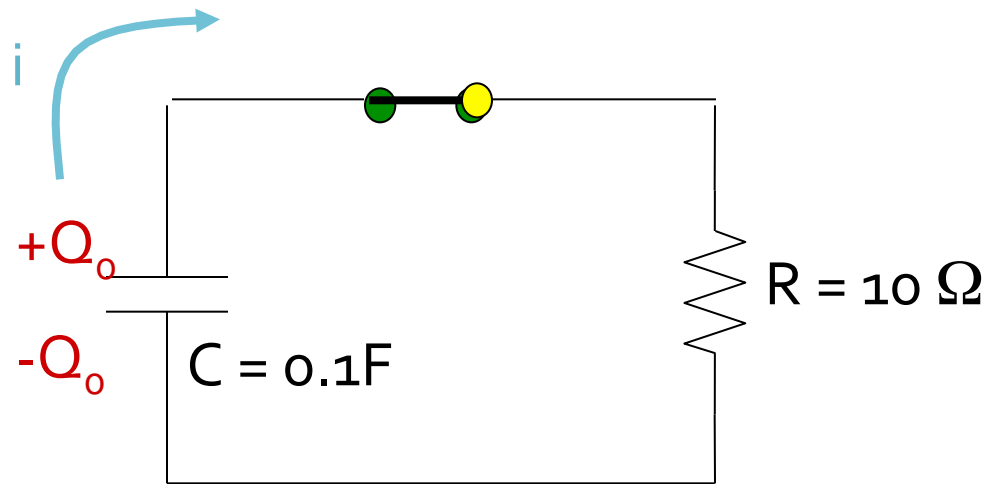Close the switch at $t=0$, then current i starts to flow.




$$\text{At } t=0, \quad i_0 = \frac{V_0}{R}$$

$$\text{Later } i(t) = -\frac{dQ}{dt}$$

* Negative sign since Q is decreasing.

Discharging Capacitor

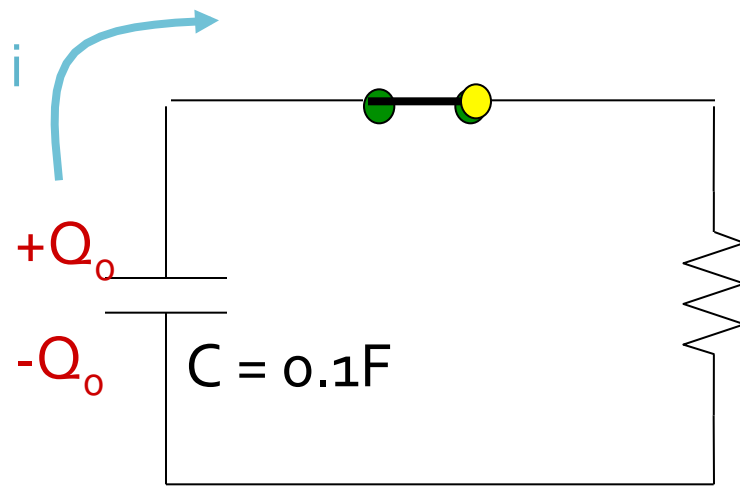

Voltage across C = Voltage across R

$$V_c = V_R$$

$$\frac{Q}{C} = iR = -\frac{dQ}{dt}R$$

$$\frac{dQ}{dt} = -\frac{1}{RC}Q$$

We now need to solve this differential equation.

Discharging Capacitor

Solving the differential equation:

$$\frac{dQ}{dt} = -\frac{1}{RC}Q \quad \longrightarrow \quad Q(t) = Q_0 e^{-t/RC}$$

Check solution by taking the derivative...

$$\frac{dQ}{dt} = Q_0 \left(-\frac{1}{RC} \right) e^{-t/RC} = -\frac{1}{RC}Q$$

Also $Q(t) = Q_0$ at $t=0$.

$$Q(t = 0) = Q_0 e^{-0/RC} = Q_0$$


Discharging Capacitor

Exponential Decay

$$Q(t) = Q_0 e^{-t/RC}$$

After a time $\tau = RC$, Q has dropped by $e^{-1} = 1/e$.

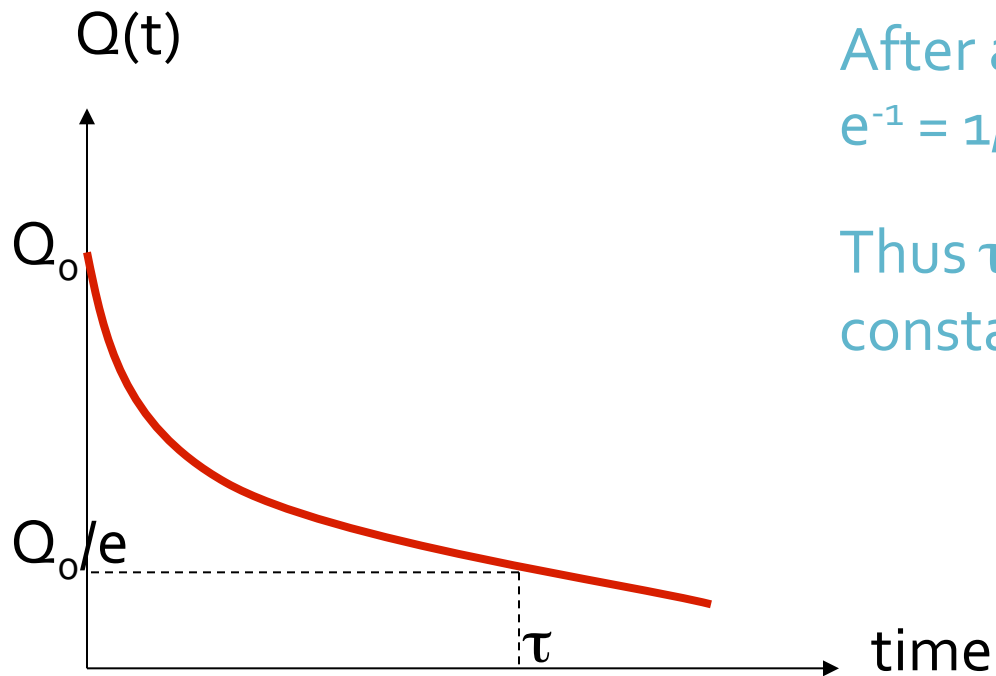Thus $\tau = RC$ is often called the time constant and has units [seconds].




Concept Check

A capacitor with capacitance 0.1F in an RC circuit is initially charged up to an initial voltage of $V_0 = 10\text{V}$ and is then discharged through an $R=10\Omega$ resistor as shown. The switch is closed at time $t=0$. Immediately after the switch is closed, the initial current is $I_0 = V_0 / R = 10\text{V} / 10\Omega$.

What is the current I through the resistor at time $t=2.0\text{ s}$?

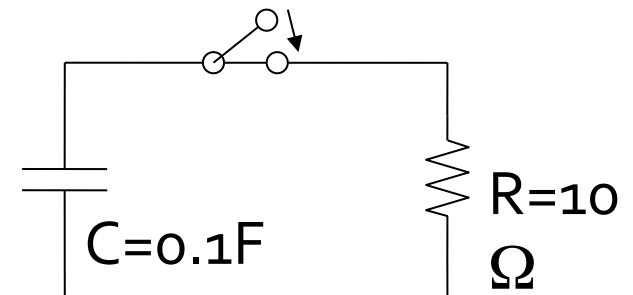- A) 1A
- B) 0.5A
- C) 0.37A
- D) 0.14A
- E) None of these.



Answer: $1/e^2\text{ A} = 0.14\text{A}$. The time constant for this circuit is $RC=(10\Omega)(0.10\text{F}) = 1.0\text{ sec}$. So at time $t=2.0\text{ sec}$, two time constants have passed. After one time constant, the voltage, charge, and current have all decreased by a factor of e . After two time constants, everything has fallen by e^2 . The initial current is 1A . So after two time constants, the current is $1/e^2\text{ A} = 0.135\text{A}$.


Discharging Capacitor

$$\frac{dQ}{dt} = Q_0 \left(-\frac{1}{RC} \right) e^{-t/RC} = -\frac{1}{RC} Q$$

$$|i(t)| = \left| \frac{dQ}{dt} \right| = \left(\frac{Q_0}{RC} \right) e^{-t/RC} = i_0 e^{-t/RC}$$

Thus, the current also falls with the same exponential function.

Energy Dissipation Discharging

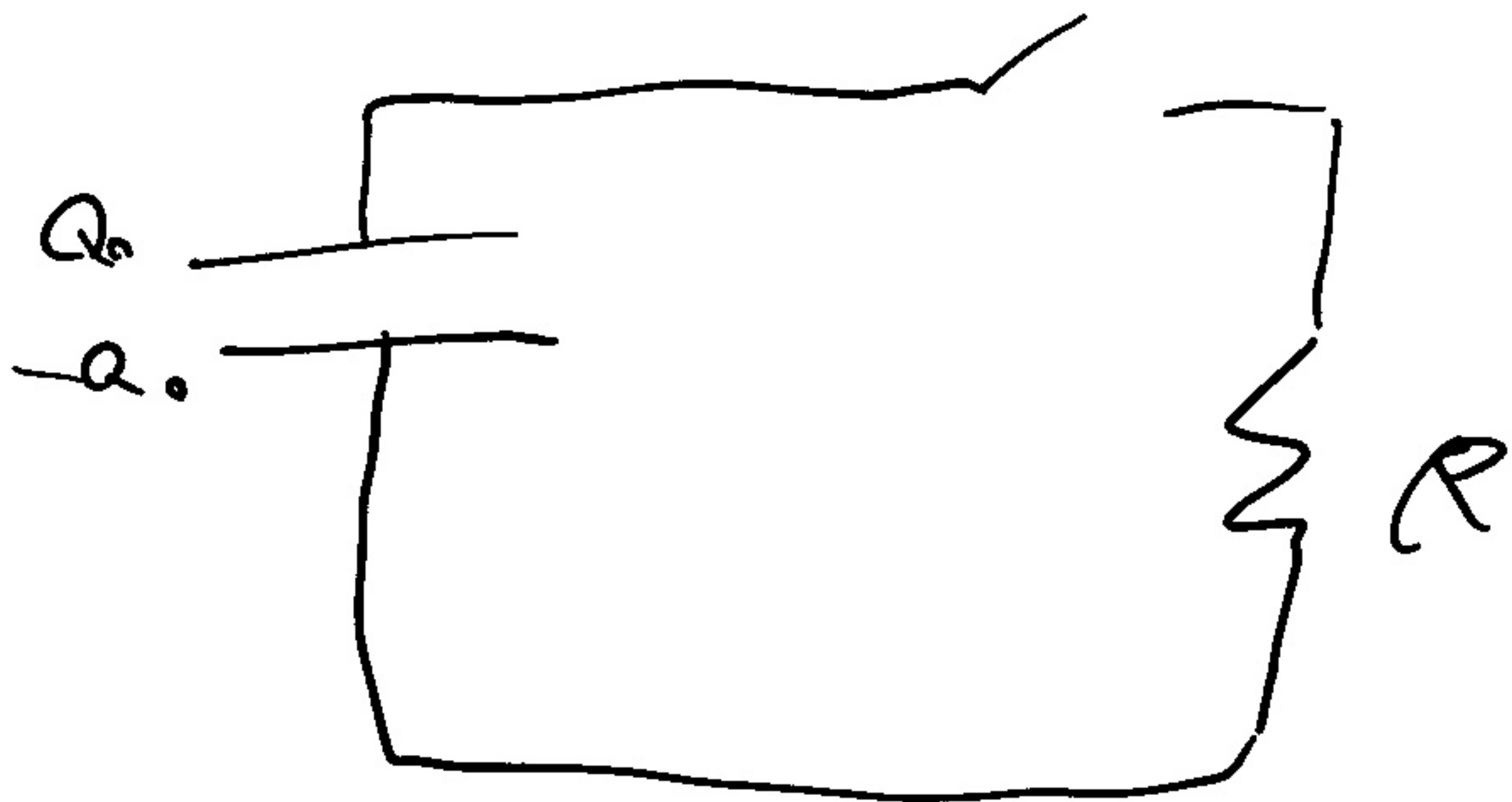

$$U_C = \frac{Q_0^2}{2C}$$

U dissipated in R

$$U_R = \int \frac{dU}{dt} dt = \int I^2 R dt$$

$$I(t) = I_0 e^{-t/RC} = \frac{Q_0}{RC} e^{-t/RC}$$

$$U_R = \int_0^{\infty} \frac{Q_0^2}{(RC)^2} e^{-2t/RC} \cdot R dt$$


$$= \frac{Q_0^2}{RC^2} \cdot \frac{-RC}{2} e^{-2t/RC} \Big|_0^{\infty}$$

$$= \frac{Q_0^2}{RC^2} \cdot \frac{RC}{2} = \frac{Q_0^2}{2C}$$

- All energy stored in capacitor dissipated in resistor

Charging Capacitor

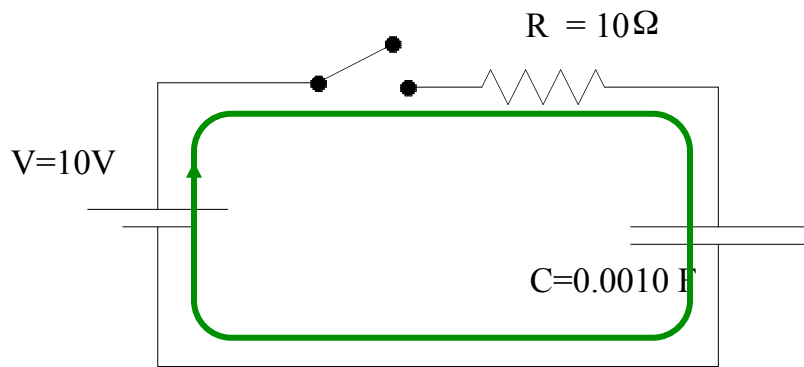More complex RC circuit: Charging C with a battery.



Before switch closed $i=0$, and charge on capacitor $Q=0$.

Close switch at $t=0$.

Try Voltage loop rule.

$$+V_b + V_R + V_C = 0$$


$$+V_b - iR - Q/C = 0$$

Charging Capacitor

$$+V_b - iR - Q/C = 0$$

$$+V_b - \frac{dQ}{dt}R - Q/C = 0$$




$$\frac{dQ}{dt} = +\frac{V_b}{R} - \frac{Q}{RC}$$


$$Q(t) = CV_b \left(1 - e^{-t/RC} \right)$$


Charging Capacitor

$$Q(t) = CV_b \left(1 - e^{-t/RC}\right)$$
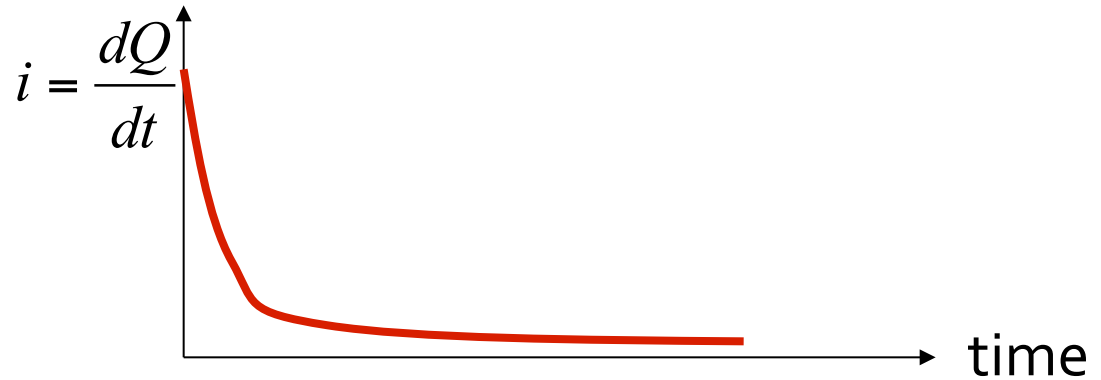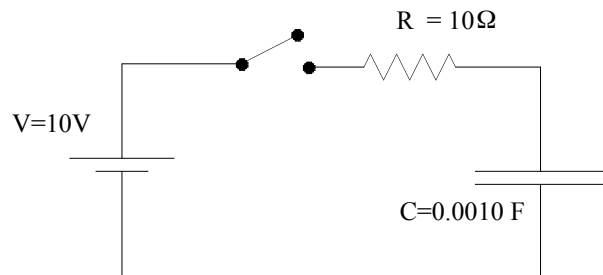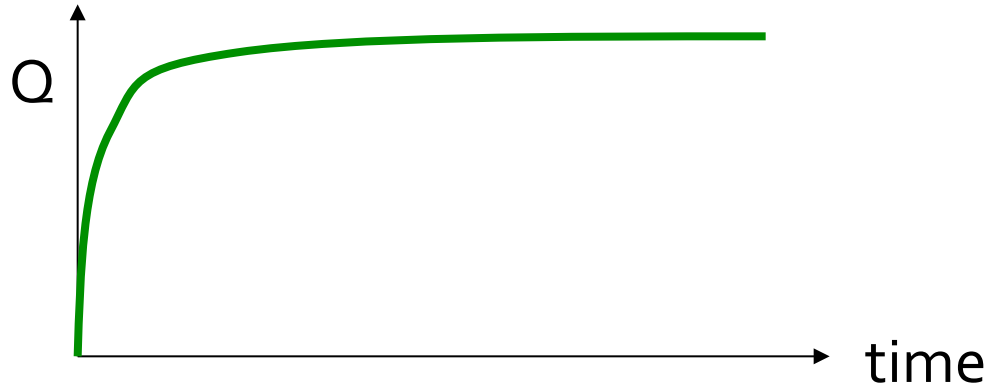
$$i(t) = \frac{dQ}{dt}(t) = \frac{V_b}{R} e^{-t/RC}$$



Energy Dissipation Charging

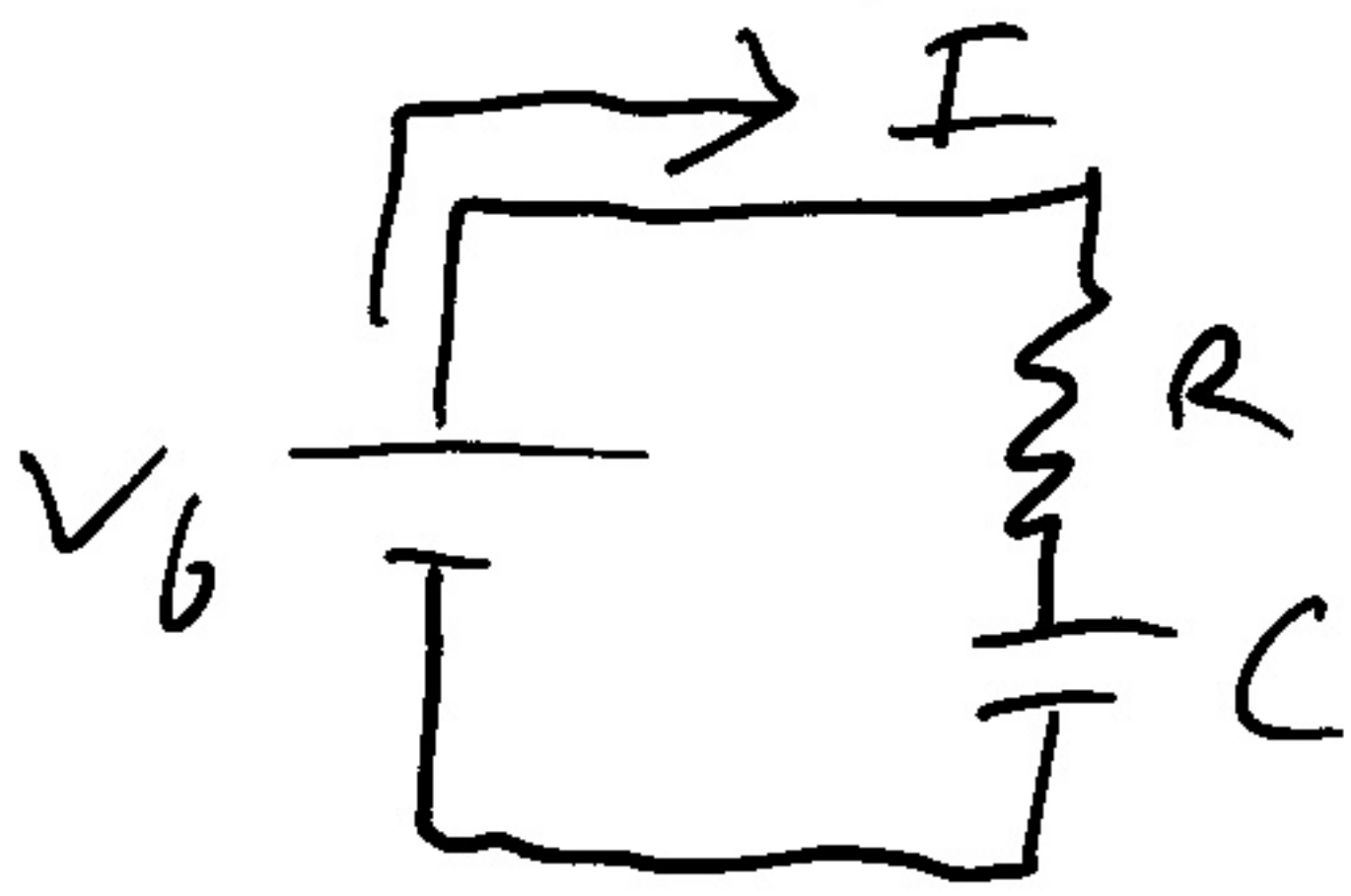

$$U_{\text{total}} = \int I V dt$$

$$= \int_0^{\infty} \frac{V_0}{R} - V_0 e^{-t/RC} dt$$

$$= \frac{V_0^2}{R} \cdot -RC e^{-t/RC} \Big|_0^{\infty}$$

$$= CV_0^2$$


$$U_C = \frac{1}{2} Q^2 / C = \frac{1}{2} CV_0^2 = U_{\text{total}} / 2$$

- Half of power dissipated in resistor while charging, half goes to capacitor

Concept Check

An RC circuit is shown below. Initially the switch is open and the capacitor has no charge. At time $t=0$, the switch is closed. What is the voltage across the capacitor *immediately* after the switch is closed (time = 0)?

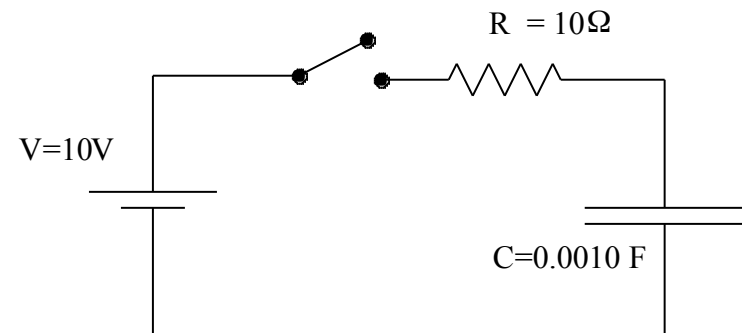- A) Zero
- B) 10 V
- C) 5V
- D) None of these.



Capacitor in Circuit

Although no charge actually passes between the capacitor plates, it acts just like a current is flowing through it.

Uncharged capacitors act like a “short” : $V_C = Q/C = 0$

Fully charged capacitors act like an “open circuit” . Must have $i_C = 0$ eventually, otherwise $Q \rightarrow \text{infinity}$.

Happy Spring Break!



Where I wish I was going to be...