

# Physics II: 1702

## Gravity, Electricity, & Magnetism

Professor Jasper Halekas


Van Allen 70 [Clicker Channel #18]

MWF 11:30-12:30 Lecture, Th 12:30-1:30 Discussion

# Announcements


- I will be on travel Tuesday and Wednesday
- All Tues/Wed office hours are canceled
  - Appointments available Thursday/Friday if needed
- Guest Lecturer Wednesday: Prof. Howes

# LC Circuit

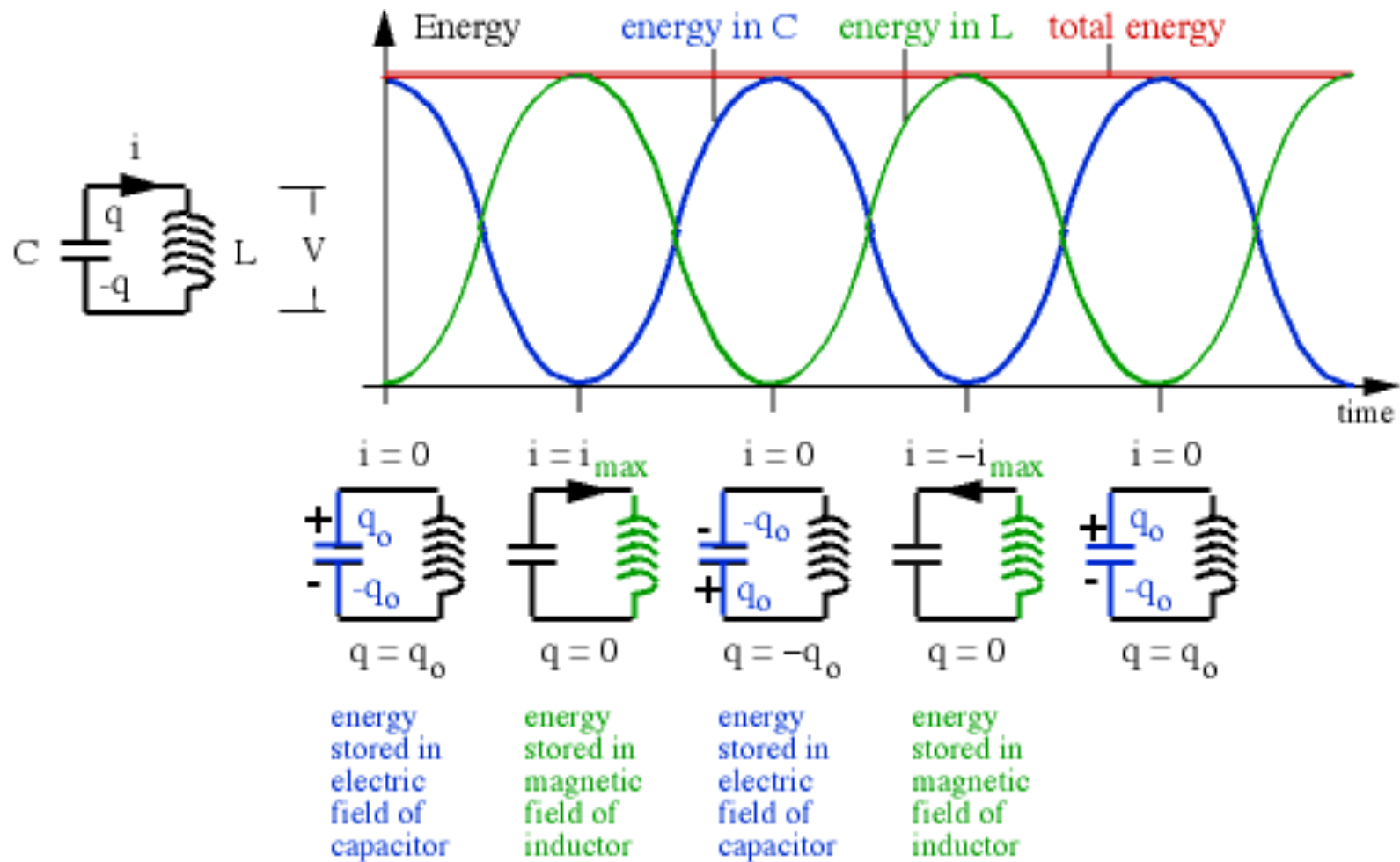

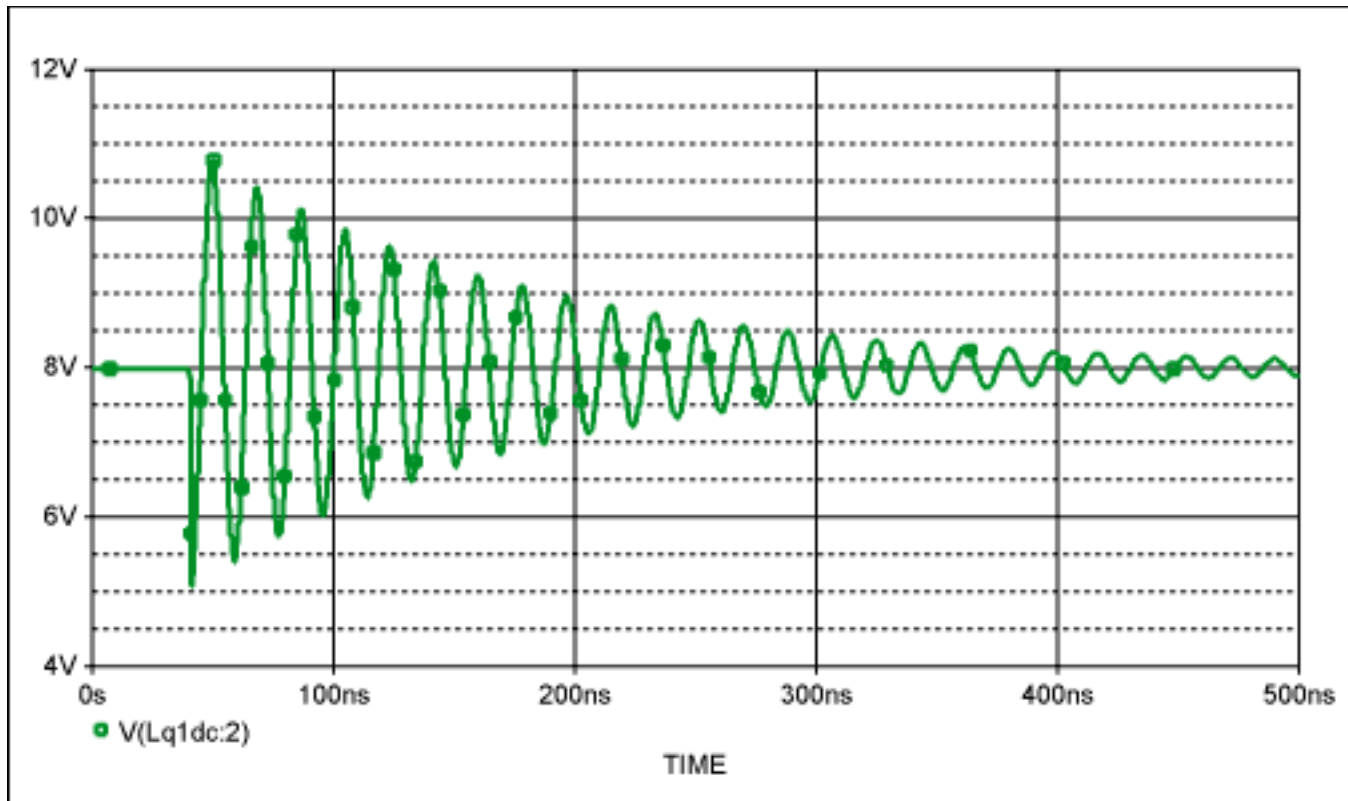
# RLC Circuit

- Any real circuit has some resistance...



# RLC circuit

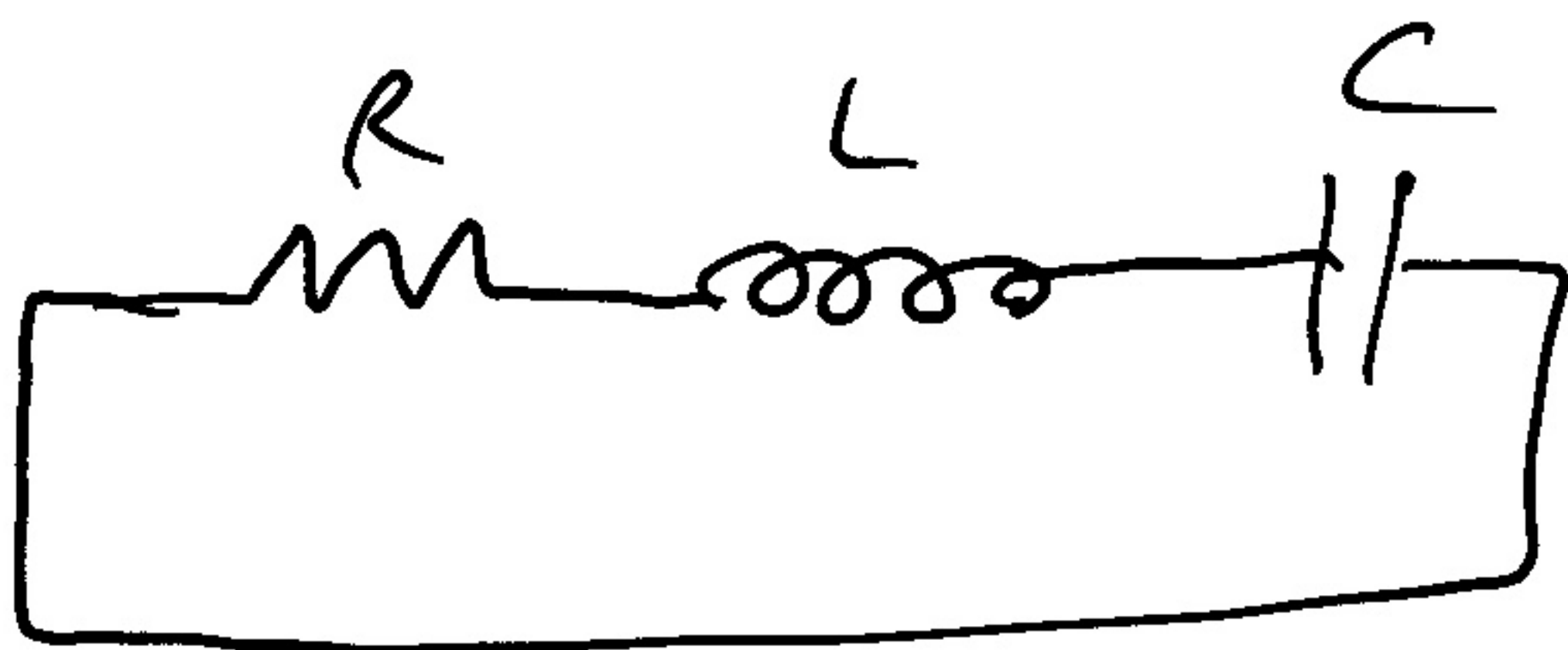

$$IR + L \frac{dI}{dt} + \frac{Q}{C} = 0$$

$$\text{or } LQ'' + RQ' + \frac{Q}{C} = 0$$

$$\Rightarrow Q'' + \frac{R}{L}Q' + \frac{Q}{LC} = 0$$

$Q = A e^{i\omega t}$  works for LC

so let's try it again

$$\Rightarrow -\omega^2 Q + \frac{R}{L} \cdot i\omega Q + \frac{1}{LC} Q = 0$$

$$-\omega^2 + \frac{R\omega}{L}i + \frac{1}{LC} = 0$$

$$\text{or } \omega^2 - i\frac{R\omega}{L} - \frac{1}{LC} = 0$$

use quadratic formula

$$\Rightarrow \omega = \left( \frac{iR}{L} \pm \sqrt{-\frac{R^2}{L^2} + \frac{4}{LC}} \right) / 2$$

$$= \frac{iR}{2L} \pm \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

$$= \frac{iR}{2L} \pm \omega'$$

$$\omega / \omega' = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

$$\Rightarrow Q(t) = A e^{i(\gamma_{RL} + \omega')t} + B e^{i(\gamma_{RL} - \omega')t}$$
$$= e^{-\frac{R}{2L}t} [A e^{i\omega't} + B e^{-i\omega't}]$$

could also write in terms  
of sines and cosines

$$Q(t) = e^{-\frac{R}{2L}t} [C \cos(\omega't) + D \sin(\omega't)]$$

- Oscillations change frequency  
from pure LC case and  
damp as a function of time
- This is a damped harmonic  
oscillator

# AC Circuits

## AC Circuits

The Voltage in your wall sockets at home is AC.


AC stands for Alternating Current, but would perhaps more appropriately be called Alternating Voltage.

Alternating = Sinusoidal with time

# Sinusoidal Oscillations

$$V(t) = V_{peak} \sin(\omega t)$$


$$\omega = 2\pi f = \frac{2\pi}{T}$$

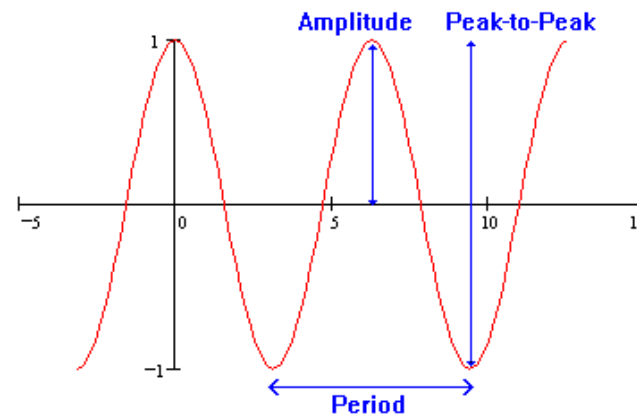

$\omega$  is the **angular frequency** (radians / second)  
f is the **frequency** in (cycles / second = Hertz)  
T is the **period** in (seconds), i.e. time for one cycle



# Standard US Power

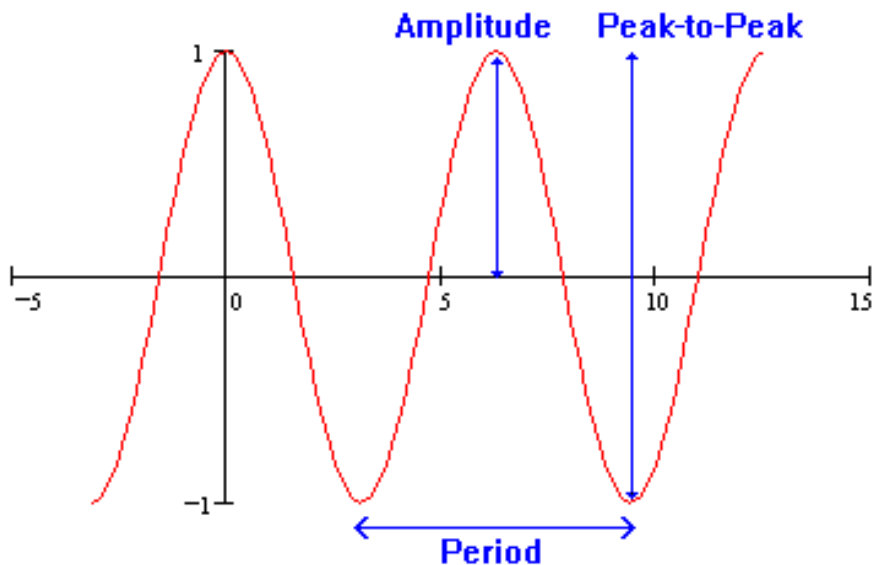

In the United States of America

$f = 60$  cycles/second or Hertz

$T = (1 / 60)$  seconds

$V_{\text{peak}} = 170$  Volts

One might be interested in something like the average Voltage.  
But, the average  $V(t) = 0$ .

# AC Voltage Levels

$$V_{rms} = V(\text{root mean square}) = \sqrt{\langle V^2 \rangle}$$

Time Average of Voltage squared.

$$V_{rms} = V_p \sqrt{\langle \sin^2(\omega t) \rangle} = V_p \sqrt{1/2} = V_p / \sqrt{2}$$


Time Average of  $\sin^2$  or  $\cos^2$  over many cycles =  $1/2$

$$V_{rms} = 170V / \sqrt{2} = 120 \text{ Volts}$$

This is how we refer to the US Standard Voltage.

# AC Power

Example: AC Voltage across a resistor

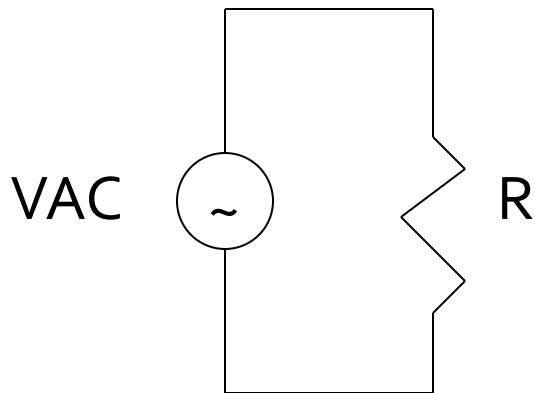

$$V(t) = V_p \sin(\omega t)$$

$$i(t) = \frac{V}{R} = \frac{V_p \sin(\omega t)}{R} = i_{peak} \sin(\omega t)$$

$$P(t) = iV = i_{peak} V_p \sin^2(\omega t)$$


Instantaneous Power is oscillating from zero to maximum.

# AC Power

$$\int \sin^2(\omega t) dt = \int [1/2 - 1/2 \cos(2\omega t)] dt$$

$$\int \sin^2(\omega t) dt = \frac{1}{2}$$

When integrated over a complete cycle.

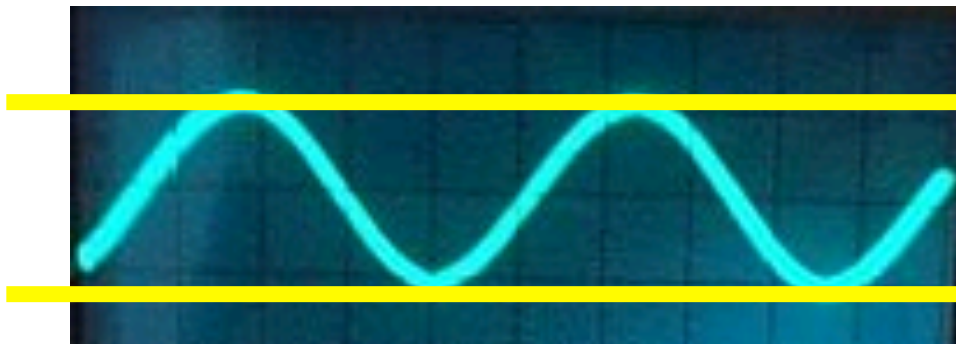

Power = maximum

Power = 0

# AC Power

$$P(t) = iV = i_{peak}V_{peak} \sin^2(\omega t)$$

$$\langle P(t) \rangle = i_{peak}V_{peak} \langle \sin^2(\omega t) \rangle = \frac{1}{2} i_{peak}V_{peak}$$

$$\langle P(t) \rangle = \left( \frac{1}{\sqrt{2}} i_{peak} \right) \left( \frac{1}{\sqrt{2}} V_{peak} \right)$$

$$P_{ave} = i_{rms} V_{rms}$$

Same form as before, but now RMS values.

# Why AC Voltage?

Why do we use AC Voltage in the United States and most of the world?

1. One reason is the ease of generating from a power generator. A rotating coil in a magnetic field creates an induced current, but it is sinusoidally alternating.
2. AC turns out to be easy to change from one peak Voltage level to another, using a [Transformer](#).


# Concept Check

Q17) The voltage across and the current through a single circuit element connected to an ac generator are shown in the graph. Which one of the following statements concerning this circuit element is true?




- 1) The element is a resistor.
- 2) The element is a capacitor.
- 3) The element is an inductor.
- 4) The element could be a resistor or an inductor.
- 5) The element could be an inductor or a capacitor.

# Driven AC Circuits: Resistor

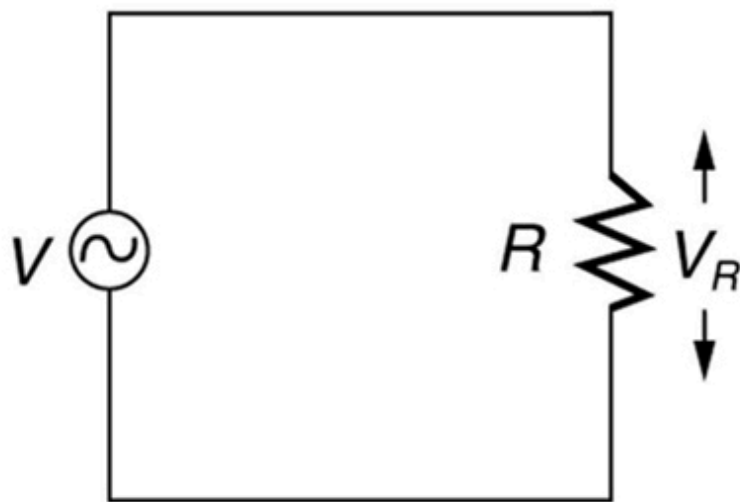


(a)

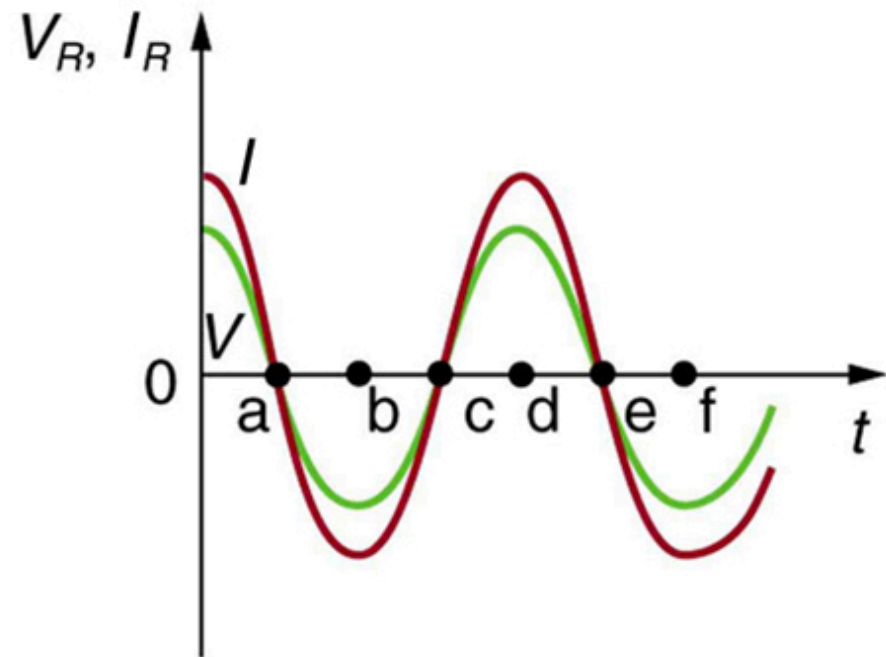


(b)



# Driven AC Circuits: Capacitor

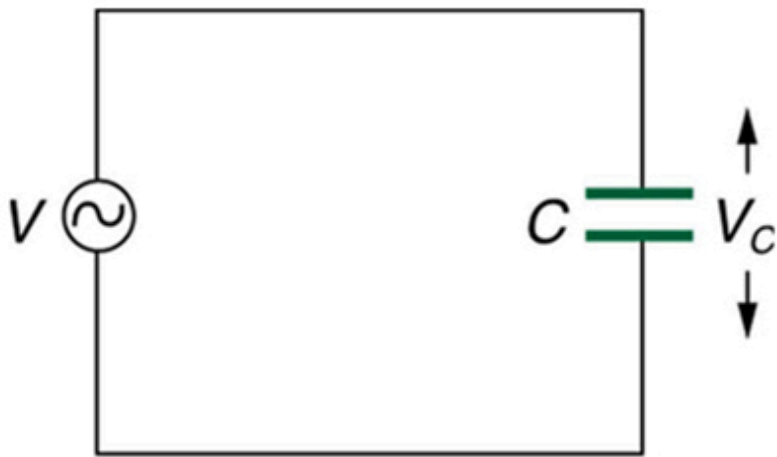

(a)

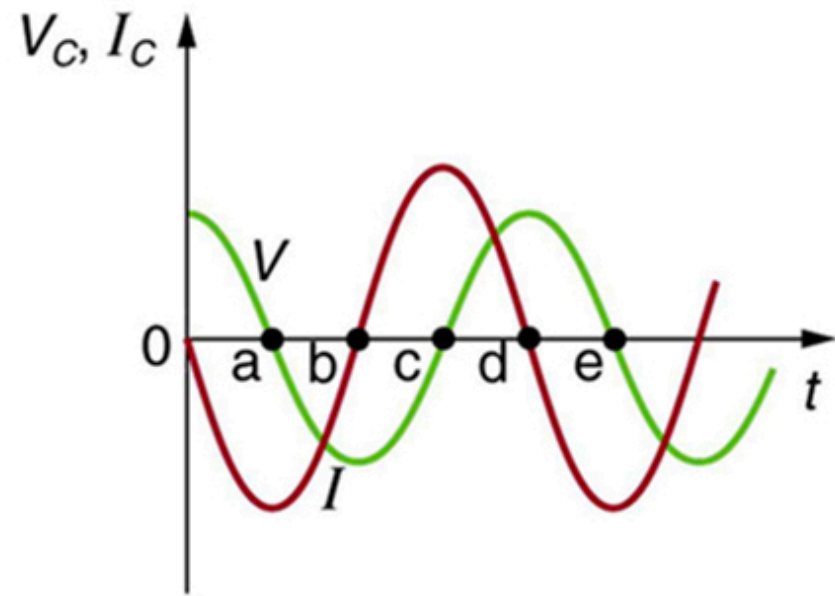


(b)

Current "Leads"

# Driven AC Circuits: Inductor




(a)

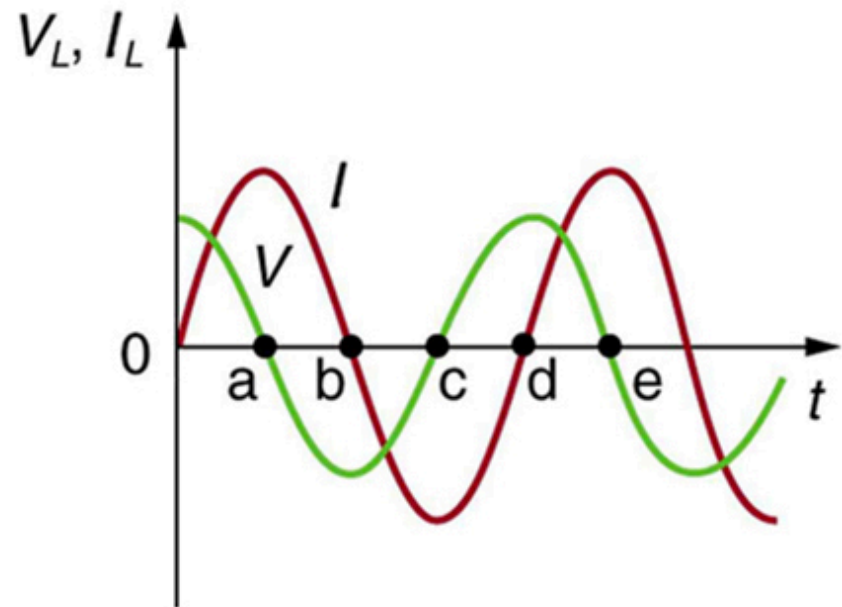


(b)

Current "Lags"

# The Unit Circle in Trigonometry

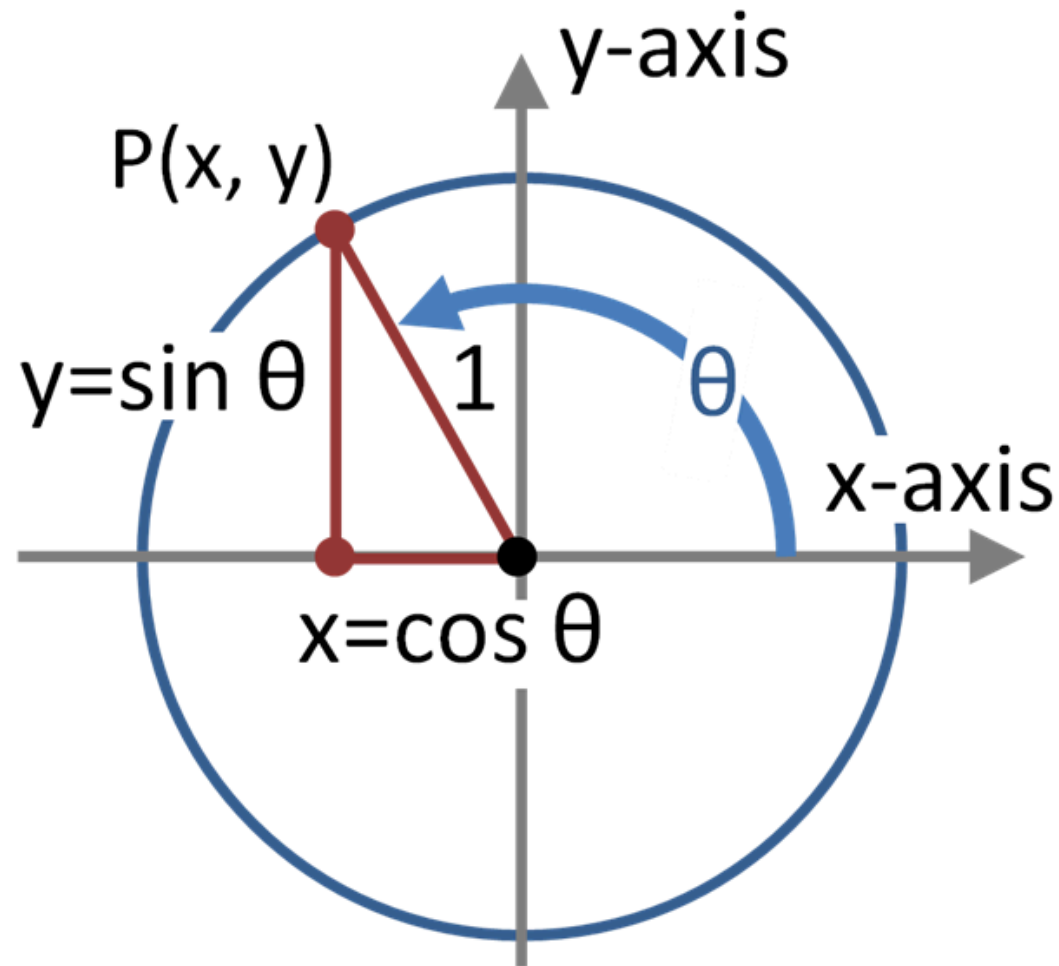


# Phasor Representation

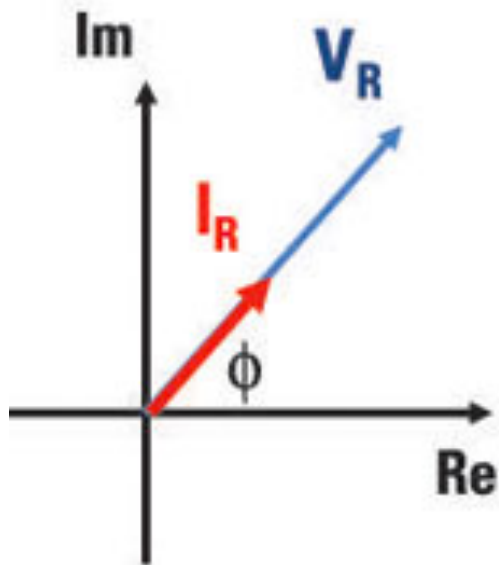


**Resistor**

Voltage in phase  
with current

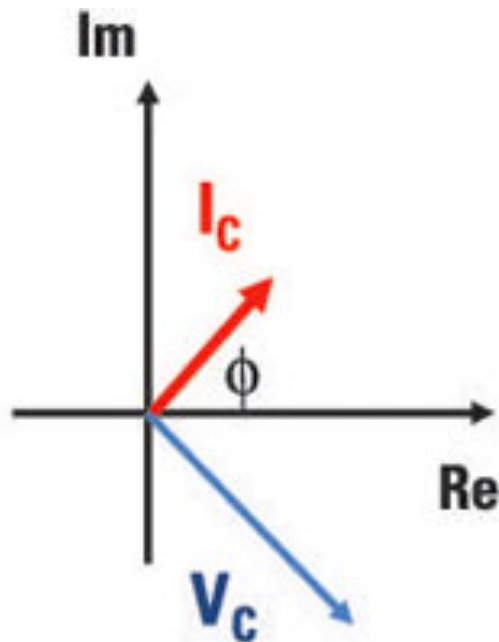

**Capacitor**

Voltage lags  
current by  $90^\circ$

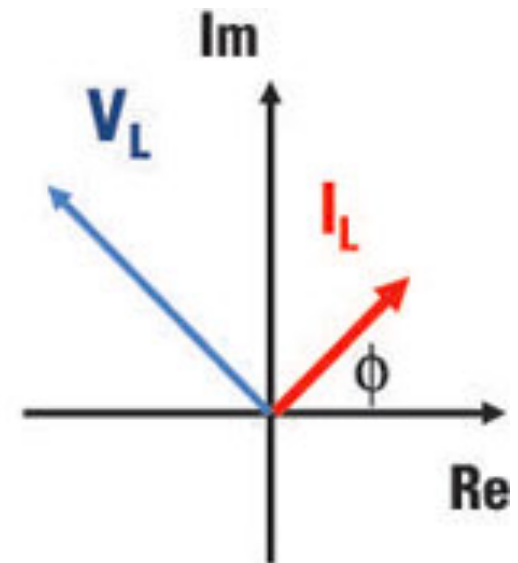

**Inductor**

Voltage leads  
current by  $90^\circ$